

Roll No. ....

Total Pages : 3

**BT-3/D-18****33083****DIGITAL ELECTRONICS**

Paper : CSE-207(N)

Time : Three Hours]

[Maximum Marks : 75

**Note :** Attempt five questions in all, selecting at least *one* question from each unit. All questions carry equal marks.

1. (a) State De-Morgan's Theorem. 3
- (b) Discuss BCD adder design procedure. 4
- (c) Draw pin configuration of 555 timer IC. 4
- (d) Explain memory decoding. 4

**UNIT-I**

2. Discuss Quine Mc-Clusky (QMC) method of Minimization. Simplify the following expression using QMC method also verify the results by K map method

$$F = \sum_{A,B,C,D} m(1, 4, 5, 6, 12, 13, 14) + \sum d(0, 8, 9, 11).$$

15

3. (a) Write the small note on the following :

(i) CMOS characteristics.

(ii) Principle of duality. 10

- (b) Realize the following logic equation using only NAND gates :

$$AB + CD = AB \cdot CD.$$

5

33083/2,500/KD/2091

[P.T.O.  
20/12**UNIT-II**

4. (a) Differentiate between serial adder and parallel adder with the help of full adder block diagram. 10
- (b) Explain magnitude comparator. 5
5. Design a BCD-to-Gray code convertor using
  - (a) 8 : 1 multiplexer.
  - (b) Dual 4 : 1 multiplexers and some gates.
  - (c) NAND gates only. 15

**UNIT-III**

6. (a) Explain the operation of twisted ring counter and give its state diagram. 8
- (b) Explain master slave flip-flop with the help of diagram. 7
7. Write short notes on the following :
  - (a) Shift register counter.
  - (b) Modulo-n counter.
  - (c) Sequence generator. 15

**UNIT-IV**

8. (a) What is dynamic RAM? Explain its cell structure. 7
- (b) Explain the following in brief :
  - (i) EPROM.
  - (ii) EAPROM. 8

33083/2,500/KD/2091

2

9. Write short notes on the following :

- (a) Memory expansion.
- (b) Implementation of PLA using ROM.
- (c) FPGA.

15

---

<http://www.kuonline.in>

Whatsapp @ 9300930012

Your old paper & get 10/-

पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से