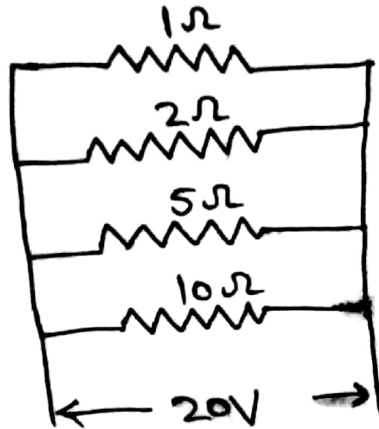


Unit - 1 Numerical Practice set


By: Rajeev Saini

1. For the given circuit, find the total resistance and the current through each branch.



Ans $\rightarrow 20, 10, 4, 2$
(All in Amperes)

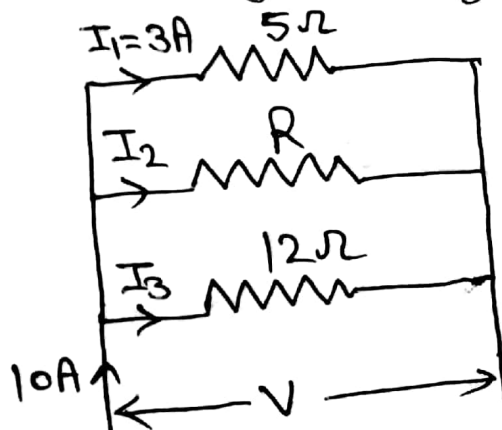
2. Find the value of unknown resistance R and total circuit resistance for the given circuit.




Ans $\rightarrow 2.6087\Omega,$
 1.5Ω

3. Determine the current delivered by the source in the circuit given below:

Ans $\rightarrow 28.46A$

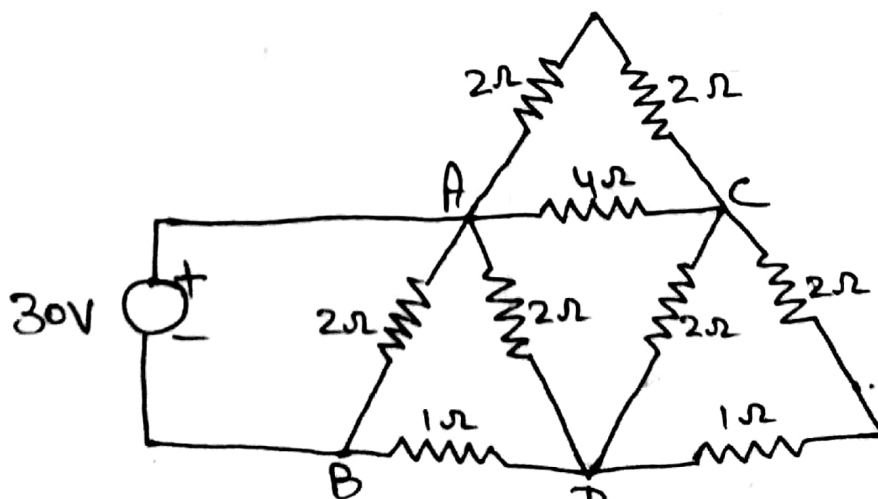


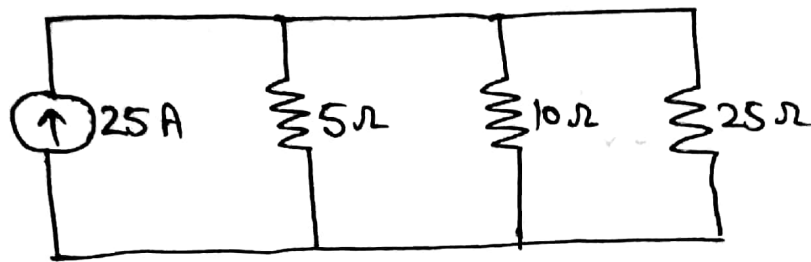4. Determine the current in all resistors in the circuit given below:




Ans \rightarrow 14.705 A,
7.3529 A,
2.9412 A.

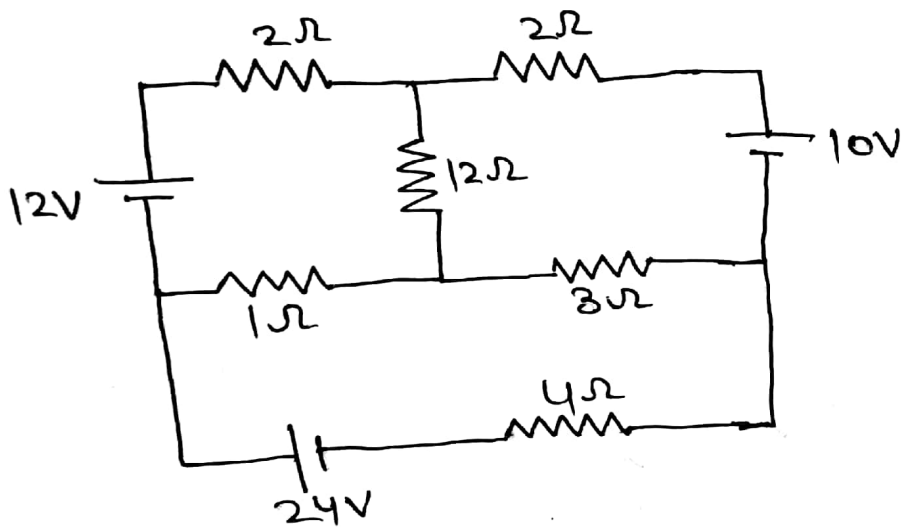5. Determine the current in the 4Ω branch using mesh analysis method.




Ans \rightarrow 4.1114 A.

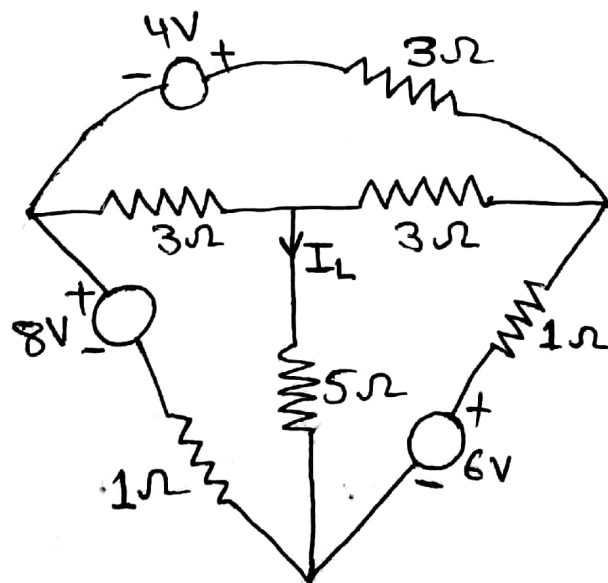6. Determine the current I_L in the circuit shown below.




Ans \rightarrow 1 A

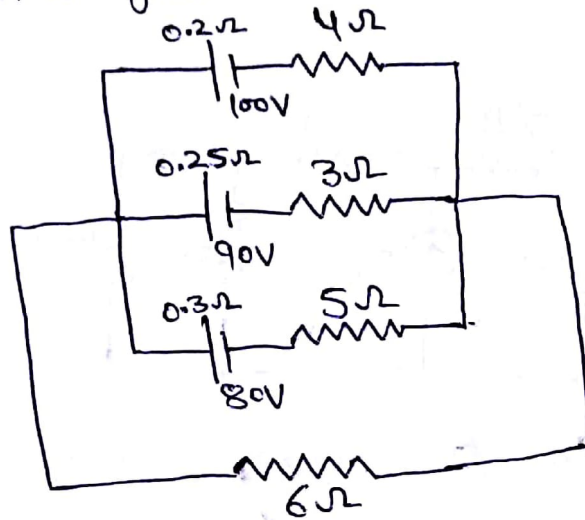7. Solve the network for the current through 6Ω resistor using mesh analysis.




Ans $\rightarrow -12.339A$

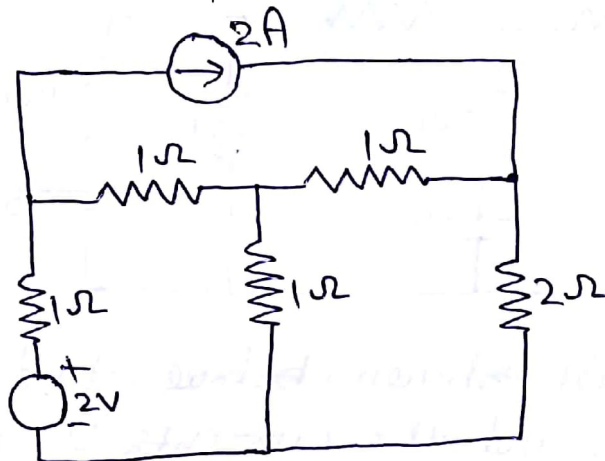8. i) Find out loop currents for the circuit given below
 (ii) Find current thro. 2Ω resistor.
 (iii) Find Power delivered by $2V$ voltage source.




(i)
 Ans $\rightarrow 1.636A,$
 $0.901A,$
 $2A,$
 (ii) 0.901
 (iii) $3.272W$

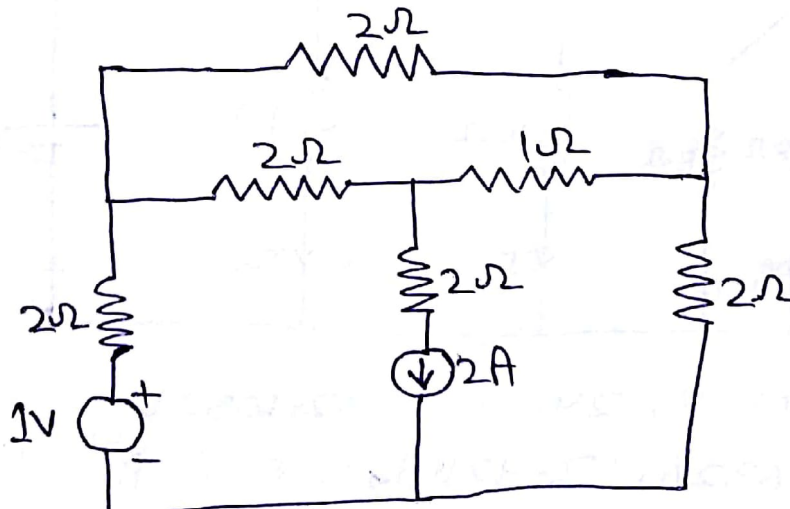9. Find out the current in each mesh using mesh current analysis for the circuit given below:




Ans $\rightarrow 1.1154A$
 $0.8846A$
 $0.2692A$

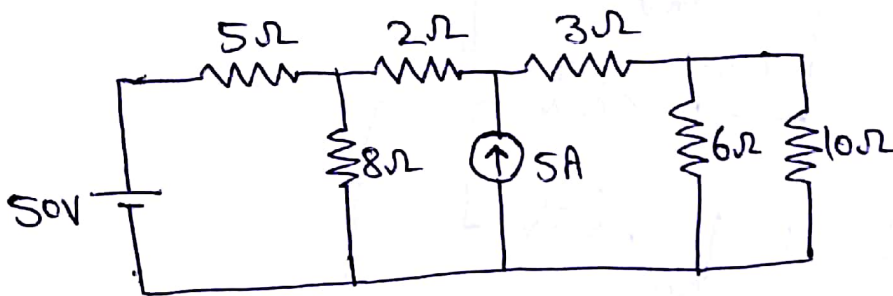10. Determine the voltage at each node and current through each element in the circuit by node voltage method.




Ans → 31.526V
32.018V
17.769V
3.695A
0.246A
4.7496A
3.941A
2.962A
1.7769A

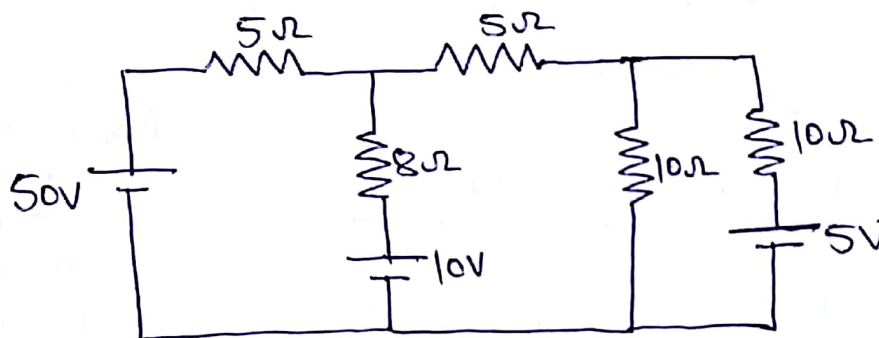11. For the circuit shown below, find the current in each branch by nodal Analysis.




Ans → 4.588A
2.1324A
2.4559A
1.4779A
1.9559A

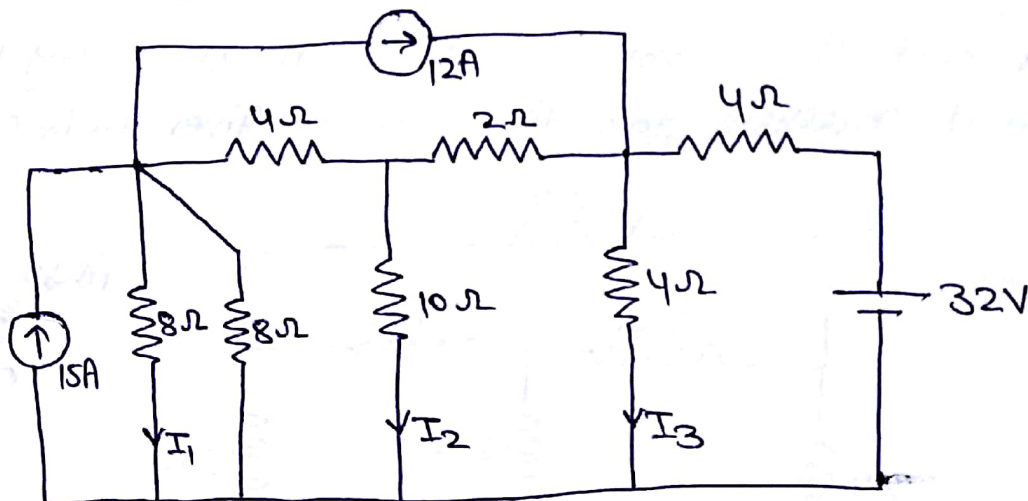12. In the circuit shown below, find the different node voltages and the currents I_1 , I_2 & I_3 .




Ans → 18.1052V, 24.211V, 32.1052V
2.2632A, 2.4211A, 8.0263A

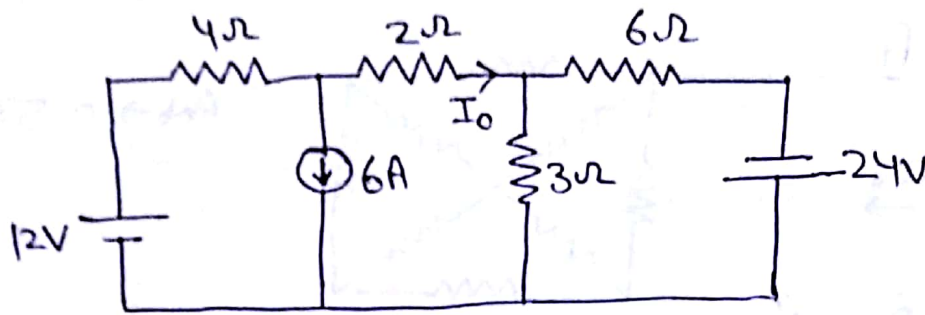13. Use source transformation to find I_0 in the circuit given below.




Ans $\rightarrow -0.5A$

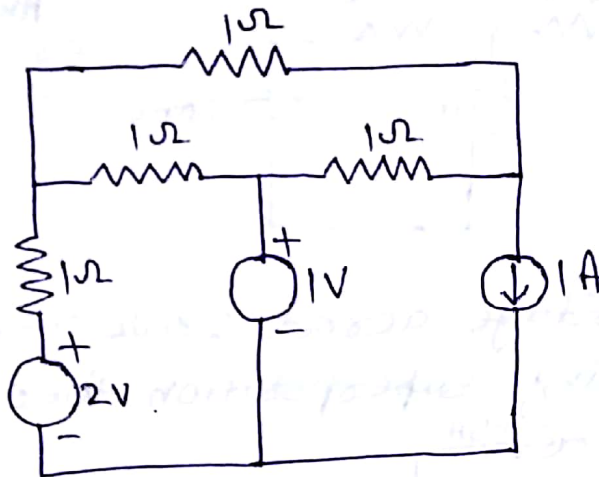14. For the given circuit, find out the current in each branch using nodal analysis.




Ans $\rightarrow 0.2A, 0.8A, 0.6A, 0.4A.$

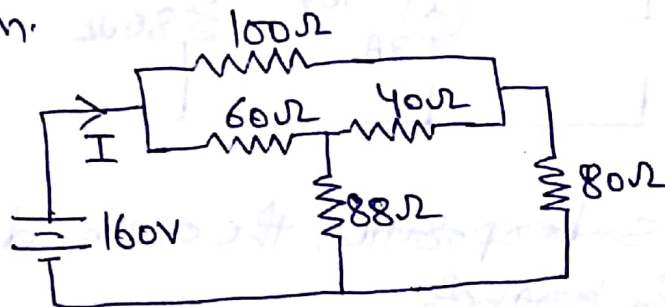15. Determine the current I using Star-Delta transformation.




Ans $\rightarrow 2A.$

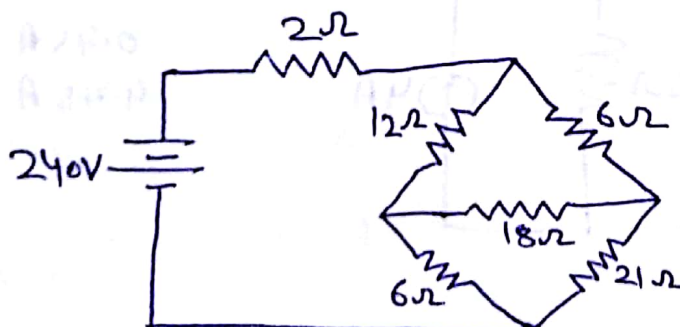16. Find the current I , using Star-Delta transformation.




Ans $\rightarrow 20A$

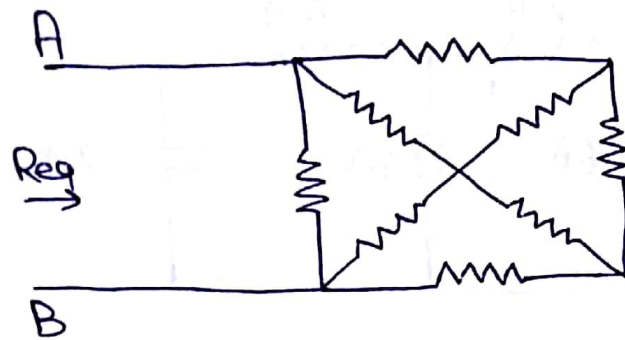17. Calculate the equivalent resistance R_{ab} when all the resistance values are equal to 1Ω .




Ans $\rightarrow 0.533\Omega$

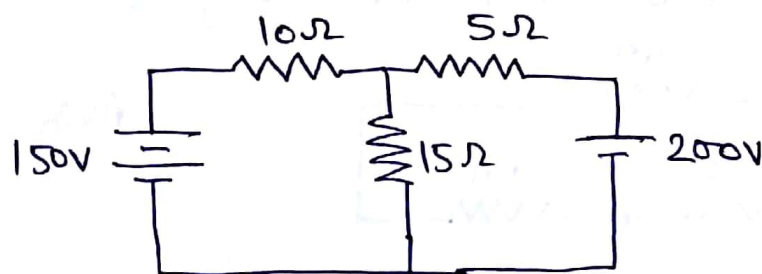18. Find the current through 15Ω resistor using superposition theorem.




Ans $\rightarrow 10A$

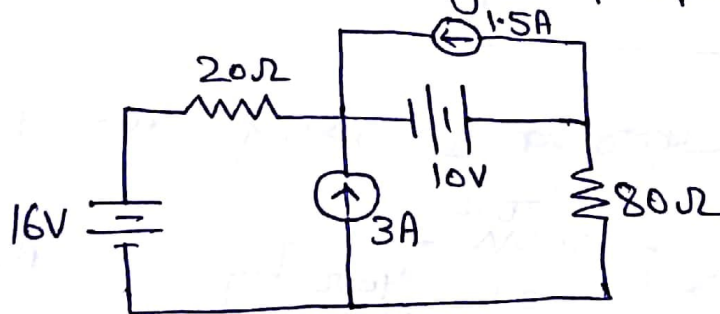19. Determine the voltage across 20Ω resistance in the circuit using superposition theorem.



Ans $\rightarrow 42.8V$

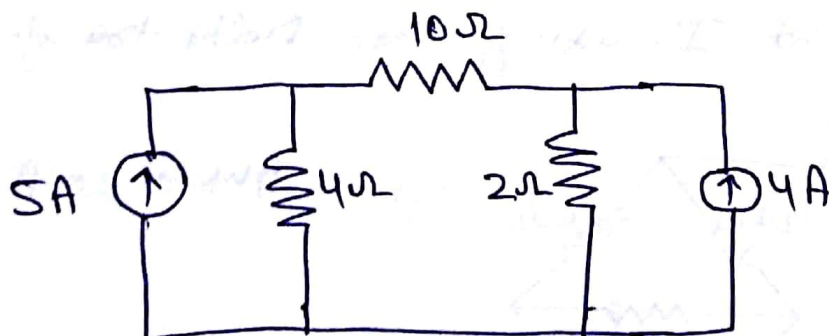20. Using superposition theorem, determine the current in each branch.




Ans $\rightarrow 4.25A$

$0.75A$


$4.75A$

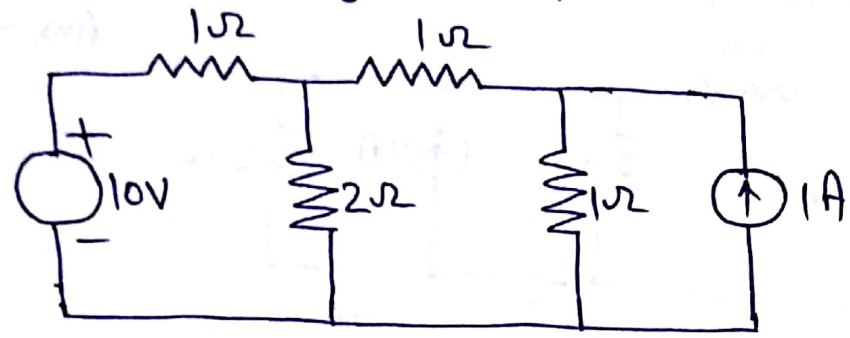21. Calculate the current through 2Ω resistor in the circuit using superposition theorem.




Ans $\rightarrow 2.625A$.

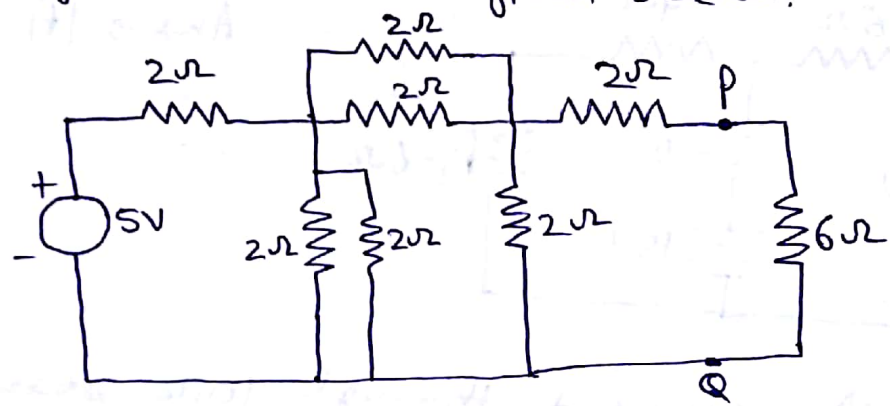22. Determine the Thevenin's equivalent across terminal PQ for the circuit given below:




Ans $\rightarrow E_{th} = 0.909V$
 $R_{th} = 2.909\Omega$

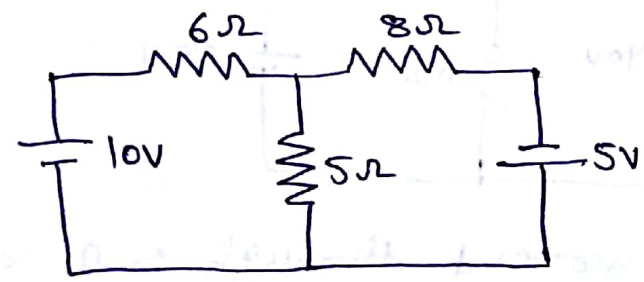23. Determine the value of current through 5Ω resistance using Thevenin's theorem



Ans $\rightarrow 0.4236A$

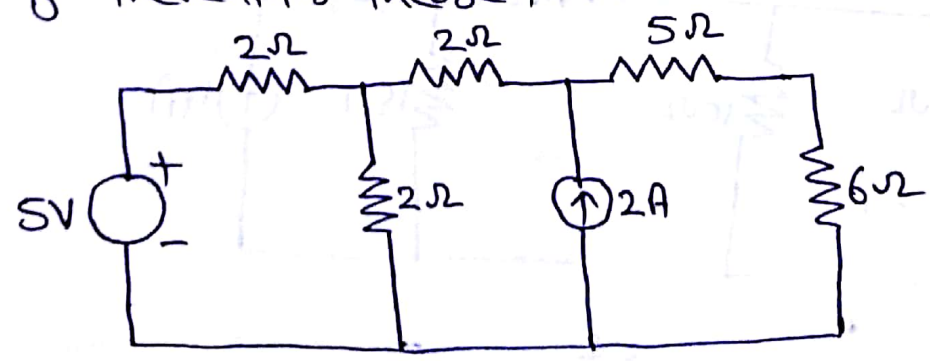
24. Determine the value of current through 6Ω resistance using Thevenin's theorem.



Ans $\rightarrow 0.607A$


25. Calculate the current through 2Ω resistor using Thevenin's theorem.

Ans $\rightarrow 0.4A$

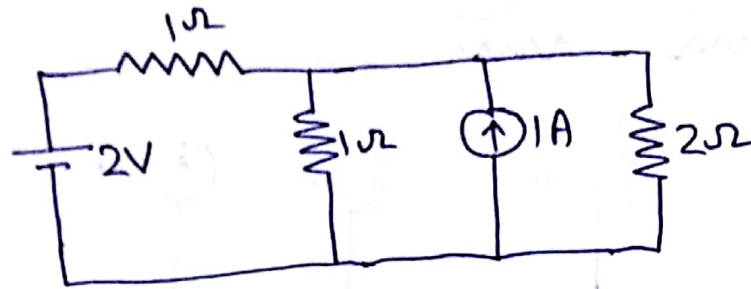


26. Calculate the current through $R_L = 6\Omega$ resistance using Thevenin's theorem.

Ans $\rightarrow 1A$

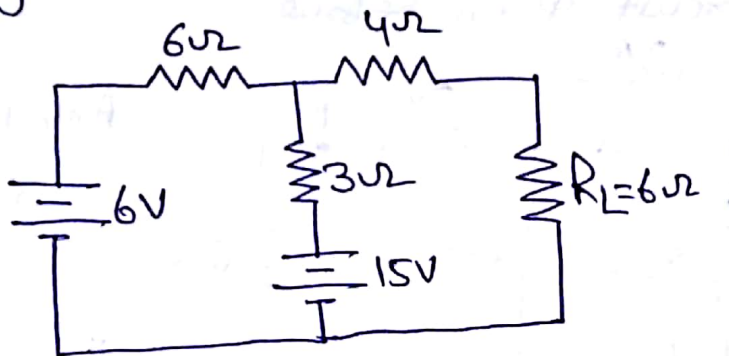


27. Calculate the current through 10Ω resistance using Thevenin's theorem.

Ans $\rightarrow 3.98A$

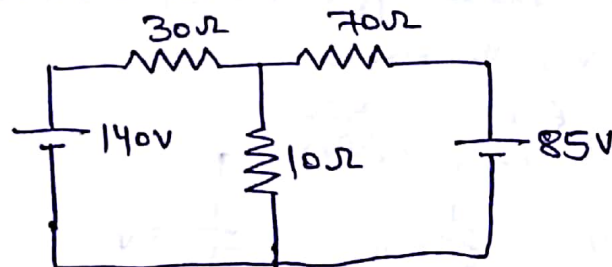


28. Calculate the current through 5Ω resistor using Thevenin's theorem.

Ans $\rightarrow 2.78A$

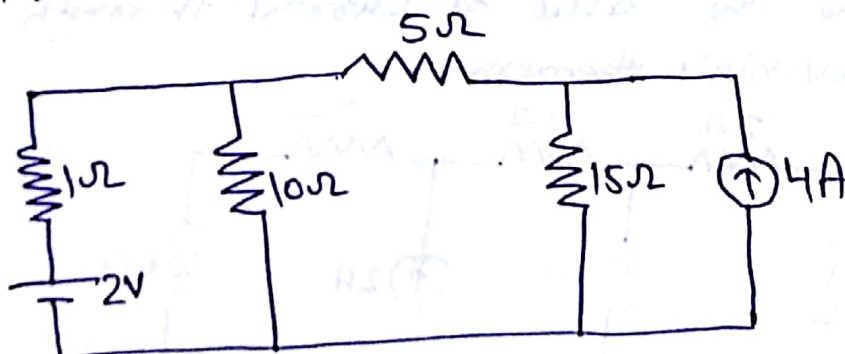


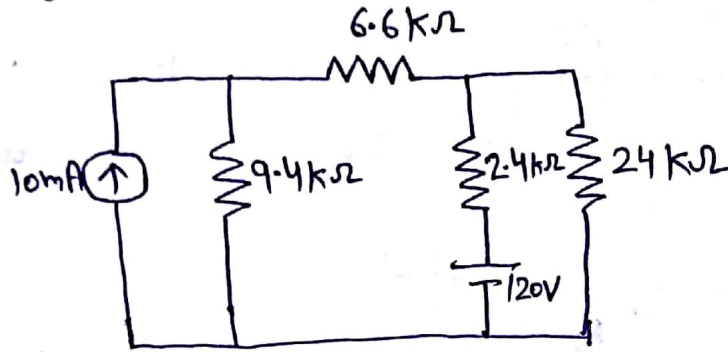29. Find the value of current through $24\text{ k}\Omega$ resistance using Norton's theorem. Rajeev saini 5.




Ans $\rightarrow 4.47\text{ mA}$

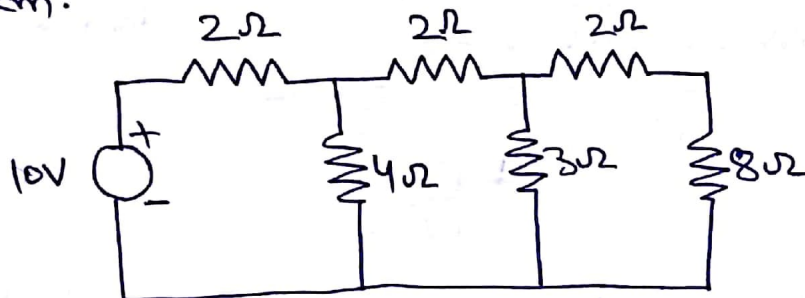30. Find current through 8Ω resistance using Norton's theorem.




Ans $\rightarrow 0.2728\text{ A}$

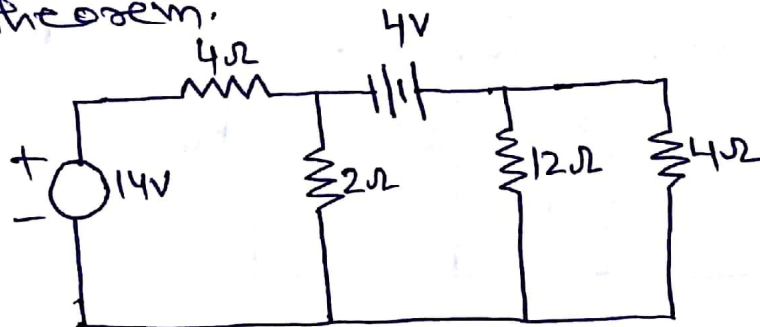31. Find the voltage drop across 12Ω resistance using Norton's theorem.




Ans $\rightarrow 6\text{ V}$

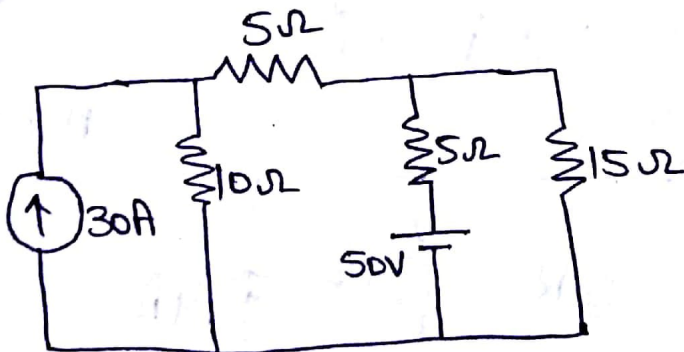32. Find the value of current through 15Ω resistor using Norton's theorem.




Ans $\rightarrow 6\text{ A}$

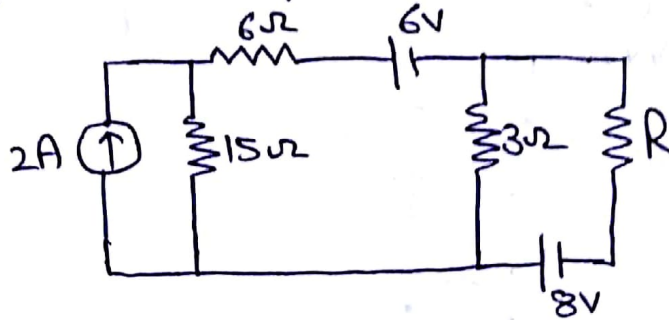33. Find the value of resistance 'R' to have maximum power transfer in the circuit below. Also obtain the value of maximum power.




Ans $\rightarrow \frac{21}{8} \Omega$,
 11.524 W

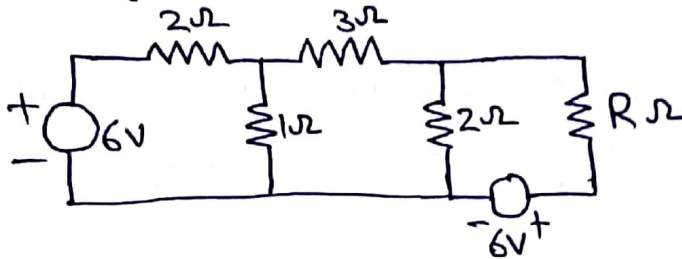34. Find the value of R in the circuit such that maximum power transfer takes place.




Ans $\rightarrow 1.29 \Omega$

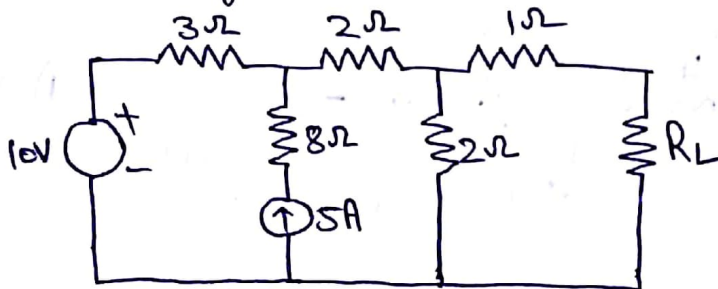35. Find the value of R_L in the circuit such that maximum power transfer takes place.



Ans $\rightarrow 2.4286 \Omega$

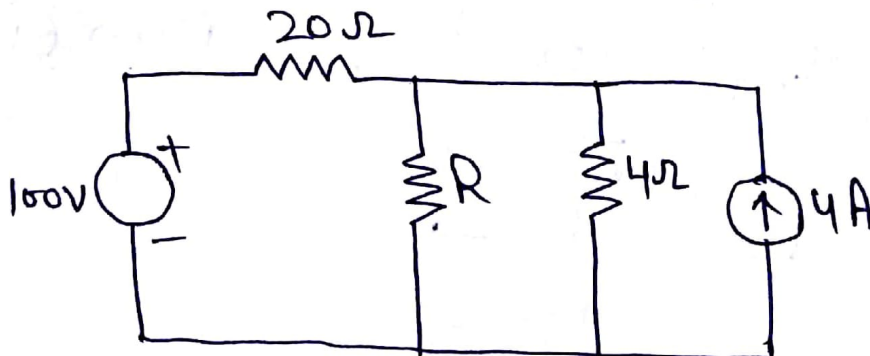36. For the circuit shown below, find the value of 'R' for maximum power transfer & also find out the maximum value of Power.



Ans $\rightarrow 3.333 \Omega$
 67.507 W