

## ASSIGNMENT No. 2

- Q1 Find selectivity, half power frequencies and Bandwidth for series RLC resonant circuit.
- Q2 A coil of resistance  $1.5\Omega$  and impedance  $6\Omega$  is placed in series with a second coil of resistance  $2\Omega$ . When a voltage of  $230V$ ,  $50Hz$  is applied to the circuit, the current flowing through the circuit is  $7A$ . Find the inductance of second coil.
- Q3 Two currents  $i_1$  &  $i_2$  are given by the expression  $i_1 = 15\sin(\omega t + \pi/3)$  and  $i_2 = 5\sin(\omega t - \pi/3)$ . Find  $i_1 - i_2$ .
- Q4 A coil of resistance  $10\Omega$  and inductance  $0.1H$  is connected in series with a condenser of capacitance  $150\mu F$  across a  $200V$ ,  $50Hz$  supply. Determine (i) Impedance (2) current (3) Power Factor (4) Voltage across the coil (5) Voltage across the Condenser.

Q5 An ac circuit consists of pure resistance and a coil in series. The power dissipated in the resistance is 500 W and the drop across it is 100 V. The power dissipated in the coil is 100 W and drop across it is 50 V. Find the inductive reactance of the coil and supply voltage.

Q6 Find out the active power delivered in Watt, to an impedance  $Z = (4 - j3) \Omega$  by a current  $i = 5 \cos(100\pi t + 100)^\circ$  A

Q7 A periodic waveform has been shown. Determine (1) frequency (2) RMS, Avg Value (3) Form Factor

