


# EXPERIMENT NO. 1

**AIM:** To verify Kirchoff's current law and voltage law.


**APPARATUS:** DC supply (0-9V), Voltmeter (0-9V), Ammeter (0-60A), Resistors ( $200\Omega$ ,  $100\Omega$ ,  $400\Omega$ ), connecting wires.

**CIRCUIT DIAGRAM:**

For KCL :-

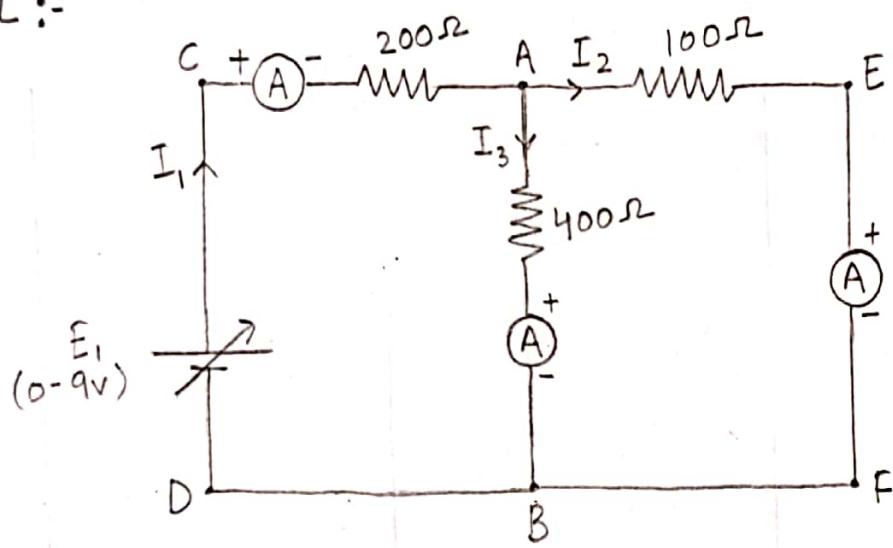

For KVL :-

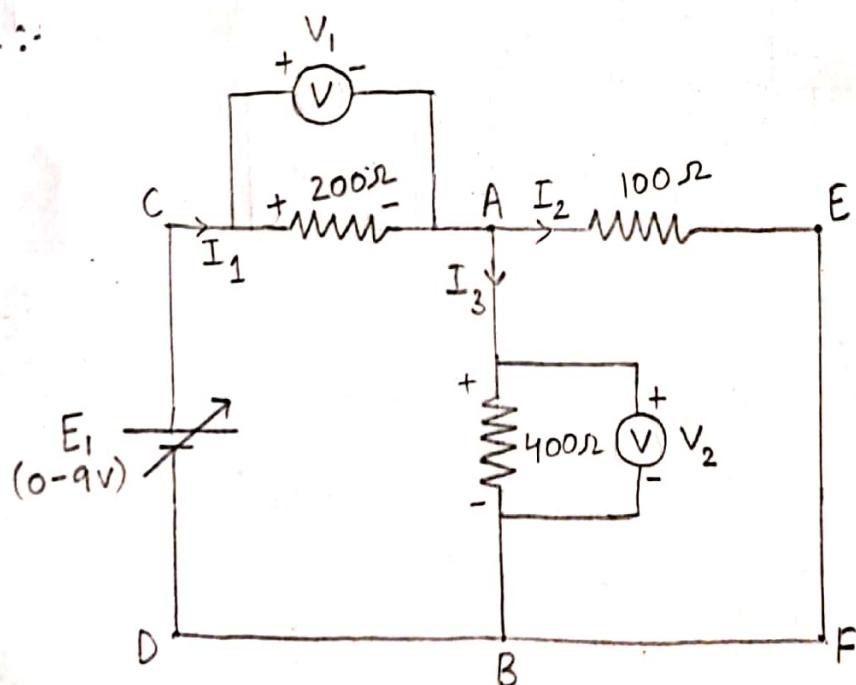

# EXPERIMENT NO. 1

**AIM:** To verify Kirchoff's current law and voltage law.

**APPARATUS:** DC supply (0-9V), voltmeter (0-9V), Ammeter (0-60A), Resistors ( $200\Omega$ ,  $100\Omega$ ,  $400\Omega$ ), connecting wires.

**THEORY:** Kirchoff's circuit Law (KCL):

In any electrical network, the algebraic sum of current meeting at a point (or junction) is zero.

→ Mathematically  $\sum I = 0$

Take Incoming current as +ve

Outgoing current as -ve

$$I_1 - I_2 - I_3 - I_4 + I_5 = 0 \quad [\text{see fig. (1)}]$$

$$I_1 + I_5 = I_2 + I_3 + I_4$$

Incoming current = Outgoing current

Kirchoff's Voltage Law (KVL):

The algebraic sum of the products of current and resistances in each of the conductors in any closed path in a network plus the algebraic sum of emf's in that part is zero.

$$\rightarrow \sum I R + \sum \text{emf} = 0$$

$$\text{i.e. } E - I_1 R_4 - I_1 R_1 - I_1 R_2 - I_1 R_5 - I_1 R_3 = 0$$

[see fig (2)]

**SIGN CONVENTIONS :**

(a) Sign of Battery Emf

Teacher's Signature.....

## OBSERVATION TABLE:

For KCL :-

$E_1$	$I_1$ (mA)	$I_2$ (mA)	$I_3$ (mA)	Error $I_1 - (I_2 + I_3)$
3V	7	6	1	$7 - (6 + 1) = 0$ mA
6V	20	16	3	$20 - (16 + 3) = 1$ mA
9V	22	17	4	$22 - (17 + 4) = 1$ mA

For KVL :-


$E_1$	$V_1$	$V_2$	Error $E_1 - (V_1 + V_2)$
3V	2.14	0.86	$3 - (2.14 + 0.86) = 0$
6V	4.29	1.71	$6 - (4.29 + 1.71) = 0$
9V	6.43	2.57	$9 - (6.43 + 2.57) = 0$

## RESULT :


From the observations and calculations, KCL and KVL has been verified.

Rise in voltage should be given a +ve sign.

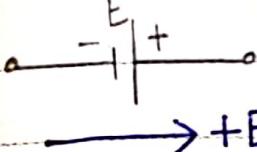Fall in voltage should be given a -ve sign.




Rise in voltage

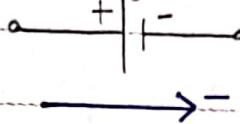


Fall in voltage

(b) Sign of IR drop

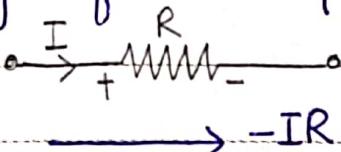

Fall in voltage

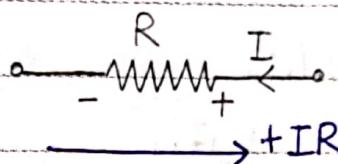

Rise in voltage

PROCEDURE : for KVL :-

1. Connect the circuit as shown in Fig. (3).
2. First, set the input voltage supply to 3V and then connect each of the three resistors ( $200\Omega$ ,  $100\Omega$  &  $400\Omega$ ) one by one in series with the ammeter on the kit.
3. Now, note the readings of ammeter with each of the resistors and name the current as  $I_1$ ,  $I_2$  and  $I_3$ .
4. Check that the readings of current should satisfy this equation  $I_1 = I_2 + I_3$  or  $I_1 - I_2 - I_3 = 0$
5. Repeat steps 2, 3, 4 with 6V and 9V as input voltage supply.
6. Switch off the supply.

For KCL :-

1. Connect the circuit as shown in Fig. (4). in the given kit.

Teacher's Signature.....

2. First, set the voltage supply to 3V and connect each of the three resistors ( $200\Omega$ ,  $100\Omega$  and  $400\Omega$ ) one by one in parallel with voltmeter on the kit.
3. Now, note the readings of voltmeter with each of the resistors and name the obtained value of voltage as  $V_1$ ,  $V_2$  respectively.
4. Find the error, if any, by the equation-  
$$E = (V_1 + V_2)$$
5. Now, repeat the steps 2, 3 & 4 with 6V and 9V as input voltage supply.
6. Switch off the supply.

#### PRECAUTIONS :

1. Check the zero settings of instruments before their use.
2. All connections should be tight.
3. Direction of current should be kept in mind.

RESULT : From the observations and calculations, both the KVL and KCL has been verified.


Teacher's Signature.....

# EXPERIMENT NO. 2


AIM: To verify Superposition Principle theorem.

APPARATUS REQUIRED: DC supply (0-9V), voltmeter (0-9V), wires, Ammeter (0-60A), Resistors  $200\Omega$ ,  $100\Omega$ ,  $400\Omega$ .

CIRCUIT DIAGRAM:

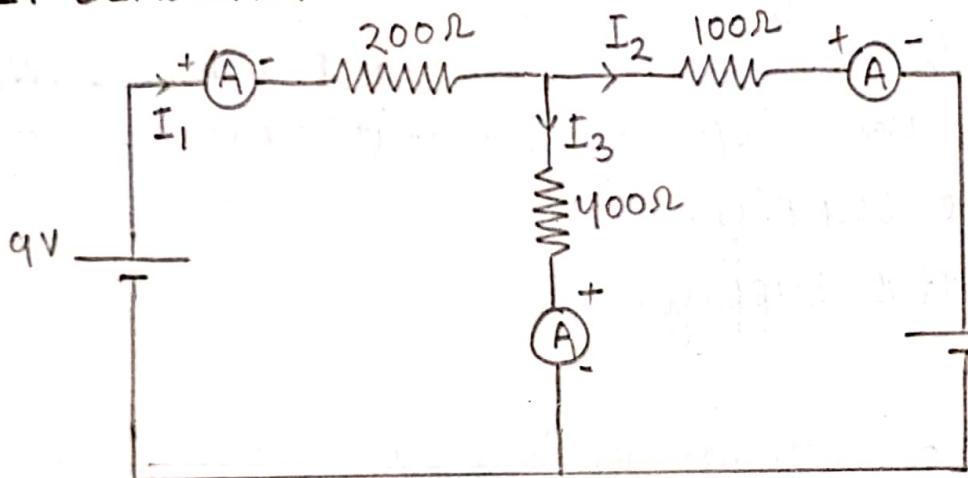

Step - I

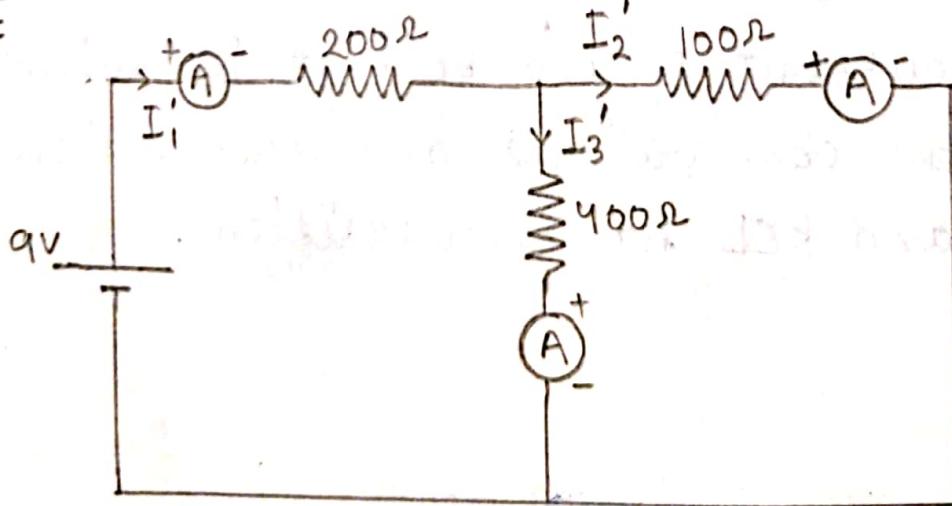

## EXPERIMENT NO. 2

AIM: To verify Superposition Principle or theorem

APPARATUS REQUIRED: DC supply (0-9V), voltmeter (0-9V), wires, Ammeter (0-60A), Resistors  $200\Omega$ ,  $100\Omega$ ,  $400\Omega$ ,


THEORY: According to this theorem, if there are two or more than two sources of emf's acting simultaneously in a linear bilateral network, the current flowing through any section is the algebraic sum of all the currents which should flow in that section if each source of emf were considered separately and all other sources are replaced by their initial resistance.

### PROCEDURE:

1. Connect the circuit as shown in Fig. (1).
2. Now find the current through each resistor by connecting them one by one with the ammeter. From this, you will get values of  $I_1$ ,  $I_2$  and  $I_3$ .
3. For verifying superposition theorem, the first step we have to follow is to cut off 5V battery.
4. Then after short-circuiting 5V battery, find out the currents in the three resistors shown in Fig. (2), by connecting ammeter one by one with the three resistors.
5. Name these currents  $I_1'$ ,  $I_2'$ ,  $I_3'$ . Now repeat these steps by short-circuiting 9V battery and this will give values of  $I_1''$ ,  $I_2''$  and  $I_3''$ .

Teacher's Signature.....

## Step-II

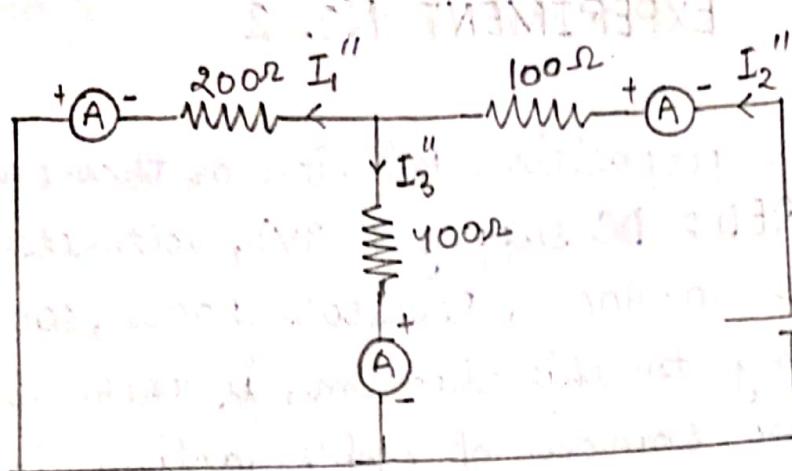

OBSERVATION TABLE :

Supply voltage	Current to mA			Error (mA)
9V	$I_1 = 20$	$I_1' = 32$	$I_1'' = 13$	$I_1 - (I_1' - I_1'') = 1$
	$I_2 = 7$	$I_2' = 26$	$I_2'' = 19$	$I_2 - (I_2' - I_2'') = 0$
5V	$I_3 = 13$	$I_3' = 7$	$I_3'' = 6$	$I_3 - (I_3' - I_3'') = 0$

## RESULT :

From the above calculations and observations, the superposition theorem is verified.

6. Now here,  $I_1$  must be equal to  $I_1' + I_1''$  and same with  $I_2$  and  $I_3$  and if not this then there must be some error in your calculation or circuit.

#### PRECAUTIONS:

1. Direction of current should be correctly identified.
2. Check zero setting of instruments before connection, rheostat terminals.
3. Connections should be tight.
4. Ratings of currents to be kept in mind.


RESULT: From the observations and calculations, superposition theorem has been verified.

# EXPERIMENT → 3


AIM: To verify Thvenin's theorem.

APPARATUS: DC supply, voltmeter, ammeter, Resistor ( $500\Omega$ ,  $100\Omega$ ,  $90\Omega$ )


CIRCUIT DIAGRAM:

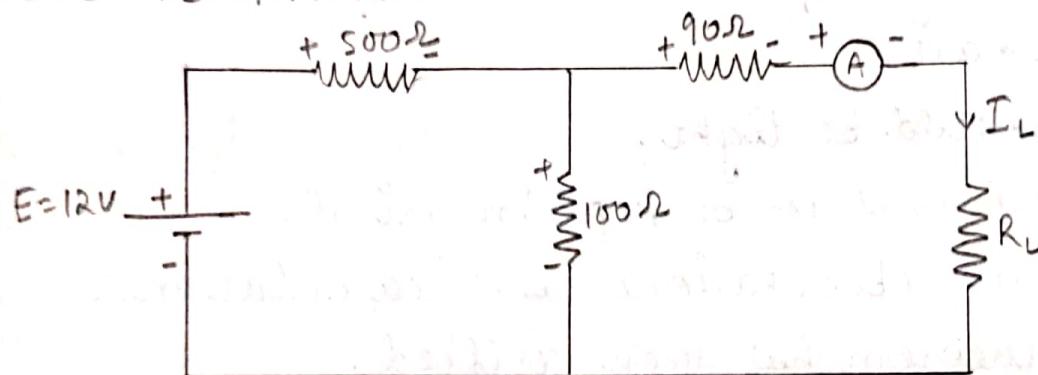

Step - I :-

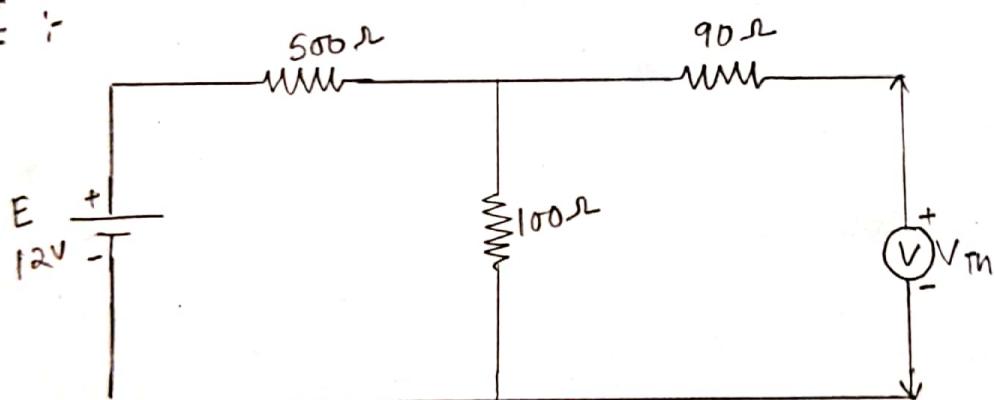

Step - II :-

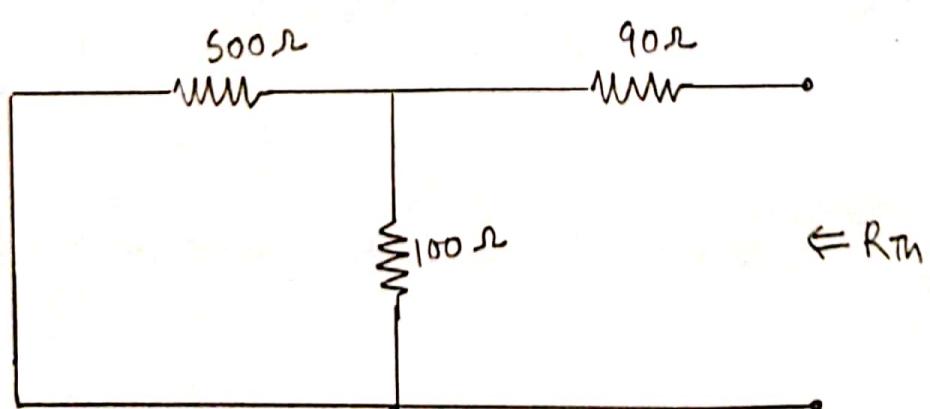

$$R_{Th} = 173.33\Omega$$

# EXPERIMENT NO. 3

AIM: To verify Thvenin's theorem.

APPARATUS REQUIRED: DC supply, voltmeter, Ammeter, resistor (500Ω, 100Ω, 90Ω)

THEORY: The current flowing through a load resistance  $R_L$  connected across any two terminals A and B of a linear active bilateral network is given by  $V_{oc}/(R_{Th} + R_L)$ , where,  $V_{oc}$  is open circuit voltage.


i.e. voltage across the two terminals when  $R_L$  is removed.  
 $R_{Th}$  is the internal resistance of network as viewed back into the open circuit network from terminals A and B with all voltage sources replaced by their internal resistance and current source by open circuit.

## PROCEDURE:

1. Make the connections on the kit as shown in figure & switch on DC supply. This will give load current across different load resistance connected by ammeter.
2. Now make the connections according to second figure i.e. open circuit load terminal and give 12V supply. This will give us open circuit voltage i.e.  $V_{Th}$ .
3. Make the calculation as shown in figure 3 and calculate  $R_{Th}$ .
4. Now we have  $V_{Th}$  and  $R_L$ , so with these values we can calculate  $I_L$ . ( $I_L = \frac{V_{oc}}{R_{Th} + R_L}$ )

Teacher's Signature.....

Step-III :-

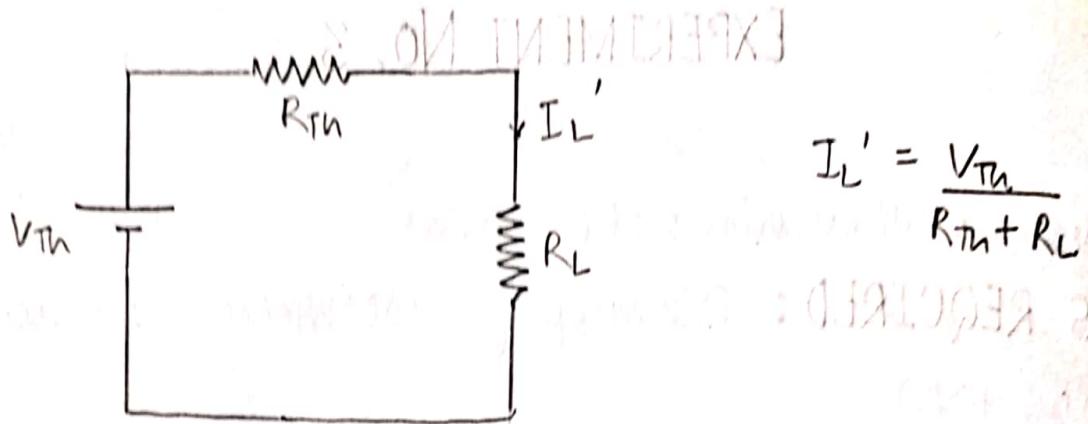

OBSERVATION TABLE :-

E(V)	R <sub>L</sub> (Ω)	I <sub>L</sub> (mA)	V <sub>Th</sub> (v)	R <sub>Th</sub> (Ω)	I <sub>L'</sub> (mA)	Error (I <sub>L</sub> - I <sub>L'</sub> )
12	25	8	1.75	173.33	3.8	0.8 mA
12	50	7	1.75	173.33	7.8	0.8 mA
12	100	5.5	1.75	173.33	6.4	0.9 mA

RESULT:-

From the above calculations and observations, Thévenin's theorem is verified.

### **PRECAUTIONS:**

1. Meters should be used within proper range.
2. We must use neat and tight connections.
3. Zero setting of all meters should be checked before giving input supply.

### **RESULT:**


From the above observations and calculations, thvenin's theorem is satisfied/verified.

# EXPERIMENT → 4


**AIM :** To verify Norton's theorem.

**APPARATUS :** AC supply, voltmeter, ammeter, Resistance ( $500\Omega$ ,  $90\Omega$  &  $100\Omega$ ).


**CIRCUIT DIAGRAM :**

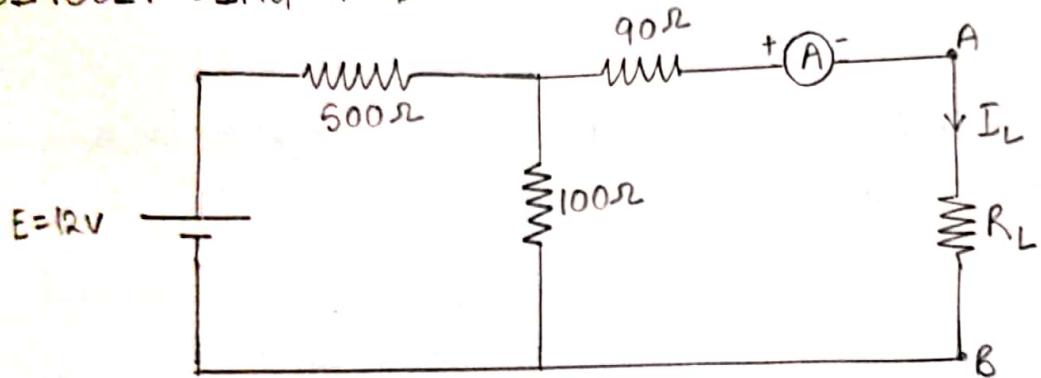

**Step - I :-**

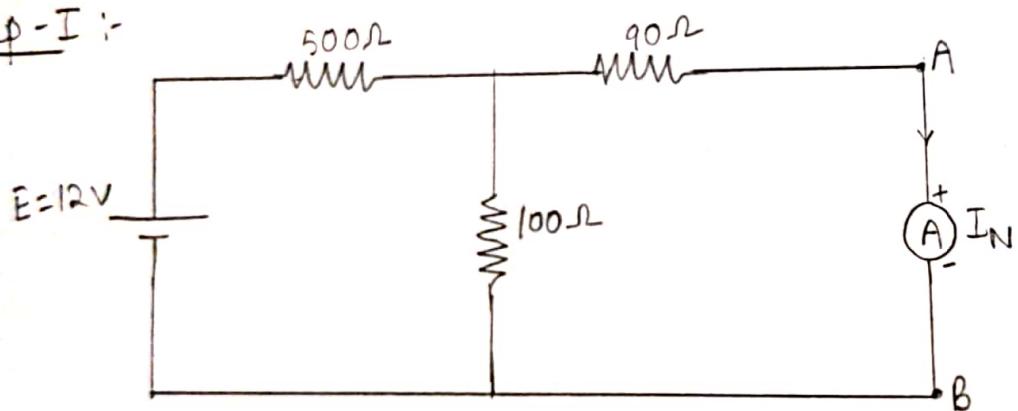

**Step - II :-**

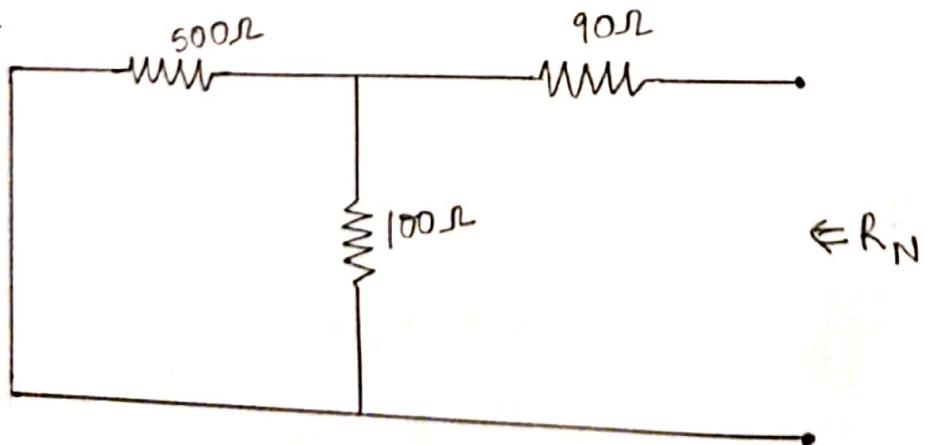

## EXPERIMENT NO.4

AIM: To verify Norton's theorem

APPARATUS: DC supply, voltmeter, ammeter, Resistance ( $50\Omega$ ,  $100\Omega$ ,  $90\Omega$ )

THEORY: The current flowing through a resistance connected across any two terminals of a network can be determined by replacing the whole networking by an equivalent circuit of a current source having a current output of  $I_N$  in parallel with resistance  $R_N$ , where  $I_N$  = short circuit current supplied by the source that would flow between the two selected terminals when they are short circuited.

$R_V$  = equivalent resistance of the networks as seen from the two terminals with all other emf sources replaced by their internal resistance and current source replaced by open circuit.


### PROCEDURE:

1. Make the connections as shown in the circuit diagram and measure the value of current ' $I_L$ ' across ' $R_L$ ' with the help of ammeter at DC supply of 12V.
2. Now, by removing load resistance ' $R_L$ ', short the circuit across terminals AB in diagram (1) and measure the value of short circuit current ' $I_N$ ' with the help of ammeter.
3. Calculate the equivalent resistance ' $R_N$ ' from the diagram (2).

Teacher's Signature.....

# EXPERIMENT NO. 11

Step - III :-

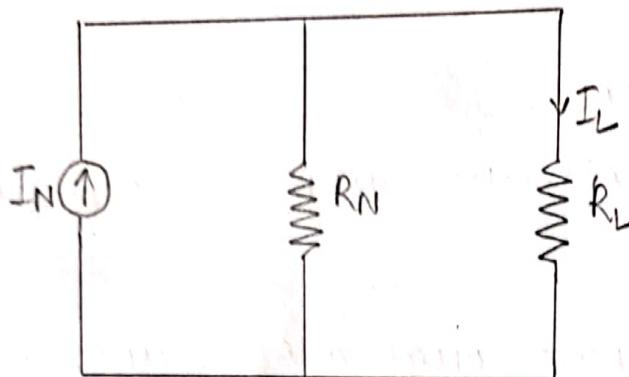

$$I'_L = \frac{R_N}{R_N + R_L} \times I_N$$

OBSERVATION TABLE :

E	R <sub>L</sub>	I <sub>L</sub>	I <sub>N</sub>	R <sub>N</sub>	I' <sub>L</sub>	Error (I <sub>L</sub> - I' <sub>L</sub> )
12V	25Ω	8mA	10mA	173.33Ω	8.7mA	0.7mA
12V	50Ω	7mA	10mA	173.33Ω	7.7mA	0.7mA
12V	100Ω	5.5mA	10mA	173.33Ω	6.3mA	0.9mA

## RESULT:

From the above observations and calculations, Norton theorem has been verified.

4. Hence, find the value of current 'I<sub>L</sub>' by using formula:

$$I_L = \frac{R_N}{R_N + R_L} \times I_N$$

#### PRECAUTIONS:

1. All the connections should be correct & tight.
2. Zero setting of all meters should be checked before giving the input supply.
3. Readings should be noted carefully.

#### RESULT:

From the above observations and calculations, Norton's theorem has been verified.