

BT-1/D-18

31044

BASIC ELECTRICAL ENGINEERING

Paper : ES-101(A)

Opt. (I)

Time : Three Hours]

[Maximum Marks : 75

Note : Attempt five questions selecting at least *one* question from each unit.

UNIT-I

1. (a) Using Mesh analysis, determine the current in the $4\ \Omega$ -branch in the circuit shown in Fig. 1. 8

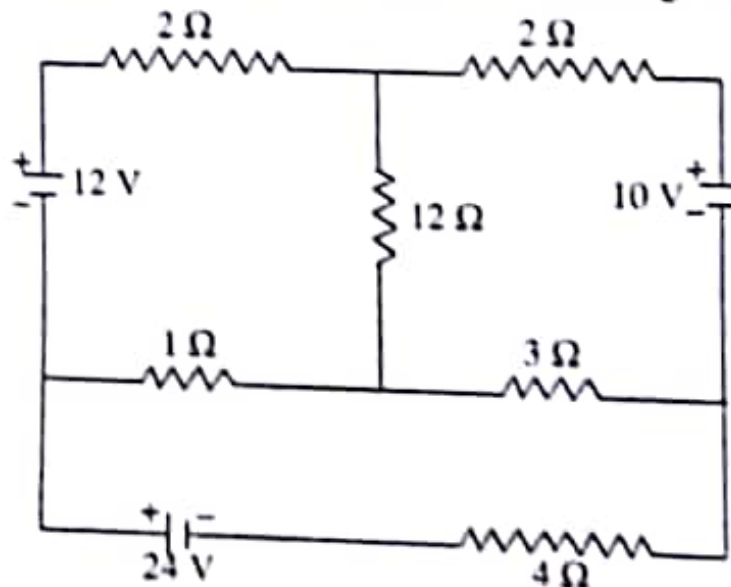


Fig. 1.

- (b) For the circuit shown in Fig. 2, find out the value of R for maximum power transfer, and also find out the maximum value of power. 7

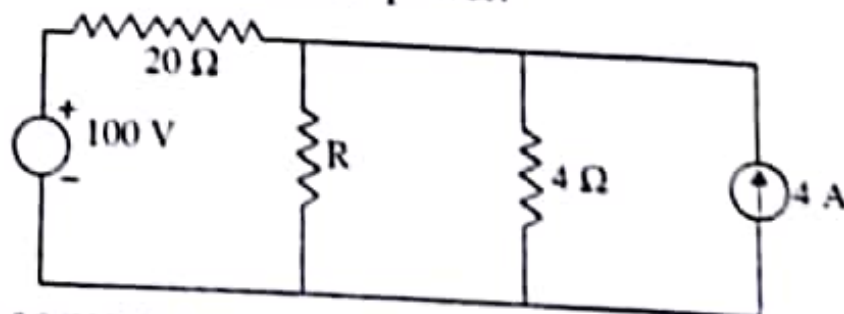


Fig. 2.

31044/1,100/KD/1673

[P.T.O.
22/12

- 2 (a) Using Node voltage method, find V_s for $I_o = 7.5 \text{ mA}$ as shown in Fig. 3. 8

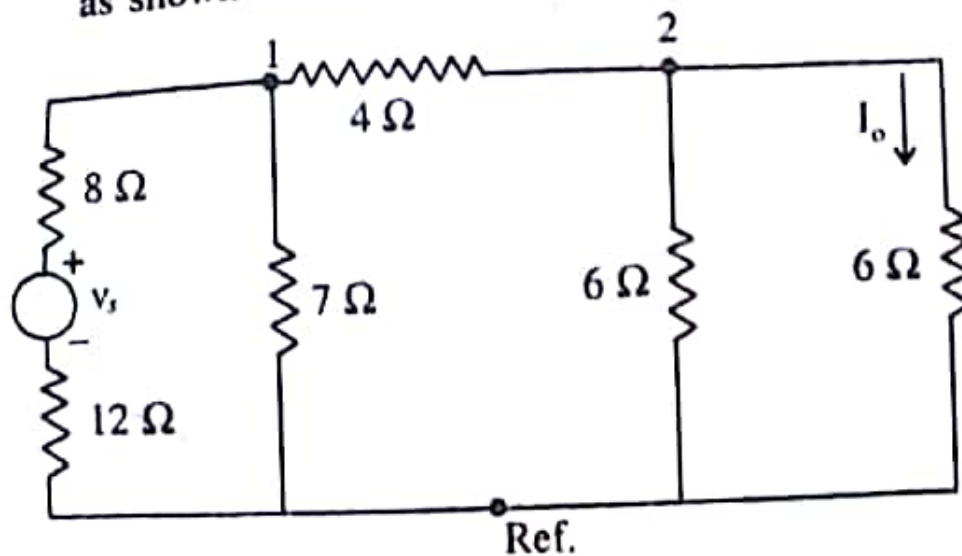


Fig. 3.

- (b) Calculate the current through 2Ω in the circuit shown in Fig. 4 using Superposition theorem. 7

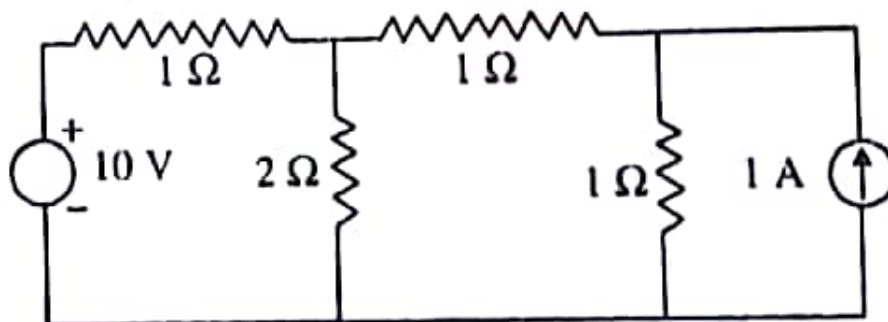


Fig. 4.

UNIT-II

3. (a) Calculate the r.m.s. and average value for the waveform shown in Fig. 5. (4+4)

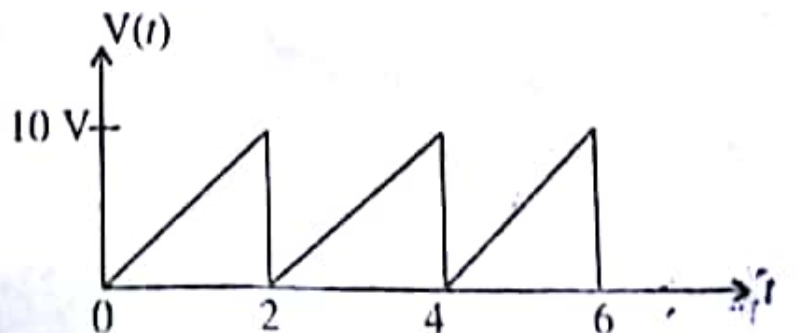


Fig. 5.

(b) Find selectivity, Q factor, half power frequencies and bandwidth for Parallel RLC resonance circuit. 7

4. (a) Find the sum of sine current given as follows : 8

$$i_1 = 12 \sin (\omega t + 30^\circ); i_2 = 20 \sin (\omega t + 60^\circ),$$

$$i_3 = 18 \sin \omega t; i_4 = 25 \cos (\omega t); i_5 = 10 \cos \left(\omega t + \frac{2\pi}{3} \right).$$

(b) Draw and explain resonance and bandwidth curve for series RLC resonance circuit. 7

UNIT-III

5. (a) Describe Three-phase delta connection with diagrams. 8

(b) Explain OC and SC tests in detail. 7

6. (a) Describe the measurement of 3-phase power by 2-wattmeter method for star connection. 8

(b) Write a note on the losses and efficiency of a single phase transformer. 7

UNIT-IV

7. (a) Explain the construction and working of dc machines with commutator action. 8

(b) Describe the various types of wires and cables. 7

- 8. (a) Explain the construction and working principle of synchronous generator and motor. 8**
- (b) Differentiate between MCB, ELCB and MCCB. 7**
-