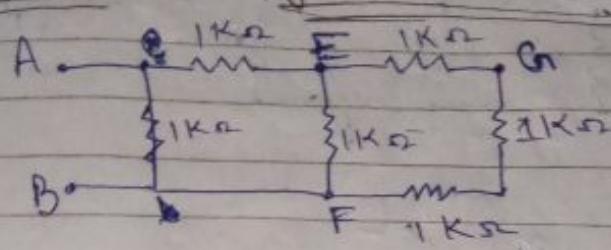


Anmol Baranwal -- 28/20208

# BEE Assignment No. 1

Ans.




(i)  $R_{AB} = ?$

$$R_{EF} \Rightarrow 3 \times 1 \text{ K}\Omega$$

$$R_{AB} \Rightarrow \frac{1 \times \left( \frac{3+1}{4} \right)}{1 + \left( \frac{3+1}{4} \right)} \Rightarrow \frac{7}{11} \text{ K}\Omega$$

(ii)  ~~$R_{EC} = ?$~~   $R_{CD} = ?$

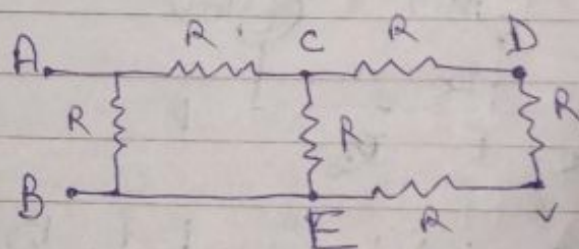

( $R = 1 \text{ K}\Omega$ )

$R_{CE} \Rightarrow$   
calculating effective resistance  
b/w terminals C and E


$$R_{CE} \Rightarrow \frac{2}{3} \text{ K}\Omega$$

now effective resistance b/w C and D


$$R_{CD} \Rightarrow \frac{1 \times \left( \frac{2+2}{3} \right)}{1 + \left( \frac{2+2}{3} \right)} \Rightarrow \frac{8}{11} \text{ K}\Omega$$

2820208

(iii)

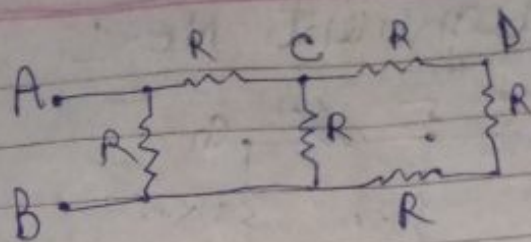


$(R = 1 \text{ k}\Omega)$

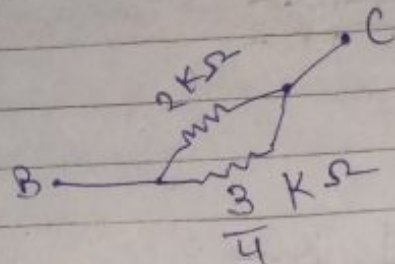

$$R_{BC} \Rightarrow \frac{2 \times \frac{3}{4}}{2 + \frac{3}{4}} \Rightarrow \frac{6}{11} \text{ k}\Omega$$

Ans 2.

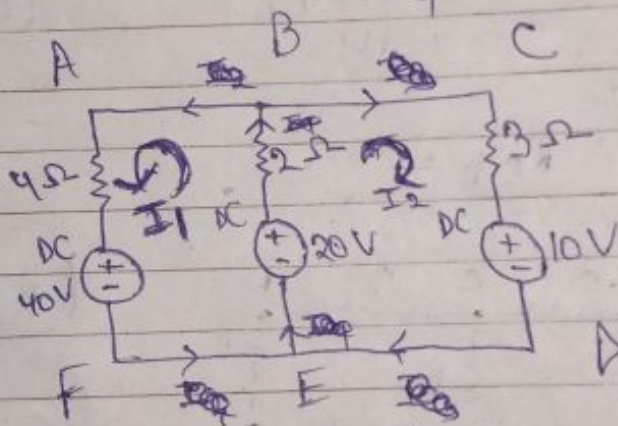

applying KVL in F E B A F

~~$$-20 + 2I_1 + 4I_2 + 40 = 0$$~~

~~$$I_1 + 2I_2 + 10 = 0$$~~

applying

$$-20 + 2(I_1 + I_2) + 4I_1 + 40 = 0$$

$$6I_1 + 2I_2 = -20$$



2820208

$$3I_1 + I_2 = -10 \quad \text{--- (1)}$$

applying KVL in  $\Delta EBCD$

$$-20 + 2(I_1 + I_2) + 3I_2 + 10 = 0$$

$$2I_1 + 5I_2 = 10 \quad \text{--- (2)}$$

solving (1) and (2)

$$13I_2 - 2I_2 = 30 + 20$$

$$13I_2 = 50$$

$$I_2 \Rightarrow \frac{50}{13} \text{ A}$$


$$I_1 = \left( \frac{-10 - \frac{50}{13}}{3} \right) \times 1$$

$$\Rightarrow -\frac{60}{13} \text{ A}$$

$\therefore$  current in  $2\Omega$


$$I_1 + I_2 \Rightarrow -\frac{10}{13} \text{ A}$$

Ans 3. delta to star  $\Rightarrow$

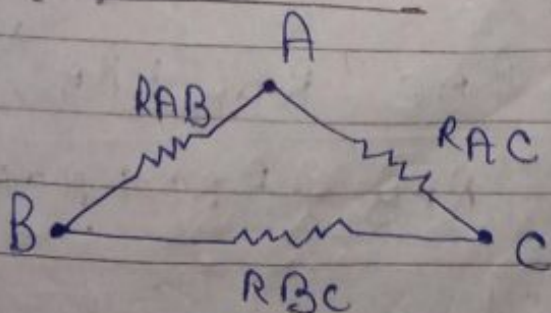

$\rightarrow$  Delta

2820208

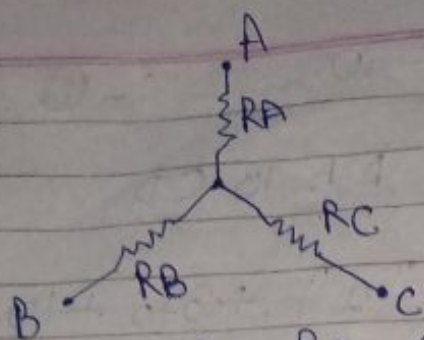

→ stars

are  
here  $R_A, R_B, R_C$  are in terms of  
 $R_{AB}, R_{BC}, R_{CA}$

Equivalent resistance b/w terminal  
A and B for delta connection

$$\frac{1}{R} = \frac{1}{R_{AB}} + \frac{1}{R_{BC} + R_{AC}}$$

$$R \Rightarrow \frac{R_{AB} \cdot (R_{BC} + R_{AC})}{R_{AB} + R_{BC} + R_{AC}}$$

Resistance b/w terminal A and B  
for star connection  $\Rightarrow R_A + R_B$

$$R_A + R_B = \frac{R_{AB} (R_{BC} + R_{AC})}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (1)}$$

$$\text{similarly, } R_B + R_C = \frac{R_{BC} (R_{AB} + R_{CA})}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (2)}$$

$$R_A + R_C = \frac{R_{AC} (R_{AB} + R_{BC})}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (3)}$$

$$\textcircled{3} - \textcircled{2} + \textcircled{1}$$

$$2R_A = \frac{-R_{BC} \cdot R_{AB} + R_{AC} \cdot R_{AB} + R_{BC} \cdot R_{AB} + R_{AC} \cdot R_{AB}}{R_{AB} + R_{BC} + R_{CA}}$$

Ans



2820208

$$\therefore R_A = \frac{R_{AB} \cdot R_{CA}}{R_{AB} + R_{BC} + R_{CA}}$$


similarly,

$$R_B = \frac{R_{AB} \cdot R_{BC}}{R_{AB} + R_{BC} + R_{CA}}$$


$$R_C = \frac{R_{BC} \cdot R_{CA}}{R_{AB} + R_{BC} + R_{CA}}$$

$$R_A = R_B = R_C \Rightarrow R/3$$

Ans 4.  $R_{AB} \Rightarrow ?$

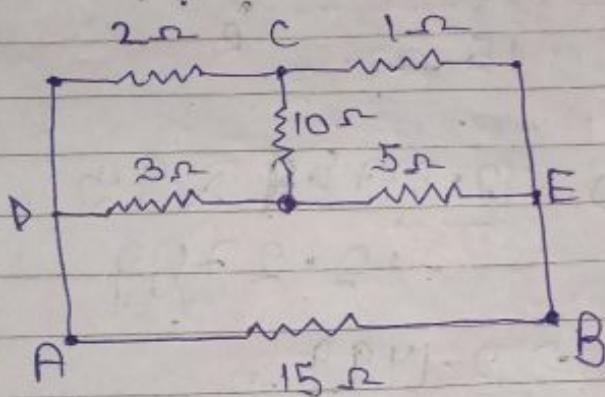

converting ~~delta~~ star CDE to delta

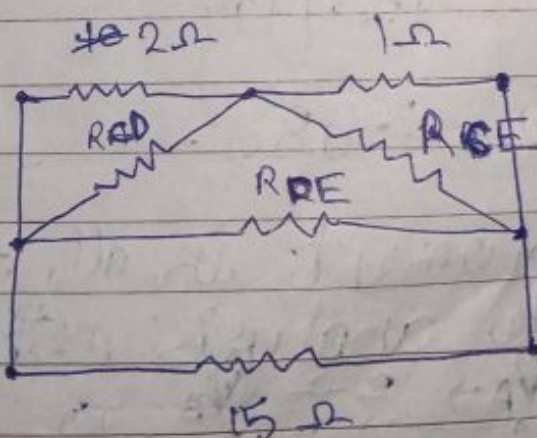

$$R_{CE} \Rightarrow \frac{10 + 5 + \frac{10 \times 5}{3}}{3} \Rightarrow \frac{95}{3} \Omega$$


$$R_{DE} \Rightarrow \frac{3 + 5 + \frac{15 \times 3}{10}}{2} \Rightarrow \frac{19}{2} \Omega$$

$$R_{CD} \Rightarrow \frac{10 + 3 + \frac{10 \times 3}{5}}{2} \Rightarrow 19 \Omega$$


28/20208

$$\Rightarrow 2.7789$$

$$\frac{95 \times 1}{3} = \frac{95}{3}$$

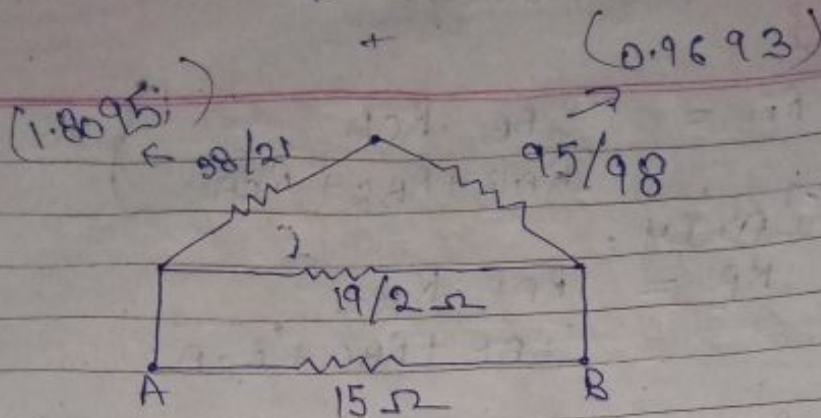

$$\frac{19 \times 2}{21}$$

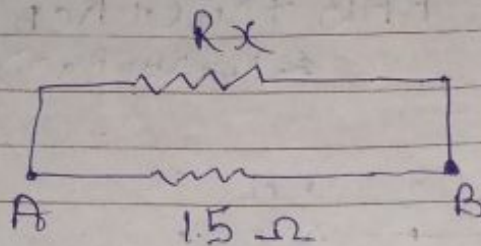


9.5

$$R_x \Rightarrow \frac{2.7789 \times 9.5}{12.2789} \Rightarrow 2.1499 \Omega$$

$$R_{AB} \Rightarrow \frac{15 \times 2.1499}{17.1499} \Rightarrow 1.880 \Omega$$

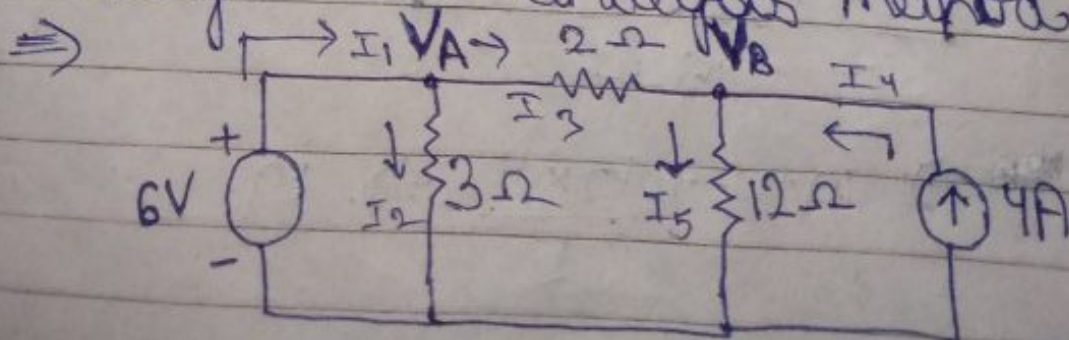Ans 5. Calculate current in all resistances using node analysis method





2020208

using KCL around  $V_A$   
 ~~$I_1 = I_2 + I_3$~~   $V_A = 6V$

~~$6 = V_A$~~

using KCL around  $V_B$   
 $I_3 + I_4 = I_5$

$$\frac{6 - V_B}{2} + 4 = \frac{V_B}{12}$$

$$6(6 - V_B) + 48 = V_B$$


$$36 + 48 = 7V_B$$

$$V_B \Rightarrow \frac{84}{7} \Rightarrow 12V$$

$$I_2 \Rightarrow 2A$$

$$I_3 \Rightarrow -3A, I_5 \Rightarrow 1A$$

2820208

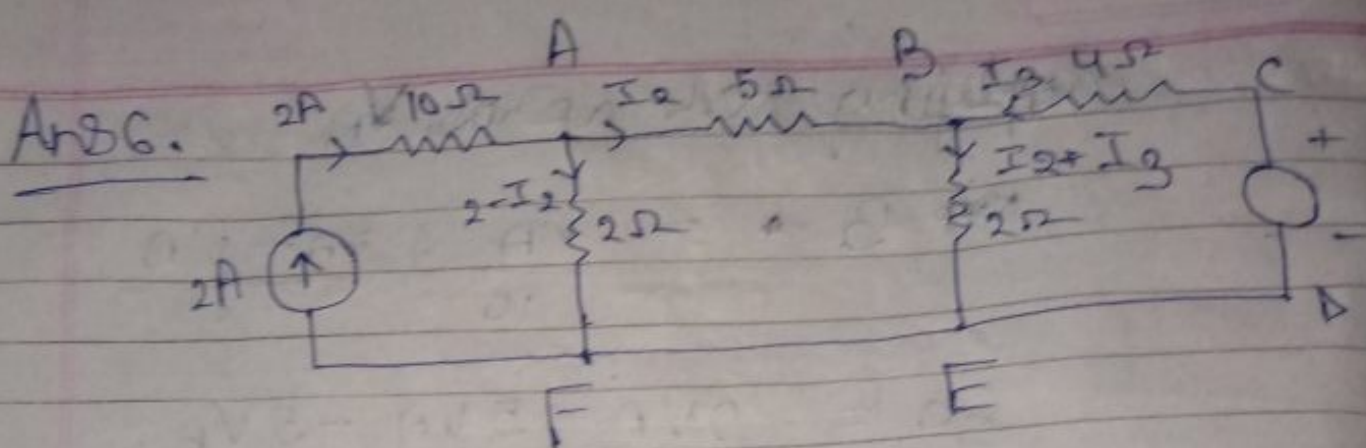

In mesh BCDEB

$$2(I_2 + I_3) + 4I_3 - 100 = 0$$

$$2I_2 + 6I_3 = 100$$

$$I_2 + 3I_3 = 50 \quad \text{--- (1)}$$

In mesh ABEFA

$$2(2 - I_2) - 5I_2 - 2(I_2 + I_3) = 0$$

~~$$2I_2 + 6I_3 = 4$$~~

$$9I_2 + 2I_3 = 4 \quad \text{--- (2)}$$

Solving (1) and (2)

$$\textcircled{1} \times 2 - 3 \times \textcircled{2}$$


$$-25I_2 = 88$$

$$I_2 = \frac{-88}{25} \text{ A}$$




28/20208

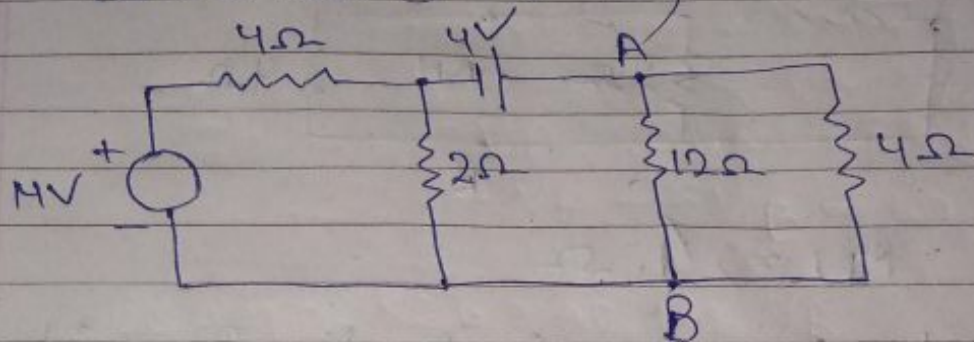Ans 7. voltage drop across  $12\Omega$  using Norton's theorem  $\Rightarrow$



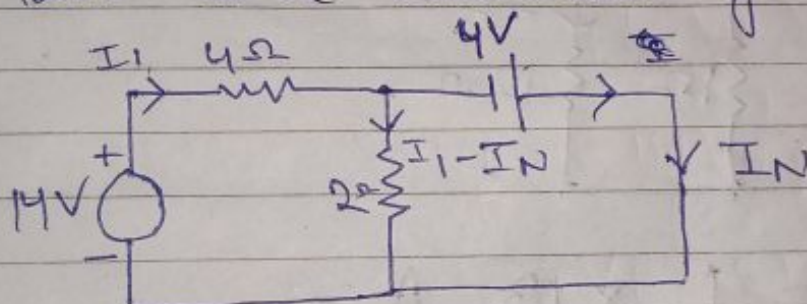1. short-circuit terminals across  $12\Omega$  and calculating  $I_N$ .



applying KVL

$$4I_1 + 2(I_1 - I_N) - 14 = 0$$

$$2(I_1 - I_N) + 4 = 0$$


$$I_N - I_1 = 2$$

$$6I_1 - 2I_N = 14$$

$$I_N = \frac{13}{2} \text{ A}$$


28/20/2018

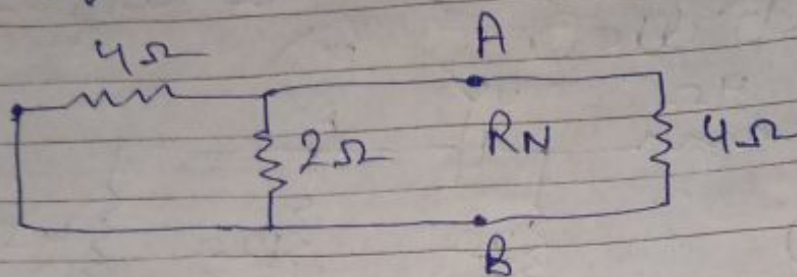2. effective resistance across  $12\Omega$



$$R_N \Rightarrow 1\Omega$$

3. Norton's equivalent circuit

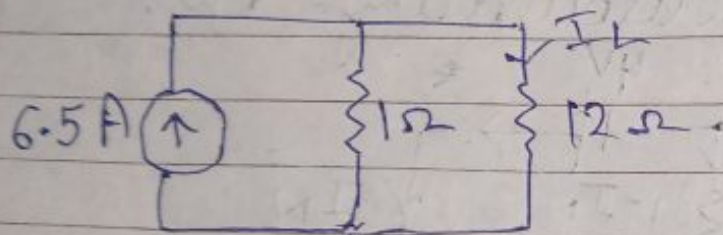

$$I_L = \frac{1}{12} \times \frac{13}{2} A$$

$$V_{AB} \Rightarrow \frac{13}{2} \times 12 \times \frac{1}{12} \Rightarrow \underline{\underline{6.5 V}}$$



2820208


voltage drop across  $12\Omega$

$$\Rightarrow I_L \times 12\Omega$$


$$\Rightarrow \left( \frac{1}{1+12} \times \frac{9}{2} \right) \times 12$$

$$\Rightarrow \frac{4.5 \times 12}{13} \Rightarrow \frac{54}{13} \checkmark$$

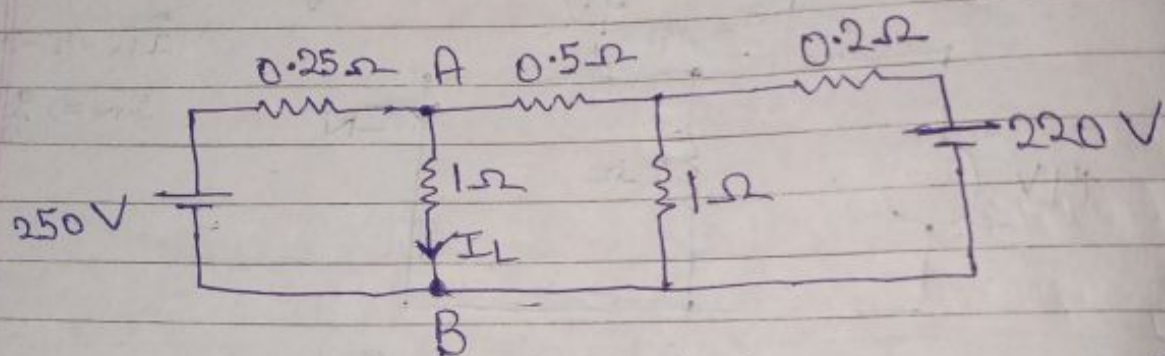Ans B. Find  $I_L$  using Thevenin's theorem  $\Rightarrow$



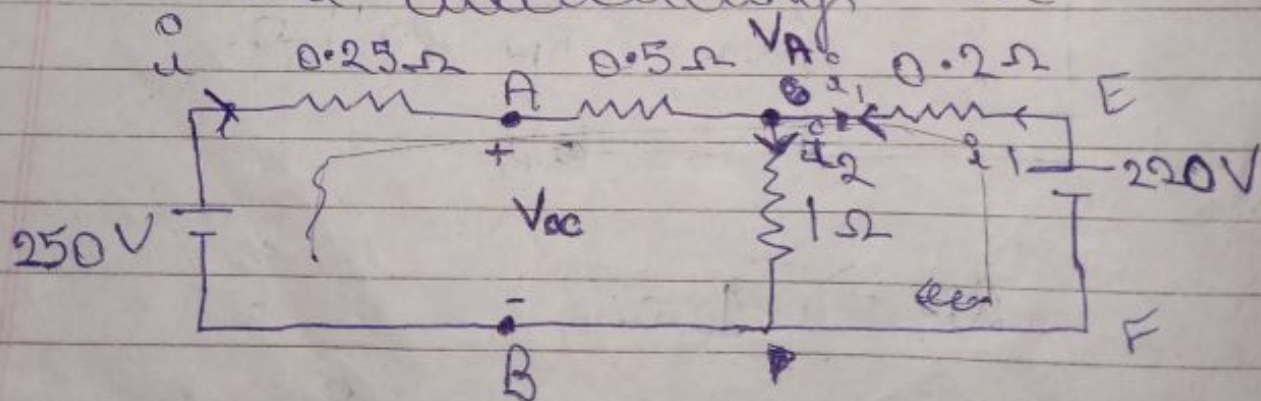1. remove a resistance ( $R_L$ ) from circuit and calculating  $V_{oc}$ .



applying KVL across big loop

$$-250 + V_{oc} + 0.95i_1 + 220 = 0$$

2820208

$$V_{oc} + 0.95i = 30$$

using nodal analysis



applying  $\frac{250 - V_A}{0.25} + \frac{220 - V_A}{0.2} = \frac{V_A}{1}$

on solving  $V_A \Rightarrow \frac{215}{1.1} V$

$$V_{oc} \Rightarrow \left( \frac{250 - \frac{215}{1.1}}{0.25} \right) \times 0.25$$

$$\Rightarrow \frac{60}{1.1 \times 3} \Rightarrow \frac{20}{1.1} V$$

2. calculate Req across RL

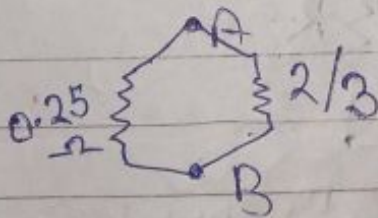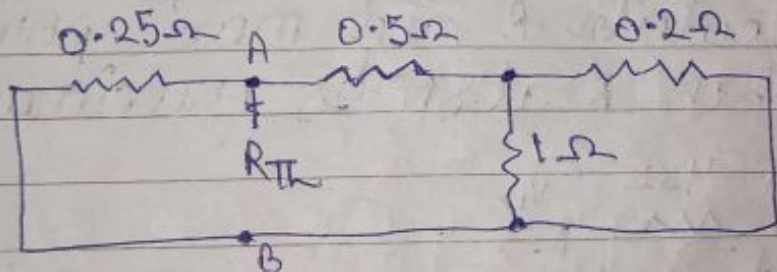


$$\Rightarrow \frac{0.25 + 0.5}{1.5} = \frac{1}{6} + \frac{1}{2}$$

$$R_{TH} \Rightarrow \frac{\frac{1}{4} \times \frac{2}{3}}{\frac{1}{4} + \frac{2}{3}} \Rightarrow \frac{2}{11} \Omega$$



2820208

Theremin's equivalent circuit

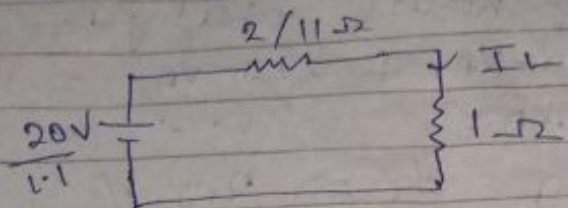


$$I_L \Rightarrow \frac{(20/1.1)}{\left(\frac{2}{11} + 1\right)}$$

$$\Rightarrow \frac{200}{11} \times \frac{11}{13}$$

$$\Rightarrow \frac{200}{13} \text{ A}$$

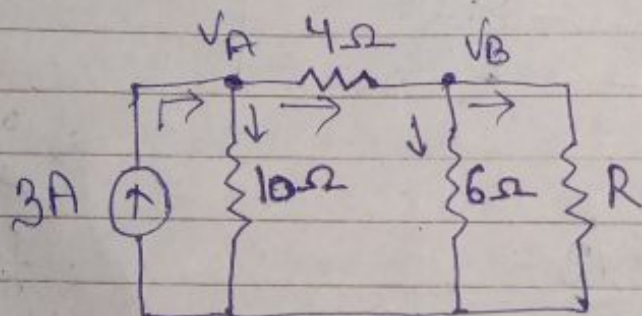Ans 9. Calculate R and max<sup>m</sup> power when R absorbs maximum power.



$\therefore$  R absorbs max<sup>m</sup> power

$\therefore$  R is equivalent to

$$\Rightarrow \frac{7/4 \times 6}{24/5} \Rightarrow \frac{21}{5} \Omega$$

Here current source is taken 3A  
so resultant  $\times 100$  will be ans

2820208

applying KCL across  $V_A$

$$3 \rightarrow = \frac{V_A}{10} + \frac{V_A - V_B}{4}$$

$$60 = 2V_A + 5V_A - 5V_B$$

$$7V_A - 5V_B = 60 \quad (1)$$

applying KCL across  $V_B$

$$\frac{V_A - V_B}{4} = \frac{V_B}{6} + \frac{V_B \times 5}{21}$$

$$21(V_A - V_B) = 14(V_B) + 4V_B \times 5$$

$$21V_A - 21V_B = 14V_B + 20V_B$$

$$21V_A - 55V_B = 0 \quad (2)$$

solving (1) and (2)

$$77V_A - 21V_A = 60 \times 11$$

$$56V_A = 11 \times 60$$

$$14V_A = 15 \times 11 \text{ V}$$

$$V_B \Rightarrow \frac{21}{55} \times \frac{15 \times 11}{14} \Rightarrow \frac{9}{2} \text{ V}$$

$$\therefore P_{\max} \Rightarrow \left( \frac{9}{2} \right)^2 \Rightarrow \frac{9 \times 9 \times 5}{4 \times 21}$$

$$\left( \frac{21}{5} \right) \Rightarrow \frac{135}{28} \text{ W}$$