


BEE Assignment No. 2

[ Riaz Ahmed Basarwala - 28202008 ]

Ans 3.  $\dot{I}_1 = 15 \sin(\omega t + \pi/3)$   
 $\dot{I}_2 = 5 \sin(\omega t - \pi/3)$

Find  $\dot{I}_1 - \dot{I}_2$ :

$15 \sin 60^\circ + 5 \sin 60^\circ$

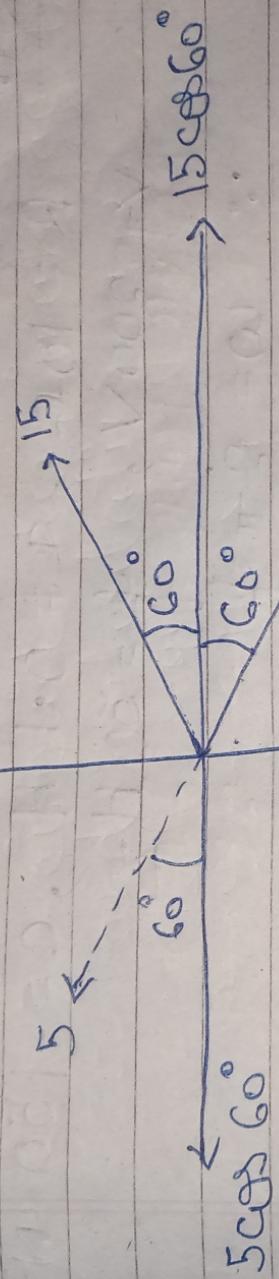

$\dot{I}_1 - \dot{I}_2 \Rightarrow \dot{I}_1 + (-\dot{I}_2)$

x-component  $\Rightarrow 15 \cos 60^\circ - 5 \cos 60^\circ$

$\Rightarrow 5$

y-component  $\Rightarrow 20 \times \frac{\sqrt{3}}{2} \Rightarrow 10\sqrt{3}$

$(15 \sin 60^\circ + 5 \sin 60^\circ)$

$$\text{Im} = \sqrt{x^2 + y^2} = \sqrt{25 + 300} = \sqrt{325} = 18.02 \text{ A}$$

Diagram showing phasor representation:

$$\phi = \tan^{-1} \left( \frac{Y}{Z} \right) \Rightarrow \tan^{-1}(2\sqrt{3})$$

$i$

$$I_s = 18.02 \sin(\omega t + 73.9^\circ)$$

~~(+90^\circ)~~

Ans 4.

$R = 10\Omega$ ,  $L = 0.1 H$ ,  $C = 150 \mu F$

$V = 200V$ ,  $f = 50 Hz$

$\therefore \omega = 2\pi f$   
 $\Rightarrow 100\pi \text{ Hz}$

$$X_L = \omega L \Rightarrow 100\pi \times 0.1 \Omega$$

$$\Rightarrow 10\pi \Omega$$

$$\Rightarrow 31.4 \Omega$$

$A_s = 1 \Rightarrow$

$$x_c = \frac{1}{\omega c} \Rightarrow \frac{10^6}{100\pi \times 150} \Rightarrow 21.2 \Omega$$

(i) Impedance,

$$Z = \sqrt{R^2 + (x_L - x_C)^2}$$

$$= \sqrt{(10)^2 + (31.4 - 21.2)^2}$$

$$\Rightarrow \text{impedance } 14.28 \Omega$$

(ii) current  $\Rightarrow$  ~~200~~  $\frac{V}{2}$

$$\Rightarrow \frac{200}{14.28} \Rightarrow 14 \text{ A}$$

(iii) Power factor

$$\Rightarrow \frac{R}{Z} \Rightarrow \frac{10}{14.28} \Rightarrow 0.7$$

(iv) Impedance of coil  $\Rightarrow \sqrt{(10^2) + (31.4)^2}$

$$(Z_c) \Rightarrow 33 \Omega$$

Voltage drop across coil  
 $\Rightarrow I \times Z_c \Rightarrow 14 \times 33 \Rightarrow 462 \text{ V}$

(v) Voltage across condenser

$$\Rightarrow 14 \times 21.2 \Rightarrow 296.8 \text{ V}$$

Ans 5.  $z = 4 - 3j \Omega$

( $\because z = R - jX_C$ )

$\therefore R = 4 \Omega, X_C = 3 \Omega$

Active Power  $\rightarrow P$


$$i = 5 \cos(100\pi t + 100) A$$

$$I_m = 5 A$$

Active Power  $\Rightarrow I_m^2 R$

$$\Rightarrow 25 \times 4 \Rightarrow 100 W$$

Ans 7.

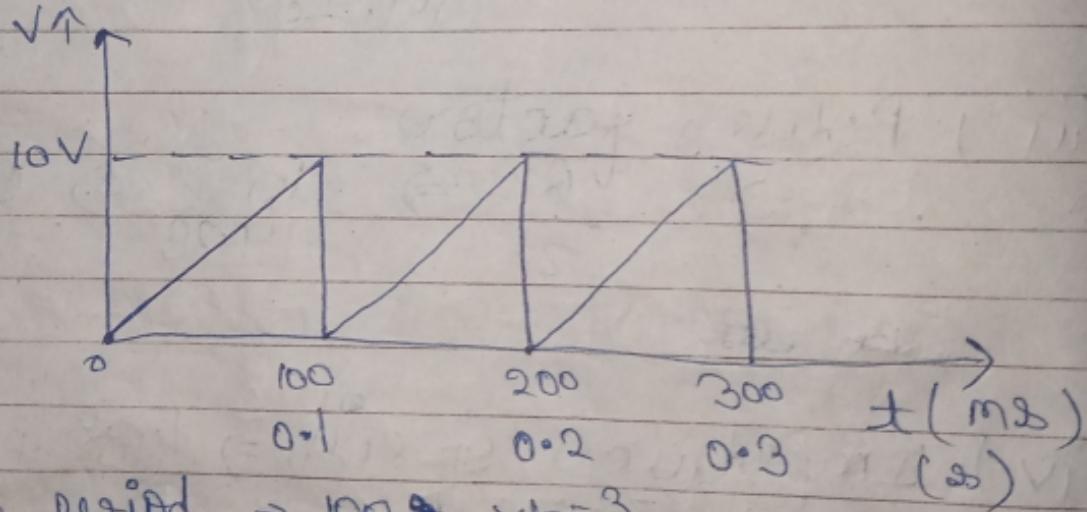

$$\text{Time period} \Rightarrow 100 \times 10^{-3} s \\ \Rightarrow 0.1 s$$

(i) frequency  $\Rightarrow \frac{1}{T} \Rightarrow 10 \text{ Hz}$

(ii) RMS value  $\Rightarrow$

from figure

$$v(t) = \frac{t}{10} \times \frac{10}{0.1} + 0$$

$$v(t) \Rightarrow 100t$$

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$= \sqrt{\frac{1}{0.1} \int_0^{0.1} 100^2 \times t^2 dt}$$

$$\Rightarrow \sqrt{\frac{10^5}{3} [t^3]_0^{0.1}}$$

$$\Rightarrow \sqrt{\frac{10^2}{3}} \Rightarrow \frac{10}{\sqrt{3}} V$$

$$V_{\text{avg}} = \frac{1}{T} \int_0^T v(t) dt$$

$$= \frac{1}{0.1} \int_0^{0.1} (100t) dt$$

$$\Rightarrow \frac{10^3}{2} [t^2]_0^{0.1}$$

$$\Rightarrow \frac{10}{2} \Rightarrow 5V$$

(iii) Form factors

$$\Rightarrow \frac{V_{\text{rms}}}{V_{\text{avg}}} \Rightarrow \frac{10}{5\sqrt{3}} \Rightarrow \frac{2}{1.732}$$

$$\Rightarrow 1.154$$

Ans 5.  $P_R = 500 \text{ W}$   
 $V_R = 100 \text{ V}$

Ans 6.  $P_{coil} = 100 \text{ W}$ ,  $V_{coil} = 50 \text{ V}$

$$\therefore P_R = \frac{(V_R)^2}{R}$$

$$R \Rightarrow \frac{100 \times 100}{500} \Rightarrow 20 \Omega$$

$$V_R = R I \\ 100 = 20 \times I \Rightarrow I = 5 \text{ A}$$

$$P_{coil} = I^2 R_c$$

$$R_c = \frac{100}{25} \Rightarrow 4 \Omega$$

resistance  
of coil

$$Z = \frac{V}{I} = \frac{50}{5} = 10$$

$$X_L = \sqrt{Z^2 - R^2} = \sqrt{(10)^2 - (4)^2}$$

$$\Rightarrow 9.168 \Omega$$

$$\therefore \text{Reactance} = 9.168 \Omega$$

$$\text{Combined resistance} = 20 + 4 = 24 \Omega$$

combined impedance,

$$Z_s = \sqrt{(R+s)^2 + (X_L)^2}$$


$$= \sqrt{(24)^2 + (9.168)^2} = 25.6 \Omega$$

$$V = Z \cdot I \Rightarrow 25.6 \times 5 \Rightarrow 128 \text{ V}$$
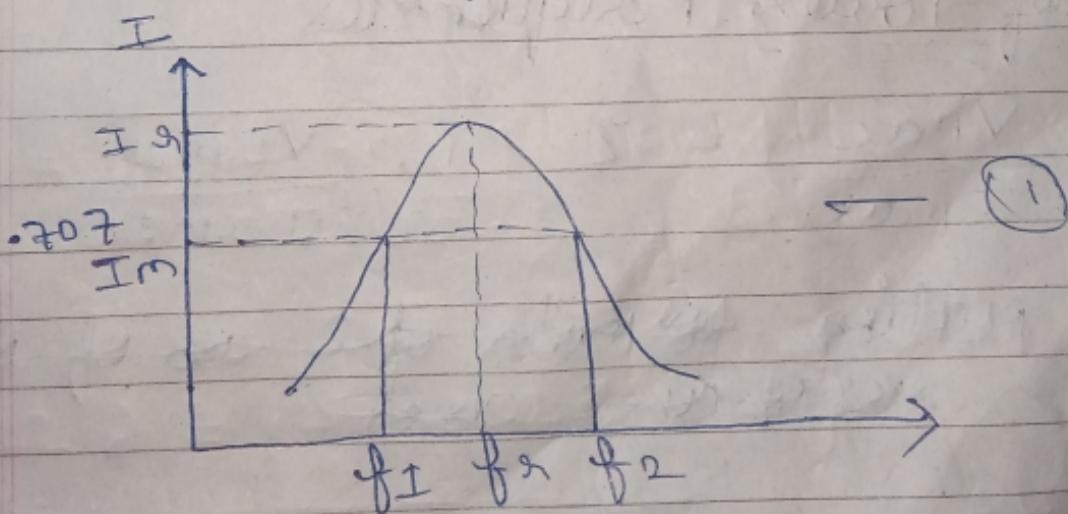
## Ans 1. Selectivity (RLC resonant circuit)

Selectivity of a circuit is a measure of its ability to reject any frequencies either side of the points. A more selective circuit will have narrower bandwidth whereas a less selective circuit will have a wider bandwidth.

The selectivity of a series resonance circuit can be controlled by adjusting the value of resistance keeping the other components the same.



$$(BW) \text{ Band width} \Rightarrow f_2 - f_1$$

$$\text{Selectivity} \Rightarrow \frac{f_r}{BW} \Rightarrow \frac{f_r}{f_2 - f_1}$$

## Band width

in figure ①

Range of frequencies over which circuit current is equal to or more than 70.7 % of max current.

$$B.W. = f_2 - f_1$$

$f_1$  = lower cutoff frequency

$f_2$  = upper cutoff frequency

$$f_1 = f_r - \frac{B.W.}{2}$$

$$f_2 = f_r + \frac{B.W.}{2}$$

## Half-Power Frequencies

$$\therefore \frac{V_{max}}{I_{max}} = Z, \quad \frac{V_{rms}}{I_{rms}} = R$$

Putting formula of 2 as of RLC  
~~resonance case~~

$$\Rightarrow \frac{V_{max}}{I_{max}} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\Rightarrow \left(\frac{V_{max}}{I_{max}}\right)^2 = R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2$$

$$\Rightarrow \left( \omega L - \frac{1}{\omega C} \right) = \sqrt{\left( \frac{V_{max}}{I_{max}} \right)^2 - R^2}$$

$$\Rightarrow \frac{V_{max}}{I_{max}} = \sqrt{2} \frac{V_{rms}}{I_{rms}}$$

as half-power frequencies  
are obtained by setting  
 $Z = \sqrt{2} R$

$$\Rightarrow \left( \omega L - \frac{1}{\omega C} \right) = \sqrt{2 \frac{V_{rms}^2}{I_{rms}^2} - R^2}$$

$$\left( \omega^2 L - \frac{1}{C} \right) = \omega \sqrt{2R^2 - R^2}$$

$$\omega^2 L - \frac{1}{C} = \omega (\pm R)$$

$$\omega^2 L - \omega (\pm R) - \frac{1}{C} = 0$$

for  $+\omega R$   
 $\omega^2 L - \omega R - (1/C) = 0$

$$\omega_1 = \frac{R \pm \sqrt{R^2 + 4L/C}}{2L}$$

$$\omega_2 = R \approx \sqrt{R}$$

$$\therefore \omega \neq -\omega$$

$$\omega_1 = \frac{R + \sqrt{R^2 + 4L/C}}{2L}$$

similarly for negative term of R

$$\omega^2 L + \omega R - (1/C) = 0$$

$$\omega_3 = \frac{-R + \sqrt{R^2 + 4L/C}}{2L}$$

(excluding one value since  
 $\omega$  cannot be negative)

$\omega_1$  and  $\omega_3$  are Half-power frequencies

$$\omega_1 = \frac{+R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_3 = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

Ans 2. coil I  $\Rightarrow$

$$R_1 = 1.5 \Omega, Z_1 = 6 \Omega$$

$$x_{L1} = \sqrt{(Z)^2 - (R)^2}$$

$$\Rightarrow \sqrt{33.75}$$

$$\Rightarrow 5.81 \Omega$$

coil II  $\Rightarrow$

$R_2 = 2 \Omega$ ,  $x$   
Let inductive reactance of second  
coil is  $x \Omega$ .  
 $x_{12} = x \Omega$

Impedance of whole circuit  
 $\Rightarrow \frac{V}{I} \Rightarrow \frac{230}{7}$

$$\therefore \frac{230}{7} = \sqrt{(1.5+2)^2 + (5.81+x)^2}$$

$$\sqrt{(32.85)^2 - 12.25} = 5.81 + x$$

$$\sqrt{1066.8725} = 5.81 + x$$

$$32.85 = 5.81 + x$$

$$x = 26.85$$

Inductance of second coil ( $L$ )

$$\omega L = 26.85$$

$$2\pi \times 50 \times L = 26.85$$

$$L \Rightarrow \frac{0.2685}{3.14} H$$

$$\Rightarrow \underline{\underline{85.5 \text{ mH}}}$$