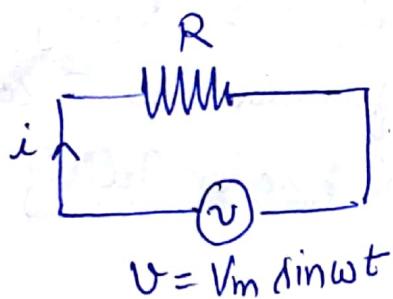


## Unit-2 (AC Circuits)

### AC through Pure Resistance only

Lecture



Let the applied voltage be  $V = V_m \sin \omega t$   
 Let  $R = \text{Resistance}$ ,  $i = \text{Instantaneous current}$

$$V = IR$$

$$V_m \sin \omega t = iR$$


$$i = \frac{V_m}{R} \sin \omega t$$

Current  $i$  is max, when  $\sin \omega t = 1$ ,  $\therefore I_m = \frac{V_m}{R}$

$$i = I_m \sin \omega t$$

→ Voltage and current are in phase with each other

With each other

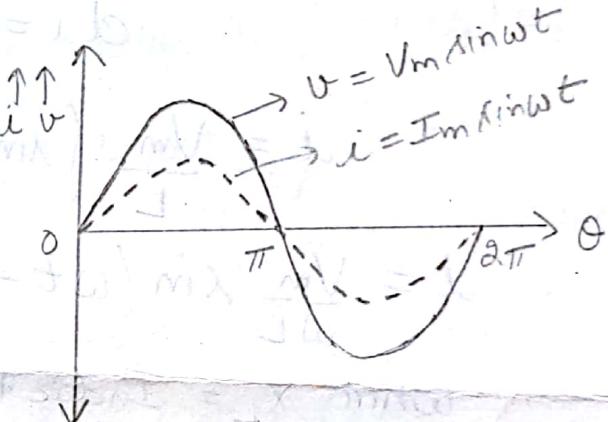

→ Power:

Instantaneous Power:

$$P = Vi = V_m \sin \omega t I_m \sin \omega t$$

$$P = V_m I_m \sin^2 \omega t = \frac{V_m I_m}{2} (1 - \cos 2\omega t)$$

$$P = \frac{V_m I_m}{2} - \frac{V_m I_m \cos 2\omega t}{2}$$

Constant part      Pulsating Part


→ Average value of  $\frac{V_m I_m \cos 2\omega t}{2}$  over complete cycle is zero

∴ Power for whole cycle


$$P = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}}$$

$$P = V_{rms} I_{rms}$$

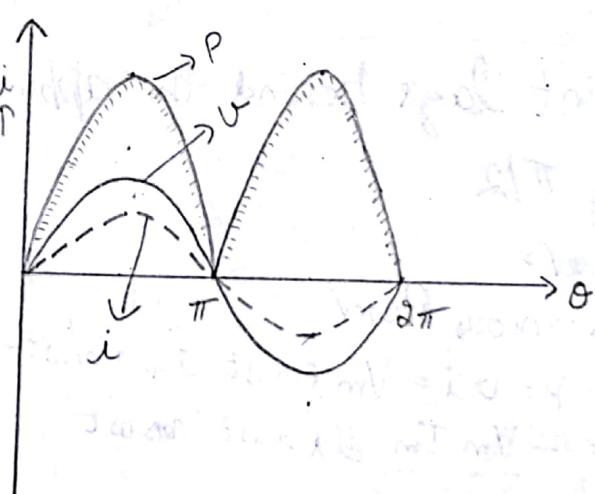In pure Resistive ckt, power is never zero.



## AC through pure inductance only

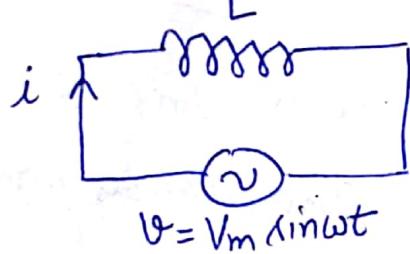

→ When an alternating voltage is applied to the pure inductive coil, a back emf is produced due to self inductance of coil.

The back emf opposes the rise or fall of current through coil

$$V = L \frac{di}{dt}$$

$$V_m \sin \omega t = L \frac{di}{dt}$$

$$di = \frac{V_m}{L} \sin \omega t dt$$

$$i = \frac{V_m}{L} \int \sin \omega t dt = \frac{V_m}{\omega L} (-\cos \omega t)$$

$$i = \frac{V_m}{\omega L} \sin(\omega t - \pi/2) = \frac{V_m}{X_L} \sin(\omega t - \pi/2)$$

Where  $X_L$  = Inductive Reactance  $= 2\pi f L$

Max. value of  $i$  is  $I_m = \frac{V_m}{\omega L}$  when  $\sin(\omega t - \pi/2) = 1$

$$i = I_m \sin(\omega t - \pi/2)$$

→ Current lags behind the applied voltage by  $\pi/2$

→ Power



Instantaneous Power

$$\begin{aligned} P &= Vi = V_m \sin \omega t I_m \sin(\omega t - \pi/2) \\ &= -\frac{V_m I_m}{2} 2 \sin \omega t \cos \omega t \\ &= -\frac{V_m I_m}{2} \sin 2\omega t \end{aligned}$$


Average value of  $\frac{V_m I_m}{2} \sin 2\omega t$  over complete cycle is zero

Average Power = 0

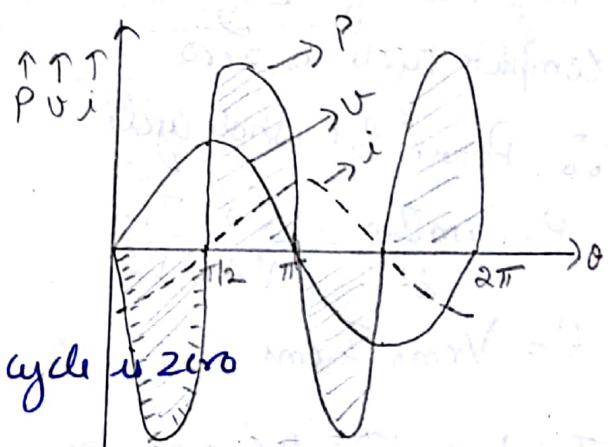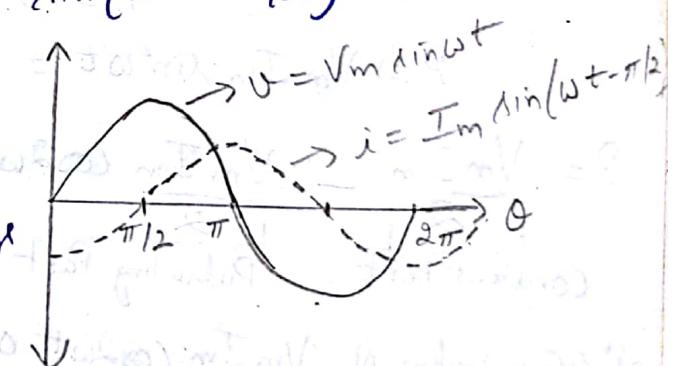→ No Power is consumed in pure inductive ckt



## AC through pure capacitance only

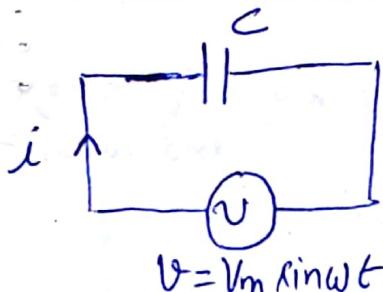

When an alternating voltage is applied to the plates of capacitor, the capacitor is charged first in one direction and then in opposite direction.

$$\text{Charge on plates, } Q = CV$$

$$Q = CV_m \sin \omega t$$

$$\text{Current, } i = \frac{dQ}{dt} = \frac{d(CV_m \sin \omega t)}{dt} = CV_m \omega \cos \omega t$$

$$= \frac{V_m}{1/\omega C} \cos \omega t = \frac{V_m}{1/\omega C} \sin(\omega t + \pi/2) = \frac{V_m}{X_C} \sin(\omega t + \pi/2)$$

$$\text{Max. value of current is } I_m = \frac{V_m}{X_C} \text{ when } \sin(\omega t + \pi/2) = 1$$

Where  $X_C = \text{Capacitive Reactance} = \frac{1}{2\pi f C}$

→ Current leads the voltage by  $\pi/2$

→ Power

$$\text{Instantaneous Power} = P = Vi$$

$$P = V_m \sin \omega t \cdot I_m \sin(\omega t + \pi/2)$$

$$= V_m I_m \sin \omega t \cos \omega t$$

$$= \frac{V_m I_m}{2} 2 \sin \omega t \cos \omega t$$



$$= \frac{V_m I_m}{2} \sin 2\omega t$$

$$\text{Average value of } \frac{V_m I_m}{2} \sin 2\omega t$$

Over complete cycle is zero

$$\text{Average Power} = 0$$

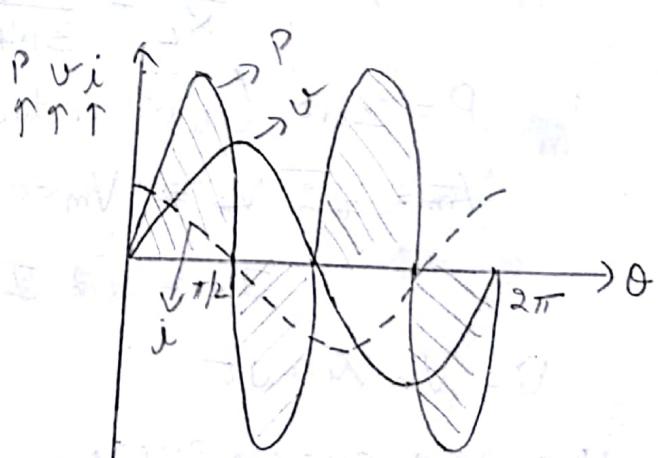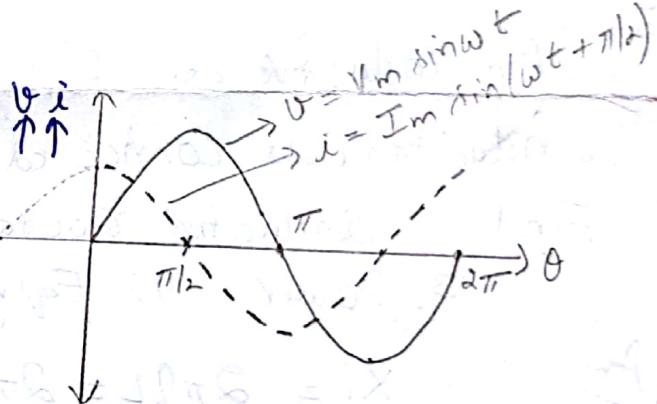→ No Power is consumed in pure capacitive ckt.



Q1 An ac ckt consists of pure resistance of  $10\Omega$  and is connected across an ac supply of  $230V, 50\text{Hz}$ . Calculate (i) Current (2) Power Consumed (3) Eq'n of voltage and current.

Ans (1) Current in the ckt,  $I = \frac{V}{R} = \frac{230}{10} = 23\text{A}$

(2) Power Consumed,  $P = V_{rms} I_{rms} = 230 \times 23 = 5290\text{W}$

Max. Value of applied voltage,  $\left[ \frac{V_m}{\sqrt{2}} = V_{rms} \right], V_m = \sqrt{2} \times 230 = 325.27\text{V}$

Max. Value of current  $\left[ \frac{I_m}{\sqrt{2}} = I_{rms} \right], I_m = \sqrt{2} \times 23 = 32.53\text{A}$

$$\omega = 2\pi f = 2\pi \times 50 = 314.16 \text{ rad/s}$$

(3)  $V = V_m \sin \omega t$   $i = I_m \sin \omega t$

$V = 325.27 \sin 314.16 t$   $i = 32.53 \sin 314.16 t$

Q2 An inductive coil having negligible resistance and  $0.1\text{Henry}$  inductance is connected across  $200V, 50\text{Hz}$  supply.

Find (1) inductive reactance (2) rms value of current

(3) Power (4) Eq'n for voltage and current.

Ans  $X_L = 2\pi f L = 2\pi \times 50 \times 0.1 = 31.416\Omega$

Current,  $I = \frac{V}{X_L} = \frac{200}{31.416} = 6.366 \text{ A}$

$P = \text{zero}$  (Pure inductive ckt doesn't consume power)

~~$V_m = \sqrt{2} V_{rms}$~~   $V_m = V_{rms} = \sqrt{2} \times 200 = 282.84\text{V}$

$$I_m = \sqrt{2} I_{rms} = \sqrt{2} \times 6.366 = 9\text{A}$$

$V = V_m \sin \omega t$


$$i = I_m \sin(\omega t - \pi/2)$$

$V = 282.84 \sin 314.16 t$

$$i = 9 \sin(314.16 t - \pi/2)$$

(3)

## R-L Series Circuit

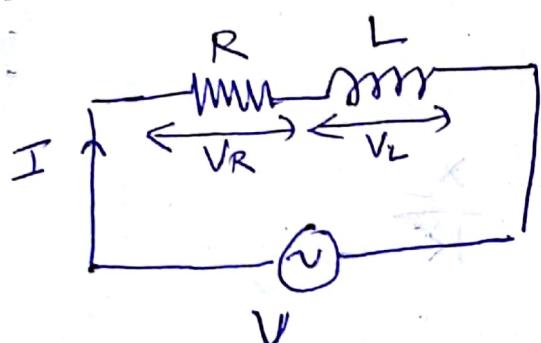


$$V = \text{RMS value of voltage}$$

$$I = \text{RMS value of current}$$

$V_R = IR$  (Voltage drop in resistance is in phase with current)

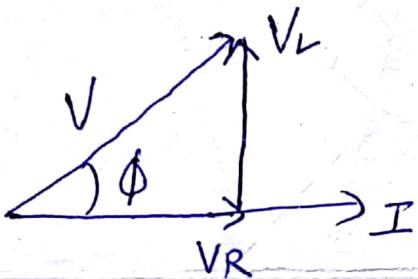$V_L = I \times L$  (Voltage drop in inductive reactance) (leads current by  $90^\circ$ )



The vector sum of  $V_R$  and  $V_L$  is equal to applied voltage  $V$ .

$$V = \sqrt{(V_R)^2 + (V_L)^2} = \sqrt{(IR)^2 + (IX)^2}$$

$$V = I \sqrt{R^2 + X_L^2}$$

$$V = I Z$$

$$I = \frac{V}{Z}$$

Where  $Z = \sqrt{R^2 + X_L^2}$  is the total opposition offered to the flow of alternating current by an R-L series circuit and is known as Impedance.

Phase Angle: Current in the circuit lags behind the applied voltage by an angle  $\phi$ .


$$\tan \phi = \frac{V_L}{V_R} = \frac{I X_L}{I R} = \frac{X_L}{R}$$

$$\phi = \tan^{-1} \frac{X_L}{R}$$
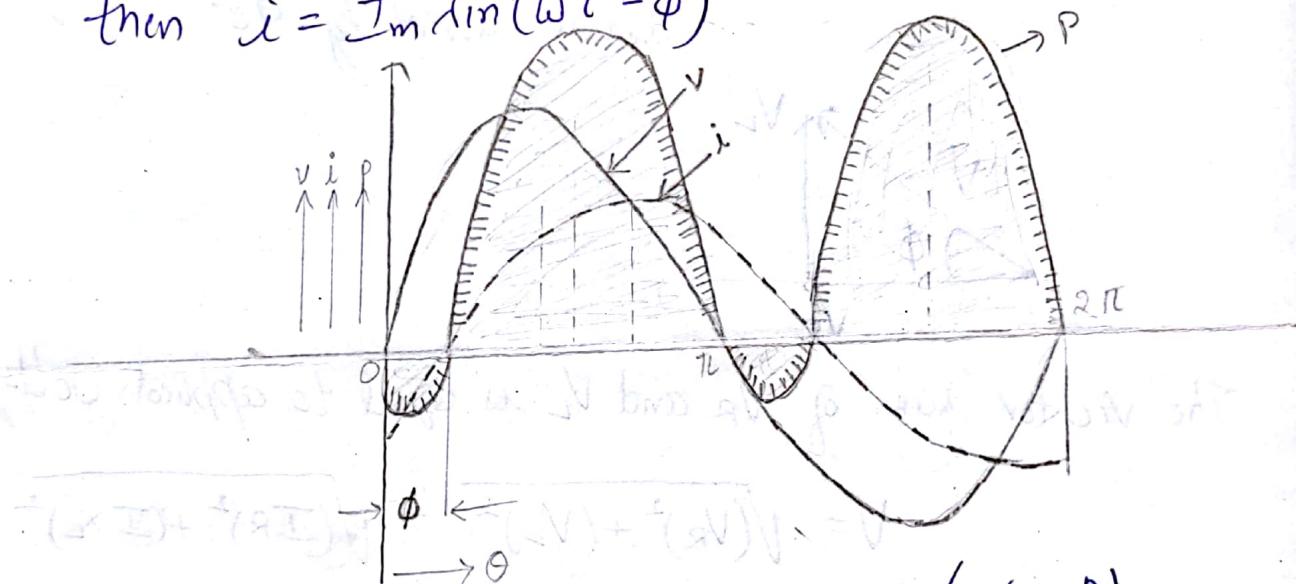
### Power

$$If V = V_m \sin \omega t$$

$$\text{then } i = I_m \sin(\omega t - \phi)$$



$$\text{Instantaneous Power, } P = V i = V_m \sin \omega t \ I_m \sin(\omega t - \phi)$$

$$= V_m \frac{I_m}{\sqrt{2}} \sin \omega t \sin(\omega t - \phi)$$

$$= \frac{V_m I_m}{\sqrt{2}} [\cos \phi - \cos(2\omega t - \phi)]$$

$$= \frac{V_m I_m}{\sqrt{2}} \cos \phi - \frac{V_m I_m}{\sqrt{2}} \cos(2\omega t - \phi),$$


bulating component

$$\begin{aligned} 2 \sin A \sin B \\ = \cos(A-B) - \cos(A+B) \end{aligned}$$

$$\text{Average Power, } P_{av} = \frac{V_m I_m}{\sqrt{2}} \cos \phi - 0$$

$$P = VI \cos \phi \quad [\cos \phi \text{ is Power Factor}]$$


## R C Series Circuit:

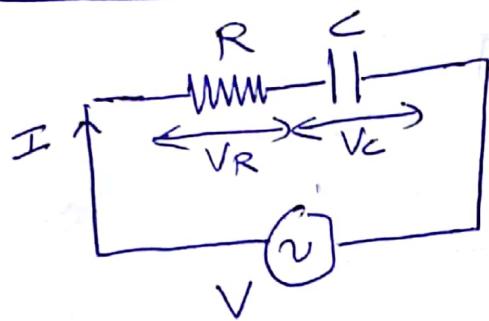

$V = \text{RMS value of applied voltage}$   
 $I = \text{RMS value of current}$

$VR = IR$  (Voltage drop in resistance is in phase with current)

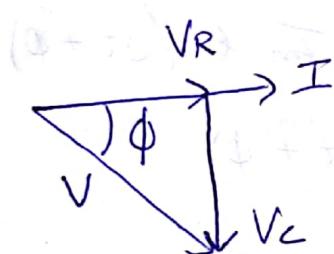$VC = IX_c$  (Voltage drop in capacitive reactance)  
lags current by  $90^\circ$



$$\begin{aligned} V &= \sqrt{VR^2 + VC^2} \\ &= \sqrt{(IR)^2 + (IX_c)^2} \\ &= I \sqrt{R^2 + X_c^2} \end{aligned}$$

$$V = I Z$$

$$I = \frac{V}{Z}$$

Where  $Z = \sqrt{R^2 + X_c^2}$  is total opposition offered to the flow of alternating current by RC series circuit.

### Phase Angle:

Current in the circuit leads the applied voltage by angle  $\phi$ .


$$\tan \phi = \frac{V_c}{V_R} = \frac{I X_c}{I R}$$

$$\phi = \tan^{-1} \left( \frac{X_c}{R} \right)$$

## Power

$$If \quad v = V_m \sin \omega t$$

$$i = I_m \sin(\omega t + \phi)$$

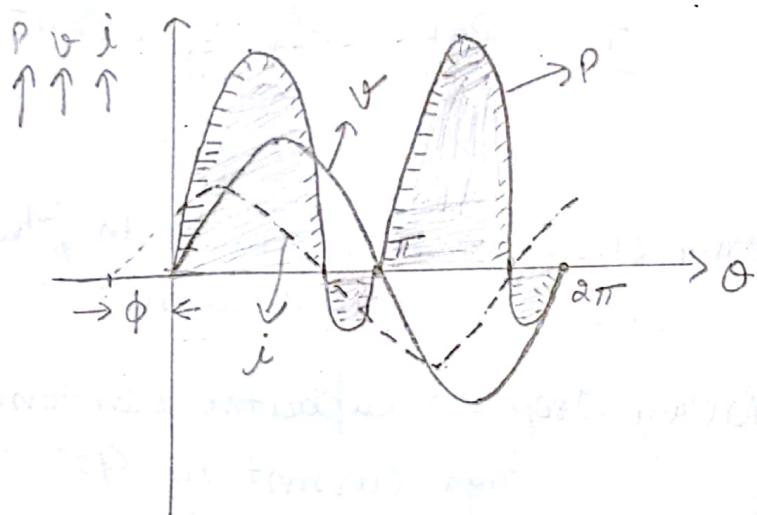

$$\text{Instantaneous Power, } P = vi = V_m \sin \omega t \cdot I_m \sin(\omega t + \phi)$$

$$= \frac{V_m I_m}{2} 2 \sin \omega t \sin(\omega t + \phi)$$

$$= \frac{V_m I_m}{2} [\cos \phi - \cos(2\omega t + \phi)]$$

$$= \underbrace{\frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos \phi}_{\text{constant part}} - \underbrace{\frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(2\omega t + \phi)}_{\text{Pulsating component}}$$

$$\text{Average Power, } P_{av} = \text{Avg of } \frac{V_m I_m}{\sqrt{2} \sqrt{2}} \cos \phi - \text{Avg of } \frac{V_m I_m}{\sqrt{2} \sqrt{2}} \cos(2\omega t + \phi)$$

$$= \frac{V_m I_m}{\sqrt{2} \sqrt{2}} \cos \phi - \text{zero}$$

$$P = V I \cos \phi$$

$$P = (I^2 Z) I \frac{V_R}{V} = (I^2 Z) I \frac{IR}{I^2 Z}$$

$$P = I^2 R$$


This shows Power is Consumed in Resistance only, Capacitor doesn't consume any power.

(5)

## Impedance Triangle

A right angled triangle whose base represents ckt resistance, perpendicular represents ckt reactance and hypotenuse represents ckt impedance.

For RL ckt

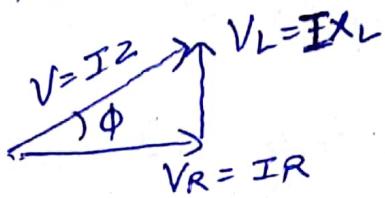

$$Z = \sqrt{R^2 + X_L^2}$$

$$\cos \phi = \frac{R}{Z}$$

## Power Factor

→ Power factor is defined as cosine of angle b/w voltage and current in an AC circuit.

(i)  $\cos \phi$

→ (2)  $\frac{R}{Z} = \frac{\text{Resistance}}{\text{Impedance}}$

(3)  $\frac{\text{True Power}}{\text{Apparent Power}} = \frac{W}{\text{Volt-ampere}} = \frac{W}{VA}$

$$\text{True Power} = VI \cos \phi$$

$$\text{Apparent Power} = VI$$

$$\text{Reactive Power} = VI \sin \phi$$


→ In case of pure resistive circuit, current is in phase with circuit voltage i.e.  $\phi = 0$ .  $\therefore$  power factor of circuit,  $\cos \phi = 1$ .

→ In case of pure inductive or capacitive circuit current is  $90^\circ$  out of phase with circuit voltage i.e.  $\phi = 90^\circ$ ;  $\therefore \cos \phi = 0$ .

→ Value of p.f. can never be more than one.
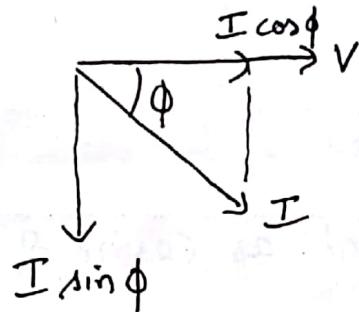
## Active and Reactive Components of Circuit Current

- Active component is that which is in phase with the applied voltage  $V$  i.e.  $I \cos \phi$ . It is also known as 'wattful' component.
- Reactive component is that which is in quadrature with  $V$  i.e.  $I \sin \phi$ . It is also known as 'wattless' component.



- True Power :- Power which is actually consumed in an ac circuit. Power is consumed only in Resistance.

$$\text{True Power} = VI \cos \phi \quad [\text{KW}]$$

$$\text{Apparent Power} = VI \quad [\text{KVA}]$$

$$\text{Reactive Power} = V.I \sin \phi \quad [\text{KVAR}]$$

$$\text{True Power} = VI \cos \phi = I^2 R$$

- Reactive Power

Power developed in the inductive reactance of circuit

$$Q = VI \sin \phi \quad [\text{VAR}] = I^2 X_L \quad \left[ \because \sin \phi = \frac{X_L}{Z} \right]$$

Volt-ampere reactive

- Apparent Power

given by product of  $\sqrt{m}$  values of current and voltage

$$S = VI = I^2 Z$$

$$P = I^2 R$$

$$Q = I^2 X_L$$

$$S = I^2 Z$$

(6)

Q1 A coil of  $12\Omega$  resistance and  $0.2\text{H}$  inductance is connected across a  $220\text{V}$ ,  $50\text{Hz}$  supply.

Find (a) the current (b) Phase angle (c) Power factor

Ans

$$R = 12\Omega, L = 0.2\text{H}$$

$$X_L = 2\pi fL = 2 \times 3.14 \times 50 \times 0.2 = 62.8\Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{12^2 + (62.8)^2} = 63.936\Omega$$

$$(a) \text{ Current, } I = \frac{V}{Z} = \frac{220}{63.96} = 3.44\text{A}$$

$$(b) \text{ Phase Angle, } \phi = \tan^{-1}\left(\frac{X_L}{R}\right) = \tan^{-1}\left(\frac{62.8}{12}\right) = 79.18^\circ$$

$$(c) \cos \phi = \frac{R}{Z} = 0.188$$

Q2 A voltage  $v(t) = 150 \sin(27\pi f)t$ ,  $50\text{Hz}$  is applied to a series circuit consisting of  $10\Omega$  resistance,  $0.0318\text{H}$  inductance. Determine (a) Expression for current  $i(t)$  (b) Phase angle b/w voltage and current (c) Power Factor (d) Active Power Consumed

Ans

$$v(t) = 150 \sin(27\pi f)t$$

$$f = 50\text{Hz}, R = 10\Omega, L = 0.0318\text{H}$$

$$X_L = 27\pi fL = 27\pi \times 50 \times 0.0318 = 134.8\Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{10^2 + (134.8)^2} = 135.17\Omega$$

(a) Current is given by  
 $i(t) = I_m \sin(\omega t - \phi)$  for R-L ckt.

$$I_m = \frac{V_m}{Z} = \frac{150}{135.17} = 1.1097 \text{ A}$$

$$i(t) = 1.1097 \sin(27\pi f t - \phi)$$

(b) Phase angle,  $\phi = \tan^{-1} \frac{X_L}{R} = \tan^{-1} \left( \frac{134.8}{10} \right) = 85.75^\circ$

(c) Power Factor,  $\cos \phi = \cos(85.75^\circ) = 0.0741$

(d) Power Consumed =  $V I \cos \phi = \frac{150}{\sqrt{2}} \times \frac{1.1097}{\sqrt{2}} \times 0.0741 = 6.169 \text{ W}$

Q3 An ac ckt consisting of resistance of  $14\Omega$  in series with a capacitor of  $250\mu\text{F}$  is connected across  $220\text{V}$ ,  $50\text{Hz}$  supply.  
 Find (a) current flowing (b) power factor (c) voltage drop across each element

(d) Power absorbed

$$\text{Ans} \quad V = 220\text{V}, f = 50\text{Hz}, R = 14\Omega, C = 250\mu\text{F} = 250 \times 10^{-6}\text{F}$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 50 \times 250 \times 10^{-6}} = 12.739\Omega$$

$$Z = \sqrt{R^2 + X_C^2} = \sqrt{14^2 + (12.739)^2} = 18.93\Omega$$

(a) Current,  $I = \frac{V}{Z} = \frac{220}{18.93} = 11.623 \text{ A}$

(b)  $\phi = \tan^{-1} \frac{X_C}{R} = 42.30^\circ$

$$\text{P.F} = \cos \phi = \cos(42.30^\circ) = 0.739 \quad \left[ \text{or } \cos \phi = \frac{R}{Z} \right]$$

(c)  $V_R = IR = 11.623 \times 14 = 162.72\text{V}$


$$V_C = I X_C = 11.623 \times 12.739 = 148.06\text{V}$$

(d) Power absorbed =  $V I \cos \phi = 220 \times 11.623 \times 0.739 = 1889.67 \text{ W}$

## RLC Series Ckt

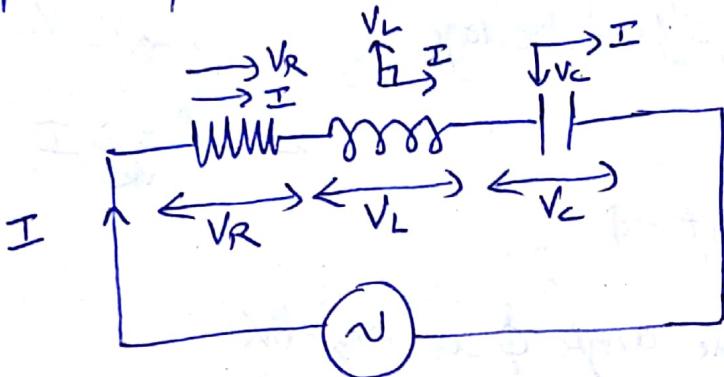(7)

A circuit that contains pure resistance, pure inductance and pure capacitance, all connected in series.




$V_R = IR$  i.e. voltage across R is in phase with I

$V_L = I X_L$  (voltage across L leads I by  $\pi/2$ )

$V_C = I X_C$  (voltage across C lags I by  $\pi/2$ )

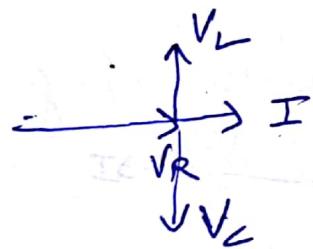
→  $V_L$  and  $V_C$  are  $180^\circ$  out of phase with each other



$$V = \sqrt{V_R^2 + (V_L - V_C)^2} = \sqrt{(IR)^2 + (IX_L - IX_C)^2}$$

$$V = I \sqrt{R^2 + (X_L - X_C)^2}$$
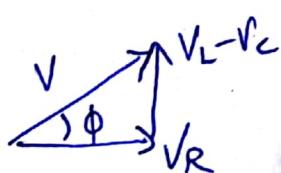
$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{V}{Z}$$



$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{IX_L - IX_C}{IR}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$\phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$

Three Cases of RLC Series Ckt:


(1) When  $X_L > X_C$ , phase angle,  $\phi$  is positive

Circuit behaves as an R-L series ckt.

Current lags behind the applied voltage

$$\text{If } V = V_m \sin \omega t$$
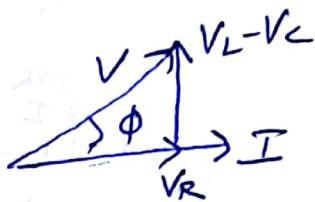
$$\text{then } i = I_m \sin(\omega t - \phi)$$




(2) When  $X_L < X_C$ , Phase angle  $\phi$  is negative

Circuit behaves as an R-C series ckt

Current leads the applied voltage

$$\text{If } V = V_m \sin \omega t$$
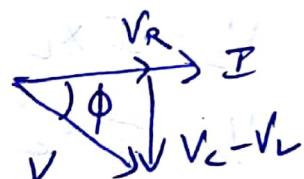
$$\text{then } i = I_m \sin(\omega t + \phi)$$



(3) When  $X_L = X_C$ , Phase angle is zero

Ckt behaves like pure resistive ckt

Current is in phase with applied voltage

$$V = V_R \rightarrow I$$

$$\text{If } V = V_m \sin \omega t$$

$$\text{then } i = I_m \sin \omega t$$

Power consumed by series RLC ckt,  $P = VI \cos \phi$

## Series Resonance in RLC ckt (Voltage Resonance)

(8)



- In  $\text{RLC}_{\text{series}}$  ckt, When ckt current is in phase with the applied voltage, the circuit is said to be in series resonance.
- This condition is obtained in an R-L-C ckt  
When  $X_L = X_C$
- Impedance  $Z_r = \sqrt{R^2 + (X_L - X_C)^2}$   
at Resonance  $= R$
- Current,  $I_r = \frac{V}{R}$
- When a series RLC ckt is in resonance, it possess minimum impedance ( $Z = R$ ), Hence ckt current is maximum.
- Resonant Frequency: The frequency at which net reactance of the series ckt is zero

$$X_L - X_C = 0 \Rightarrow X_L = X_C$$

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$f_r^2 = \frac{1}{4\pi^2 LC}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

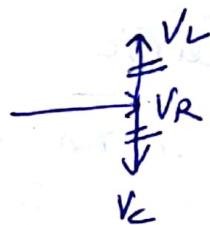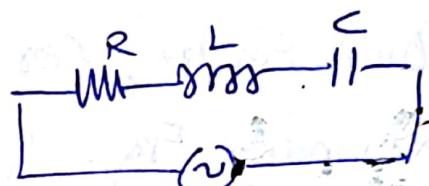


When an R-L-C ckt. is in resonance:

- (1) Net Reactance of the ckt is zero i.e.  $X_L - X_C = 0$
- (2) Circuit Impedance is minimum i.e.  $Z_r = R$
- (3) Circuit Current is maximum i.e.  $I_r = \frac{V}{R}$
- (4) Power Dissipated is maximum i.e.  $P_r = I_r^2 R$
- (5) Power Factor,  $\cos \phi = 1$  [ $\because \phi = 0$ ]
- (6) Resonant Freq.  $f_r = \frac{1}{2\pi\sqrt{LC}}$
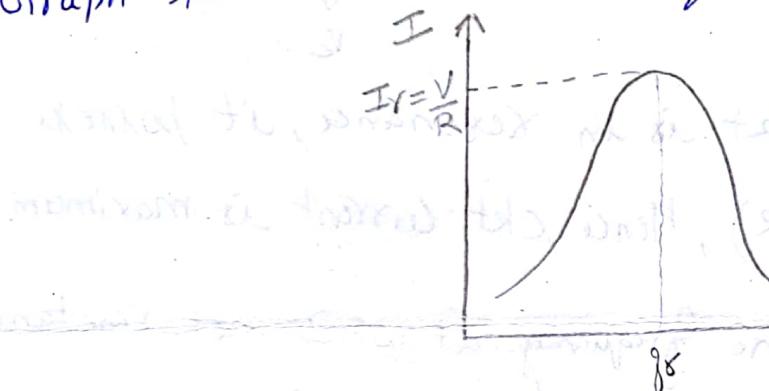
### Resonance Curve

Graph b/w current and frequency is known as Resonance Curve



(1) For any freq. less than  $f_r$ ,

$X_L < X_C$ , ckt acts as capacitive ckt


(2) For any freq. higher than  $f_r$ ,

$X_L > X_C$ , ckt acts as inductive ckt

(3) For  $f = f_r$ ,  $X_L = X_C$

Ckt behaves as resistive ckt
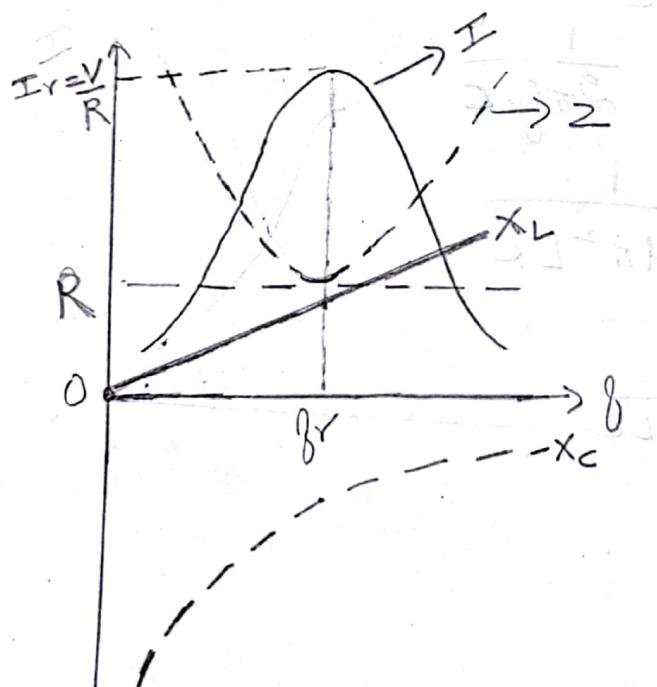
### Variation of Circuit Parameters with Frequency



#### (1) Resistance

Resistance is constant (fixed value)  
Represented by straight line.

(2)  $\underline{X_L} \quad X_L = 2\pi f L$

$X_L \propto f$

$X_L$  is directly proportional to  $f$

(3)  $\underline{X_C} \quad X_C = \frac{1}{2\pi f C}, \quad X_C \propto \frac{1}{f}$

$X_C$  is inversely proportional to  $f$


(4)  $\underline{Z} \quad$  Circuit Impedance

$Z$  has min. value ( $R$ ) at  $f_r$

(9)
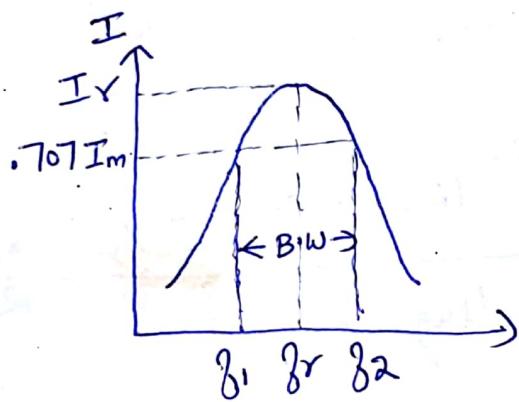
## Band width

Range of frequencies over which circuit current is equal to or more than 70.7% of max. current.



$$B.W = f_2 - f_1$$

$f_1$  = lower cut off freq.

$f_2$  = upper cut off freq

$$f_1 = f_r - \frac{B.W.}{2}$$

$$f_2 = f_r + \frac{B.W.}{2}$$

## Q-Factor of Series Resonant circuit (Quality Factor)

(i) It is given by voltage magnification produced in the circuit at resonance

$$\text{Q-Factor} = \frac{\text{Voltage across } L \text{ or } C}{\text{Applied voltage}} = \frac{I_o X_L}{I_o R} = \frac{X_L}{R}$$
$$= \frac{\omega_o L}{R} = \underline{\underline{\tan \phi}}$$



$$\text{Where } \omega_o = 2\pi f_o = 2\pi \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{LC}}$$

$$\text{Q-Factor} = \frac{L}{R} \times \frac{1}{\sqrt{LC}} = \underline{\underline{\frac{1}{R} \sqrt{\frac{L}{C}}}}$$

## Parallel Resonance (Current Resonance)

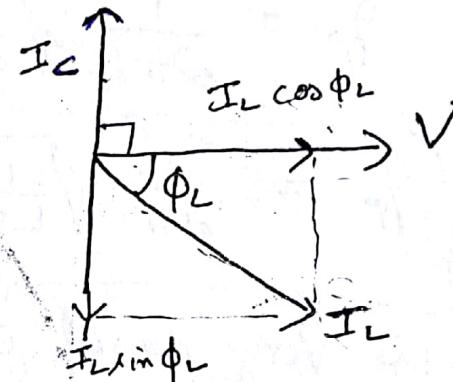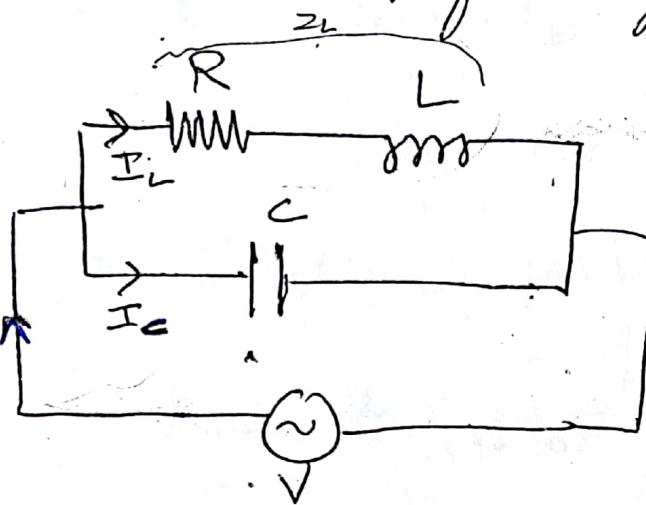(15)

- Consider an inductor of  $L$  Henry having some resistance  $R$  connected in parallel with a capacitor of capacitance  $C$  across a supply voltage of  $V$  Volts.



- $I_L$  will lag the voltage by an angle  $\phi$ , where  $\phi = \tan^{-1} \frac{X_L}{R}$
- $I_C$  will lead the voltage by  $90^\circ$ .
- For Resonance, the reactive component of circuit current must be zero

$$I_C - I_L \sin \phi_L = 0 \Rightarrow I_C = I_L \sin \phi_L$$

Where  $I_L = \frac{V}{Z_L}$ ,  $\sin \phi_L = \frac{X_L}{Z_L}$ ,  $I_C = \frac{V}{X_C}$



$$\frac{V}{X_C} - \frac{V}{Z_L} \times \frac{X_L}{Z_L} = 0$$

$$\sin \phi_L = \frac{X_L}{Z_L}$$

$$\cos \phi_L = \frac{R}{Z_L}$$

$$\frac{V}{X_C} = \frac{V}{Z_L} \times \frac{X_L}{Z_L}$$

$$Z_L^2 = X_L X_C$$

$$Z_L^2 = X_L X_C \Rightarrow Z_L^2 = \frac{WL}{WC} = \frac{L}{C}$$

$$R^2 + X_L^2 = \frac{WL}{WC}$$

$$R^2 + (2\pi f_0 L)^2 = \frac{L}{C}$$

$$2\pi f_0 L = \sqrt{\frac{L}{C} - R^2}$$

$$f_0 = \frac{1}{2\pi L} \sqrt{\frac{L}{C} - R^2}$$

Resonant  
freq

$$\boxed{f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}}$$

If  $R$  is very small compared to  $L$ ,

then resonant frequency  $f_0 = \frac{1}{2\pi\sqrt{LC}}$

Current at Resonance

The circuit current is  $I = I_L \cos \phi_L = \frac{V}{Z_L} \frac{R}{Z_L} = \frac{VR}{Z_L^2}$


Putting the value of  $Z_L^2 = \frac{L}{C}$

$$\boxed{I = \frac{VR}{L/C} = \frac{V}{L/CR}}$$

$\frac{L}{CR}$  is known as equivalent/dynamic impedance of the parallel circuit at resonance
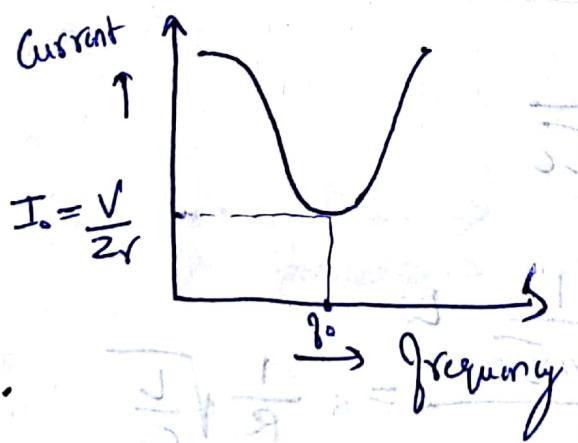
## Parallel Resonance (Important Points)

- Net susceptance is zero i.e.  $\frac{1}{Z} = \frac{X_L - X_C}{Z^2}$  or  $Z = \sqrt{\frac{L}{C}}$
- Admittance equals conductance
- Reactive (or wattless component) of line current is zero, hence circuit power factor is unity.
- Impedance is purely resistive i.e.  $Z_r = \frac{V}{I_{CR}}$   
because there is no frequency term.
- Line current is minimum and is equal to  $\frac{V}{Z_r}$   
and is in phase with applied voltage



## Q Factor of Parallel resonant circuit :-

The ratio of current circulating b/w its two branches to the line current drawn from the supply.

$$Q\text{-factor} = \frac{\text{Current circulating b/w } L \& C}{\text{Line current}} = \frac{I_C}{I}$$

$$I_C = \frac{V}{X_C} = \frac{V}{1/\omega C} = \omega C V.$$

$$\frac{I_C}{I} = \frac{V}{L/R}$$


$$Q\text{-factor} = \frac{\omega C V}{L/R} = \frac{\omega C V L}{V R} = \frac{\omega L}{R} = \frac{2\pi f_0 L}{R}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$Q\text{-factor} = \frac{2\pi \frac{1}{2\pi\sqrt{LC}} \cdot L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

# AC Parallel Circuits

## Phasor Method

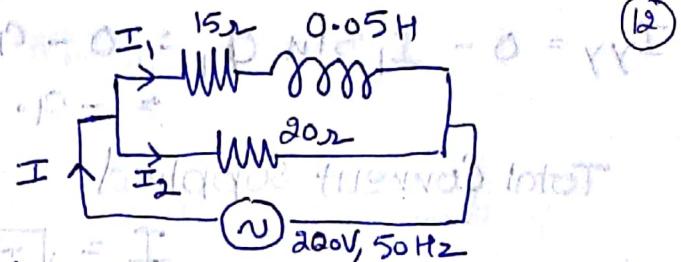

- Q) A coil resistance 15 ohm and inductance 0.05 H is connected in parallel with a non inductive resistance of 20 ohm. Find (i) Current in each branch (ii) Total Current Supplied (iii) phase angle and p.f of combination when a voltage of 200 volt at 50 Hz is applied (iv) Power Consumed in the Circuit.

Solu Applied Voltage  $V = 200V$  Supply Frequency  $f = 50Hz$

Branch I

$$R_1 = 15 \Omega$$

$$X_L = 2\pi f L_1 = 2\pi \times 50 \times 0.05 = 15.7 \Omega$$

$$Z_1 = \sqrt{R_1^2 + X_L^2} = \sqrt{(15)^2 + (15.7)^2} = 21.7 \Omega \text{ ohm.}$$

Current in the coil

$$I_1 = \frac{V}{Z_1} = \frac{200}{21.7} = 9.2A \text{ (Ans)}$$

Phase angle


$$\phi_1 = \tan^{-1}\left(\frac{X_L}{R}\right) = \tan^{-1}\left(\frac{15.7}{15}\right) = 46.3^\circ \text{ lagging}$$

Branch II

$$R_2 = 20 \Omega$$

$$I_2 = \frac{V}{R_2} = \frac{200}{20} = 10A \text{ (Ans.)}$$
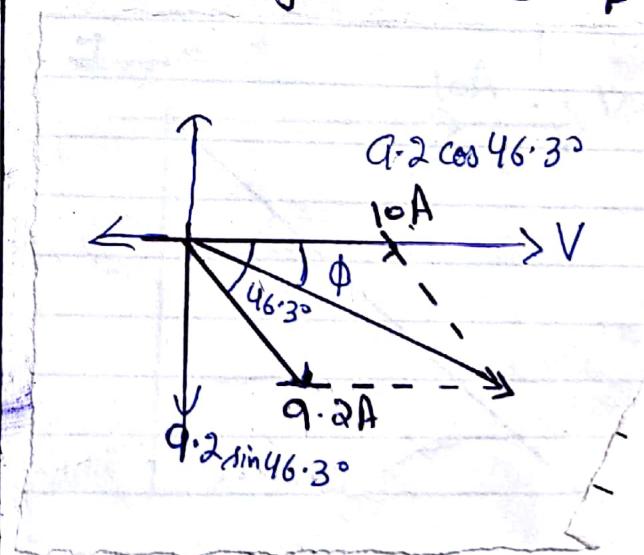
$$\text{Phase angle } \phi_2 = 0^\circ \text{ (I}_2 \text{ is in same phase as } V)$$



$$I_{xx} = I_2 + I_1 \cos \phi_1$$

$$= 10 + 9.2 \cos 46.3^\circ$$

$$= 10 + 9.2 \times 0.6909$$

$$= 16.356A$$

$$I_{yy} = 0 - I_1 \sin \phi_1 = 0 - 9.2 \sin 46.3^\circ = -9.2 \times 0.723 = -6.65 \text{ A}$$

Total Current Supplied

$$I = \sqrt{I_{xx}^2 + I_{yy}^2}$$

$$\text{Total current supplied } I = \sqrt{(16.356)^2 + (6.65)^2} \text{ Ans}$$

$$\text{Total current supplied } I = 17.6566 \text{ A (Ans)}$$

$$\text{Phase angle } \phi = \tan^{-1} \frac{I_{yy}}{I_{xx}} = \tan^{-1} \left( \frac{-6.65}{16.356} \right)$$

$$\text{Phase angle } \phi = -22.126^\circ \text{ (Ans)}$$

Power factor of the circuit

$$\cos \phi = \cos (-22.126^\circ)$$

$$= 0.9264 \text{ (lagging) Ans}$$

$$\text{Power } P = VI \cos \phi = 200 \times 17.656 \times 0.9264$$



$$= 3271.3 \text{ W (Ans)}$$



$$V = IR + \frac{1}{2\pi fL} I^2$$
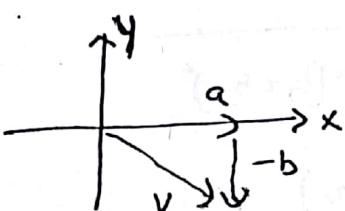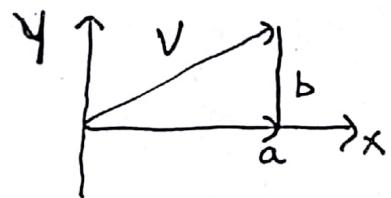
# Phasor Algebra / Symbolic Method / $j$ -Method

→ The symbol  $j(\sqrt{-1})$  is used to represent the vertical components of phasor quantities.



Phasor  $V$  is represented by

$$V = a + jb$$

$$V = a - jb$$

## Mathematical representation of Phasors


### a) Rectangular Form

$$\boxed{\bar{V} = a + jb}$$
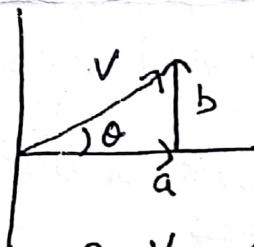
### b) Trigonometrical Form

$$\bar{V} = a + jb = V \cos \theta + j V \sin \theta$$

$$\boxed{\bar{V} = V (\cos \theta + j \sin \theta)}$$



$$a = V \cos \theta$$

$$b = V \sin \theta$$

$$\text{Where } V = \sqrt{a^2 + b^2}$$

$$\theta = \tan^{-1} \left( \frac{b}{a} \right)$$

### c) Polar Form

$$\boxed{\bar{V} = V \angle \theta}$$

### d) Exponential Form

$$\boxed{\bar{V} = V e^{j\theta}}$$

$$e^{j\theta} = \cos \theta + j \sin \theta$$

## Addition and Subtraction of Vector Quantities

Let  $\bar{V}_1 = a + jb$ ,  $\bar{V}_2 = a_2 + jb_2$

Addition

$$\bar{V} = \bar{V}_1 + \bar{V}_2 = (a_1 + a_2) + j(b_1 + b_2)$$

\* Rectangular Form is best suited for addition and subtraction

$$\text{Magnitude} = \sqrt{(a_1 + a_2)^2 + (b_1 + b_2)^2}$$

$$\theta = \tan^{-1} \left( \frac{b_1 + b_2}{a_1 + a_2} \right)$$

Subtraction

$$\bar{V} = \bar{V}_1 - \bar{V}_2 = (a_1 - a_2) - j(b_1 - b_2)$$

$$\text{Magnitude} = \sqrt{(a_1 - a_2)^2 + (b_1 - b_2)^2}$$

$$\theta = \tan^{-1} \left( \frac{b_1 - b_2}{a_1 - a_2} \right)$$

## Multiplication and Division of Phasor Quantities

\* Polar Form is best suited for multiplication and division

Let  $\bar{V}_1 = V_1 \angle \theta_1$ ,  $\bar{V}_2 = V_2 \angle \theta_2$

Multiplication  $\bar{V}_1 \times \bar{V}_2 = V_1 V_2 \angle (\theta_1 + \theta_2)$

Division  $\frac{\bar{V}_1}{\bar{V}_2} = \frac{V_1}{V_2} \angle (\theta_1 - \theta_2)$

Q Work the equivalent exponential and polar form of vector  $3+j4$ . (13)

$$\text{Magnitude} = \sqrt{3^2+4^2} = 5$$


$$\tan \theta = \frac{4}{3}$$

$$\theta = \tan^{-1}(4/3)$$

$$\theta = 53.1^\circ$$

$$\text{Exponential Form} = 5 e^{53.1^\circ}$$
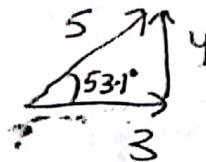
$$\text{Polar Form} = 5 \angle 53.1^\circ$$



Q A vector is represented by  $20e^{-j120^\circ}$ . Write the equivalent rectangular and polar form.

Rectangular form,  $a = 20 \cos(-120) = -10$

$$b = 20 \sin(-120) = -17.32$$

$$a+jb = -10 - j17.32$$

Polar Form

$$20 \angle -120^\circ$$

$$\cos(-120) = -0.5$$

$$\sin(-120) = 0.866$$

Q Given the following two vectors

$$A = 20 \angle 60^\circ \text{ and } B = 5 \angle 30^\circ$$


Find (i)  $A \times B$  (ii)  $A/B$

$$A \times B = 20 \angle 60^\circ \times 5 \angle 30^\circ = 100 \angle 90^\circ$$

$$\frac{A}{B} = \frac{20 \angle 60^\circ}{5 \angle 30^\circ} = 4 \angle 30^\circ$$


## RL and RC Circuits in Rectangular Form

RL

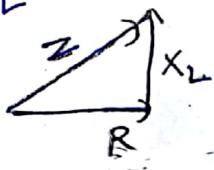

$$Z = R + jX_L$$

RC

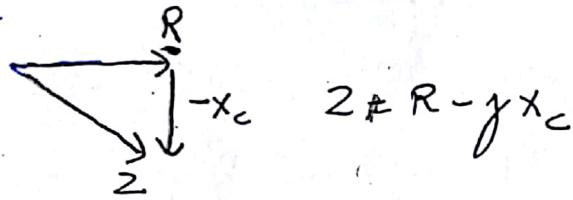

$$Z = R - jX_C$$

An alternating voltage of  $(160 + j120)$  is applied to a circuit and current in the circuit is given by  $(6 + j8)$  A.

Find (i) Values of elements of the circuit

(2) Power factor of the circuit

(3) Power consumed

$$V = 160 + j120, \quad I = 6 + j8$$

$$V = 200 \angle 36.87^\circ \quad [ \sqrt{160^2 + 120^2} = 200, \theta = \tan^{-1}\left(\frac{120}{160}\right) = 36.87^\circ ]$$

$$I = 10 \angle 53.13^\circ \quad [ \sqrt{6^2 + 8^2} = 10, \theta = \tan^{-1}\left(\frac{8}{6}\right) = 53.13^\circ ]$$

$$\text{Impedance, } Z = \frac{V}{I} = \frac{200 \angle 36.87^\circ}{10 \angle 53.13^\circ} = 20 \angle -16.26^\circ$$


$$= 20 \cos(-16.26) + j20 \sin(-16.26)$$

$$= 19.2 - j5.6$$

$$\text{i) } R = 19.2, \quad X_C = 5.6 \Rightarrow \frac{1}{2\pi f C} = 5.6 \Rightarrow \frac{1}{2\pi 50 C} = 5.6 \\ \Rightarrow C = 568.4 \mu F$$

$$\text{ii) } \cos \phi = \frac{19.2}{20} \left( \frac{R}{Z} \right) = 0.96 \text{ (leading)} \quad \text{(3) } P = VI \cos \phi = 200 \times 10 \times 0.96 \\ = 1920 W$$

(19)

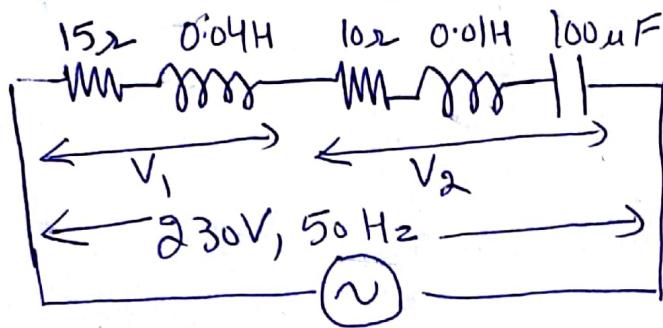

- Find (i) Current drawn  
 (ii) Voltages  $V_1$  &  $V_2$   
 (iii) Power Factor

Draw also Phasor diagram indicating the voltages  $V_1$ ,  $V_2$  and supply voltage wrt current.

$$\text{Ans} \quad X_{L_1} = 2\pi f L_1 = 2\pi 50 \times 0.04 = 12.566 \Omega$$

$$X_{L_2} = 2\pi f L_2 = 2\pi 50 \times 0.01 = 3.141 \Omega$$

$$X_{C_2} = \frac{1}{2\pi f C} = \frac{1}{2\pi 50 \times 100 \times 10^{-6}} = 31.831 \Omega$$

$$Z_1 = R_1 + jX_{L_1} = 15 + j12.566 = 19.568 \angle 39.95^\circ$$

$$Z_2 = R_2 + jX_{L_2} - jX_{C_2} = 10 + j3.141 - j31.831 \\ = 10 - j28.69 = 30.383 \angle -70.78^\circ$$

$$\text{Total Impedance, } Z = Z_1 + Z_2 = 15 + j12.566 + 10 - j28.69 \\ = 25 - j16.124 = 29.748 \angle -32.82^\circ$$

$$\text{Current } I = \frac{V}{Z} = \frac{230 \angle 0^\circ}{29.748 \angle -32.82^\circ} = 7.73 \angle 32.82^\circ \text{ A}$$

$$V_1 = I Z_1 = 7.73 \times 19.568 \angle (32.82^\circ + 39.95^\circ) \\ = 151.29 \angle 72.77^\circ \text{ V}$$

$$V_2 = I Z_2 = 7.73 \times 30.383 \angle (32.82^\circ - 70.78^\circ) \\ = 234.9 \angle -37.96^\circ \text{ V}$$

$$\text{Power Factor, } \cos \phi = \cos 32.82^\circ \\ = 0.8404 \text{ leading}$$

