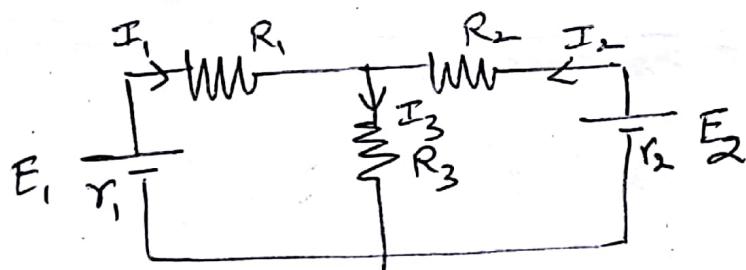



## Superposition Theorem YESTU Unit - I Part - 2 ~~Unit~~ B (1)

Acc. to this theorem, if there are two or more than two sources of emf's acting simultaneously in a linear bilateral n/w, the current flowing through any section is the algebraic sum of all the currents which should flow in that section if each source of emf were considered separately and all other sources are replaced by their internal resistance.

When both the sources are acting the currents flowing in  $R_1$ ,  $R_2$  and  $R_3$  are  $I_1$ ,  $I_2$  and  $I_3$  respectively



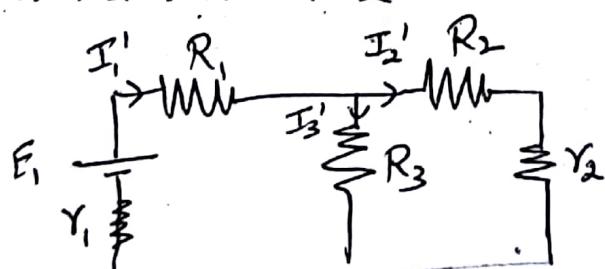
Step 1 Short circuit voltage source  $E_2$  and replace it by its internal resistance  $r_2$



Now, Find out branch currents  $I'_1$ ,  $I'_2$  and  $I'_3$

Step 2

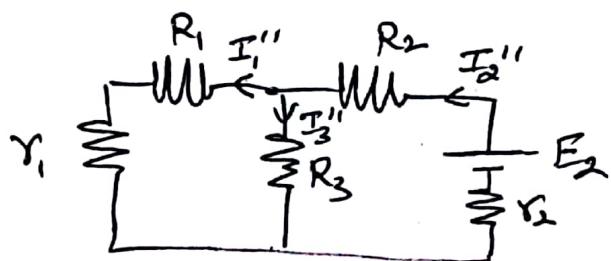Short circuit the voltage source  $E_1$  and replace it by its internal resistance  $r_1$



Now, find out branch currents  $I_1''$ ,  $I_2''$  and  $I_3''$

Step 3


Add algebraically the above currents and we find actual current

$$I_1 = I_1' - I_1''$$


$$I_2 = I_2' - I_2''$$

$$I_3 = I_3' + I_3''$$

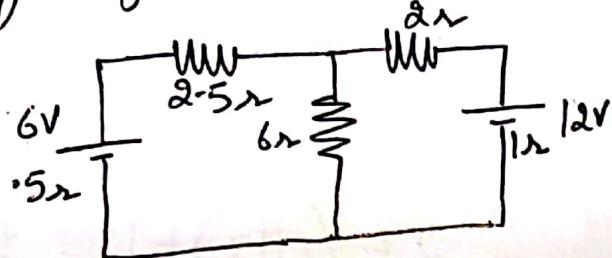(Q) Find different currents flowing in the branched and voltage across 6 ohm resistor using superposition theorem in n/w shown  
 Let battery emf be 6V and 12V, their internal resistance  $0.5\Omega$  and  $1\Omega$



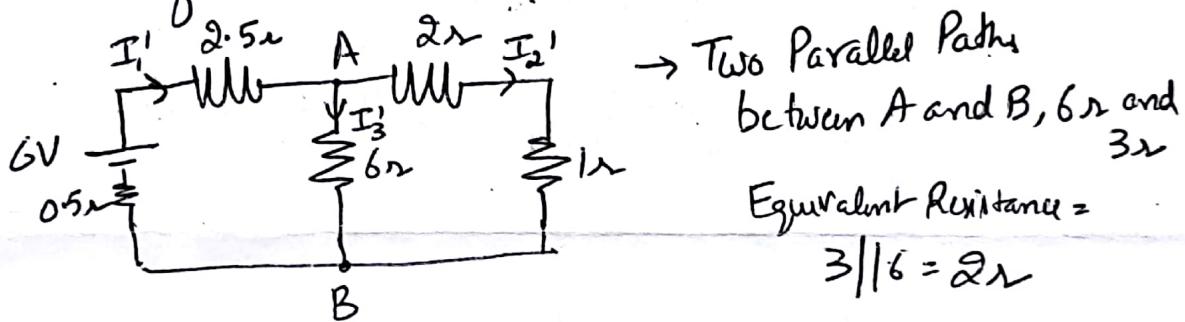Step 1 12 Volt battery has been removed through its internal resistance of  $1\Omega$ .




$$\text{Total Resistance} = 2.5 + 2 + 0.5 = 5\Omega$$

$$\therefore I_1' = \frac{6V}{5\Omega} = 1.2A$$

~~$$I_2' = \frac{6}{6+3} \times 1.2 = 0.8A$$~~

$$I_3' = I_1' - I_2' = 1.2 - 0.8 = 0.4A$$

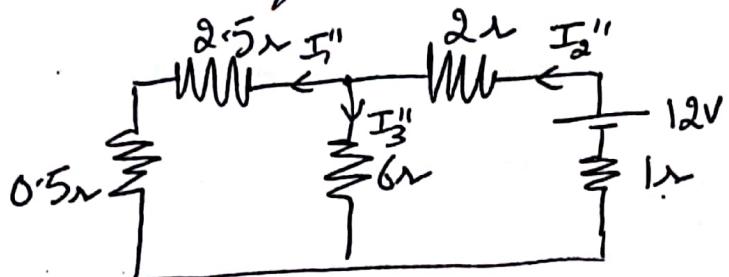Step 2 6 volt battery has been replaced by its internal resistance



$$\text{Total Resistance} = 2 + (6 \parallel 3) + 1 = 5\Omega$$

$$I_2'' = \frac{12}{5} = 2.4 \text{ A}$$

$$I_1'' = \frac{6}{9} \times 2.4 = 1.6 \text{ A}$$

$$I_3'' = I_2'' - I_1'' = 2.4 - 1.6 = 0.8 \text{ A}$$

Step 3 Net current

$$I_1 = I_1' - I_1'' = 1.2 - 1.6 = -0.4 \text{ A}$$



$$I_2 = I_2' - I_2'' = 1.6 \text{ A}$$

$$I_3 = I_3' + I_3'' = 1.2 \text{ A}$$

Q) Apply the principle of Superposition to the network shown to find out current in the  $10\Omega$  resistance.

Ans

Step 1: 4V has been removed

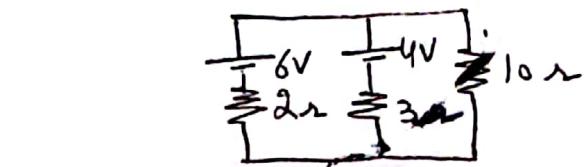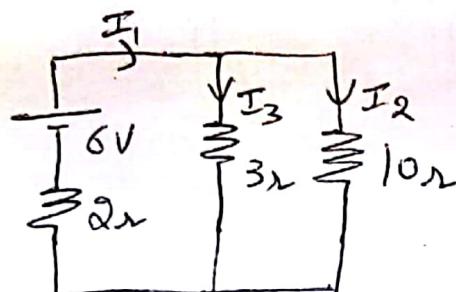

$$I_1 = \frac{6}{2+3||10} = \frac{6}{56} = \frac{39}{28} A$$


$$\begin{aligned} I_2 &= \frac{3}{3+10} \times I_1 = \frac{3}{13} \times \frac{39}{28} \\ &= \frac{9}{28} A \end{aligned}$$

Step 2

6V has been removed



OR

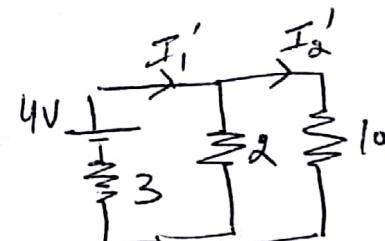

$$I_1' = \frac{4}{(2||10)+3} = \frac{6}{7}$$

$$I_2' = \frac{2}{2+10} \times I_1' = \frac{2}{12} \times \frac{6}{7} = \frac{1}{7}$$


Step 3

Net current through  $10\Omega$  resistor


$$= I_2 + I_2' = \frac{9}{28} + \frac{1}{7} = \underline{\underline{0.464 A}}$$

Q Find current through  $3\Omega$  resistance connected b/w C and D

Ans

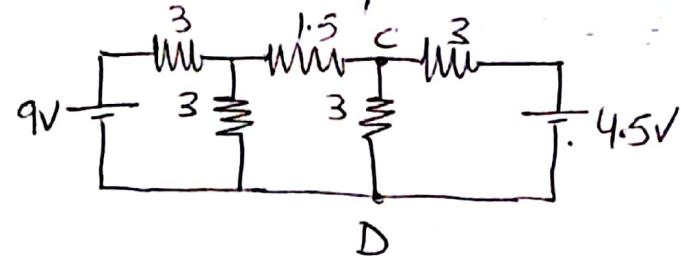


Step 1 . 4.5V battery has been removed

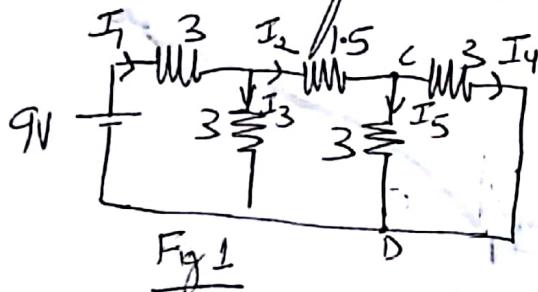

$$\text{Equivalent Resistance} = \left[ \left( 3 \parallel 3 \right) + 1.5 \right] \parallel 3 + 3 = 4.5$$

$$I_1 = \frac{9}{4.5} = 2A$$

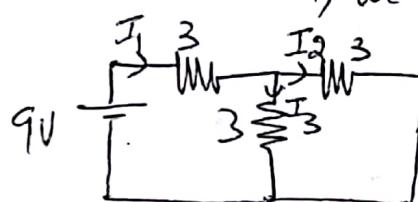For current division, we should have two parallel branches




$$I_2 = \frac{3}{3+3} \times 2 = 1A$$

and Now from Fig. 1 Find out value of  $I_5$  (By current division)

$$I_5 = \frac{3}{3+3} \times 1 = 0.5A$$


Step 2 9V battery has been removed

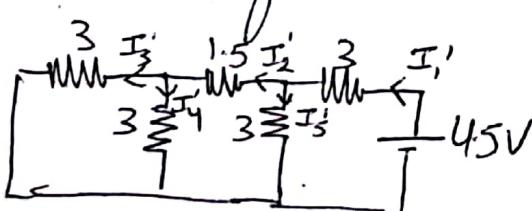

$$\text{EQUIVALENT RESISTANCE} = \left[ \left( 3 \parallel 3 \right) + 1.5 \right] \parallel 3 + 3 = 4.5\Omega$$

$$I_1' = \frac{4.5}{4.5} = 1A$$

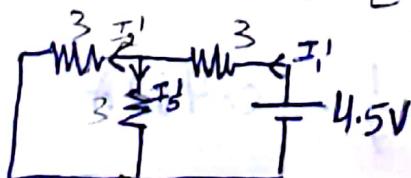Find current  $I_5'$  [By current division]



$$I_5' = \frac{3}{3+3} \times I_1' = 0.5A$$

Step 3


Net current flowing through  $3\Omega$  resistor connected b/w C and D

$= I_5 + I_5'$


$$= 0.5 + 0.5$$

$$= 1A$$

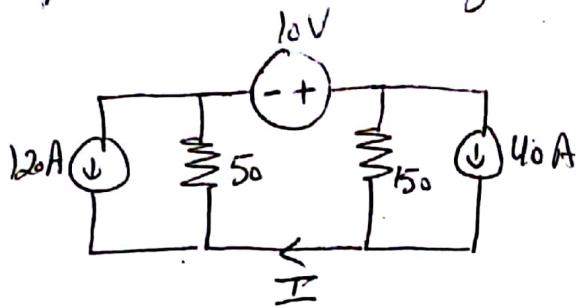
Use superposition theorem to find current  $I$  in the circuit, shown



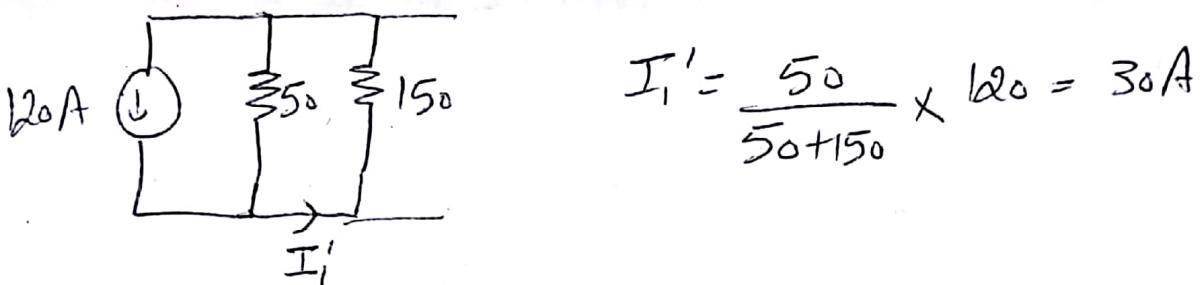
Step 1: 10V voltage source has been replaced by short circuit and 40A current source by open circuit



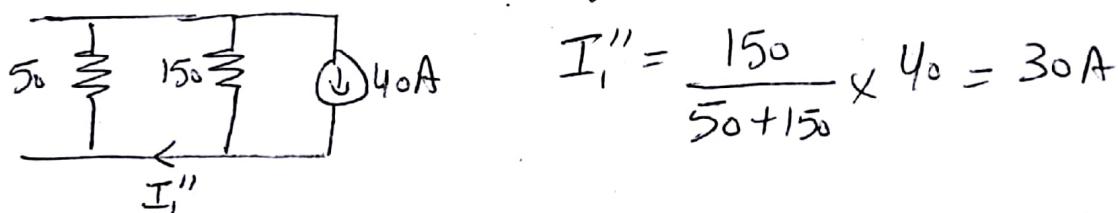Step 2: 120A current source has been replaced by open circuit and 10V voltage source by short circuit



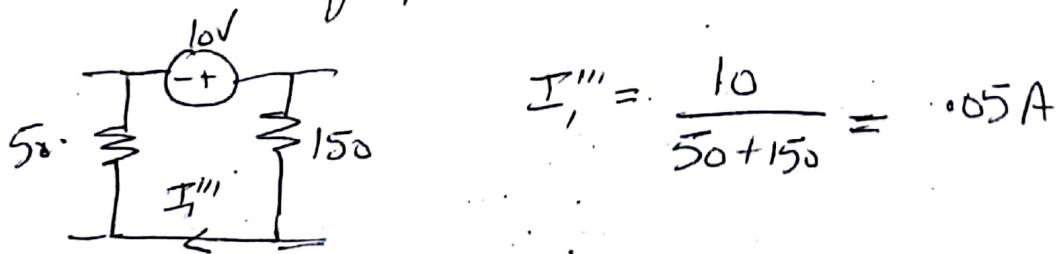Step 3: 120A current source and 40A current source have been replaced by open circuit



Step 4: Net current  $I = -I'_1 + I''_1 + I'''_1$

$$= -30 + 30 + 0.05$$

$$= 0.05A$$

## Thevenin Theorem

Statement → The current flowing through a load resistance  $R_L$  connected across any two terminals A and B of a linear, active bilateral network is given by  $V_{oc} \parallel (R_{th} + R_L)$

Where,  $V_{oc}$  is the open circuit voltage

i.e. Voltage across the two terminals when  $R_L$  is removed


$R_{th}$  is the internal resistance of network as viewed

back into the open circuited n/w from terminals A and B

with all voltage sources replaced by their internal resistance

and current source by open circuit.


### Explanation

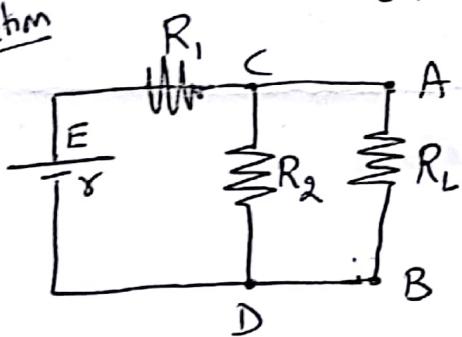

Suppose it is required to find current flowing through  $R_L$
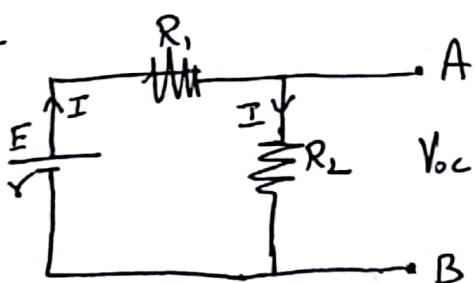
### Step 1

Remove  $R_L$  from the circuit terminals A and B and  
redraw the circuit



Now, calculate open circuit voltage  $V_{oc}$  which appears across terminals A and B when they are open

$$V_{oc} = \text{Drop across } R_2 = IR_2$$


$$I = \frac{E}{R_1 + R_2 + r}$$

$$V_{oc} = IR_2 = \frac{E R_2}{R_1 + R_2 + r}$$

It is also called Thvenin Voltage  $V_{Th}$

Step 2

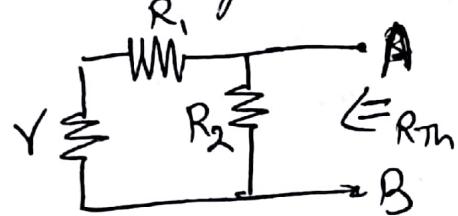Remove the voltage source and replace it by internal resistance



$$R_{Th} = (R_1 + r) \parallel R_2$$


This is equivalent resistance of n/w when viewed from terminals A and B

This resistance is also called Thvenin Resistance

Step 3

Thvenin Equivalent Circuit

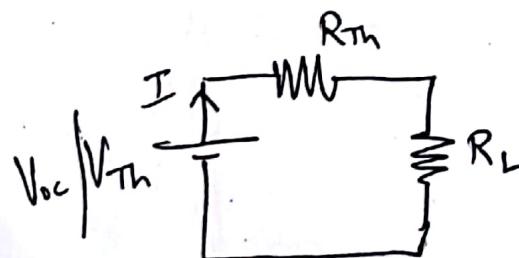
$R_L$  is connected back across terminals A and B




Current flowing through  $R_L$  is given by

$$I = \frac{V_{Th}}{R_{Th} + R_L}$$

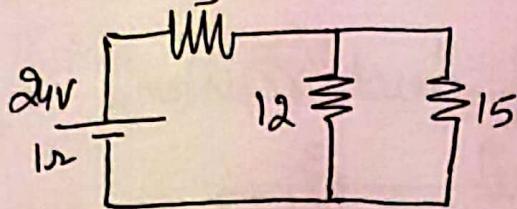(Q) Using Thevenin Theorem, find current in  $15\Omega$  resistor B(6)



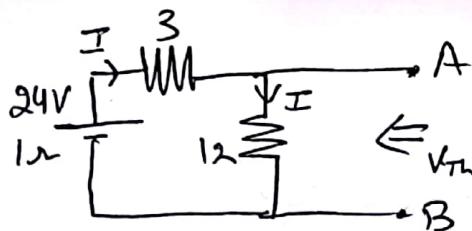
Ans Step 1  $15\Omega$  has been removed and replaced by open circuit.



$$I = \frac{24}{12+3+1} = 1.5A$$


$$V_{Th} = 12 \times 1.5 = 18V$$

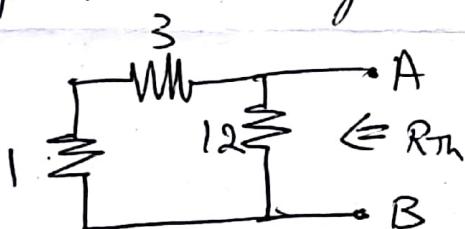Step 2 Replace 24V voltage source by its internal resistance




$$R_{Th} = (1+3) \parallel 12 = 4 \parallel 12 = \frac{4 \times 12}{4+12} = 3\Omega$$

Step 3 Thevenin Equivalent Circuit

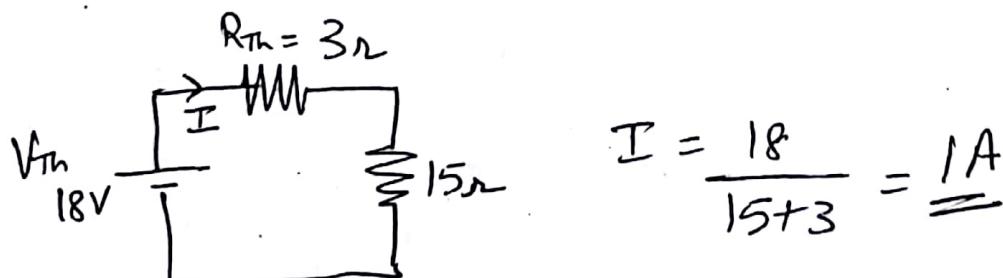


For a network shown determine the current flowing through  $R_L$  when value of load resistance is 3 ohm.

Thermal

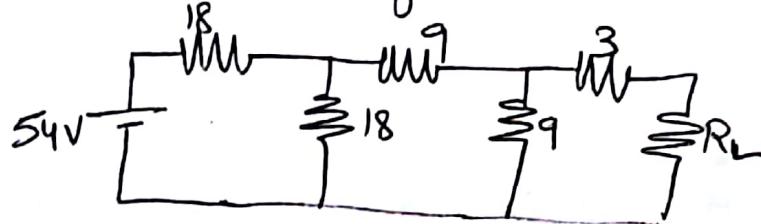

Aus

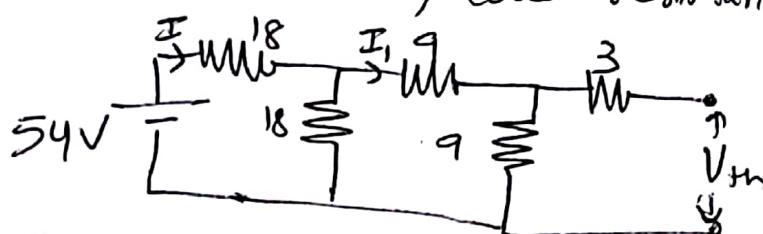Step 1 - To determine  $V_{th}$ , load resistance  $R_L$  is removed



$$R = (9+9) \parallel 18 + 18 = 27\Omega$$


$$I = \frac{54}{27} = 2A$$

$$I_1 = \frac{18}{18+18} \times I = \frac{18}{36} \times 2 = 1A$$

$$V_{th} = 9 \times I_1 = 9V$$


Step 2

Battery is replaced by short circuit

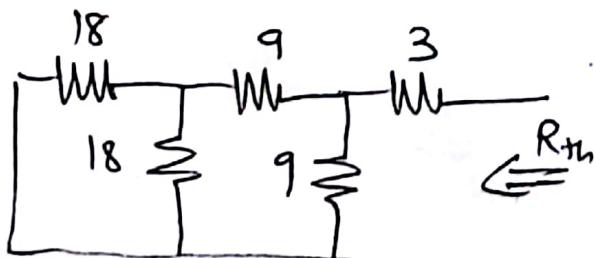

$$R_{th} = [(18 \parallel 18) + 9] \parallel 9 + 3 \\ = 9\Omega$$


Step 3

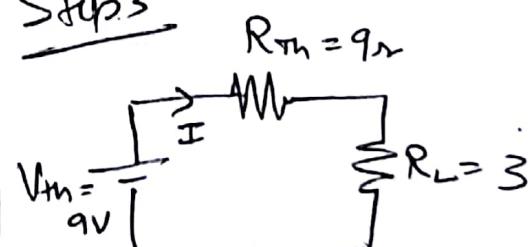

$$I = \frac{V_{th}}{R_{th} + R_L} = \frac{9}{9+3}$$


$$= 0.75A$$

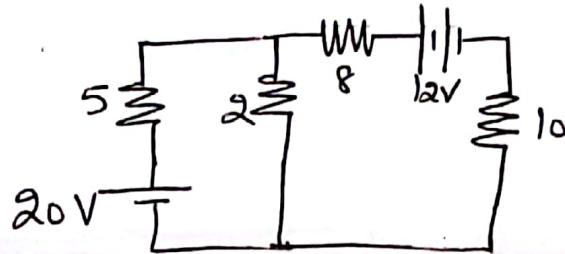Q. For the circuit calculate the current in  $10\Omega$  resistance B 7  
using Thevenin Theorem.



Step 1

Remove  $10\Omega$  resistance

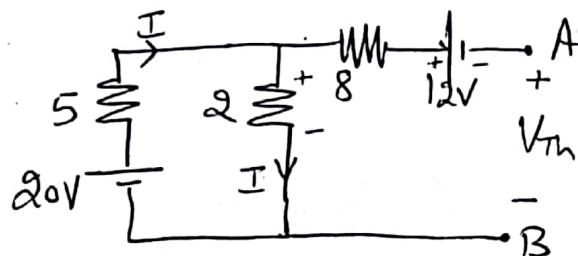

$$I = \frac{20}{5+2} = \frac{20}{7} A$$


Applying KVL,  $V_{Th} + 12 - 2I = 0$

$$V_{Th} = -12 + 2I$$

$$\begin{aligned} V_{Th} &= -12 + 2 \times \frac{20}{7} \\ &= -6.29V \end{aligned}$$



[ No current will flow  
in  $8\Omega$  resistance,  
so voltage drop  
across it is zero ]

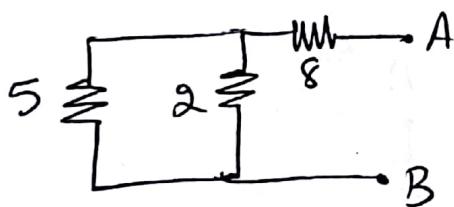Step 2 Replace the ~~batteries~~ batteries by short circuit



$$R_{Th} = 5//2 + 8 = 9.43\Omega$$


Step 3 Thevenin Equivalent circuit

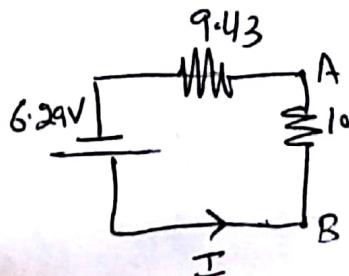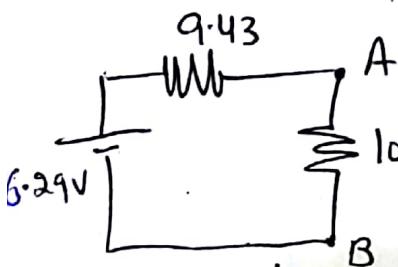

$$I = \frac{6.29}{9.43 + 10} = 0.32A$$

Current flows from B to A.

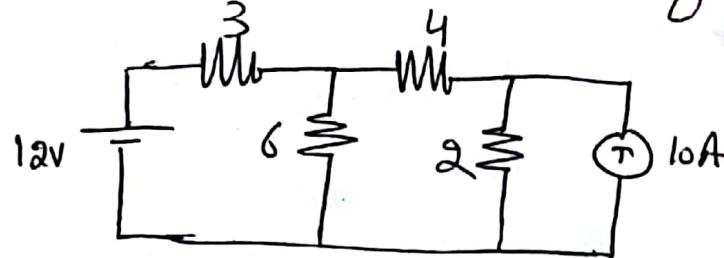Q) Using Thevenin Theorem, calculate the current flowing through  $4\Omega$  resistor



Ans Step 1 Remove  $4\Omega$  resistor



$$\text{Drop across } 6\Omega = 6 \times \frac{4}{3} = 8V$$

$$\text{Drop across } 2\Omega = 10 \times 2 = 20V$$

Applying KVL,


$$V_{Th} - 8 + 20 = 0$$

$$V_{Th} = -12V$$

Step 2


12V battery has been short circuited

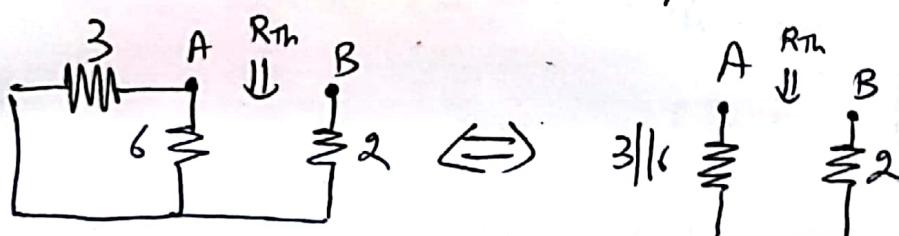10A Current source has been open circuited



$$R_{Th} = 3 || 6 + 2 = 4\Omega$$

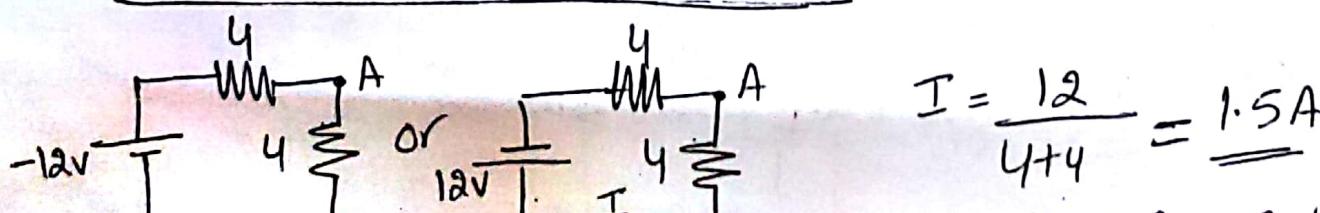Step 3 Thevenin Equivalent ~~Parallel~~ Circuit



Current flows from B to A.

## NORTON'S THEOREM

B(8)


Statement: The current flowing through a resistance connected across any two terminals of a network can be determined by replacing the whole network by an equivalent circuit of a current source having a current output of  $I_N$  in parallel with resistance  $R_N$ .

Where  $I_N$  = Short circuit current supplied by the source  
(Norton Current) that would flow between the two selected terminals when they are short circuited.


$R_N$  = Equivalent Resistance of the network as seen from the two terminals with all other emf sources replaced by their internal resistance and current source replaced by open circuit.
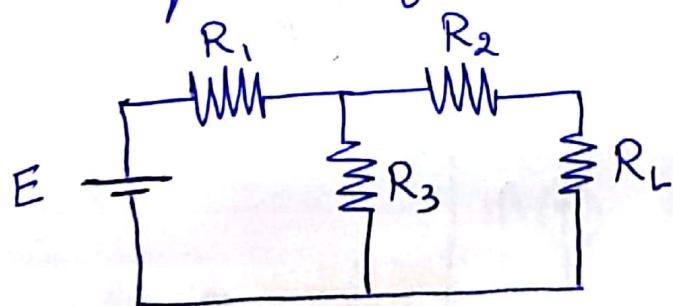
### Explanation:

Suppose it is required to find current in load resistance  $R_L$



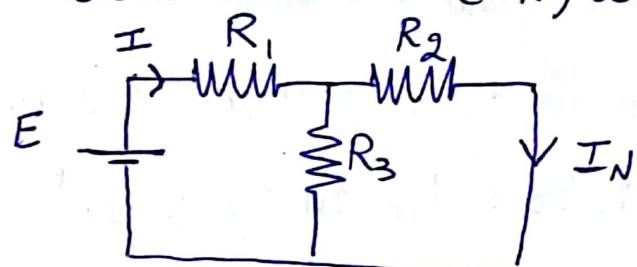
- ① Short circuit the terminals across which load resistor is connected and calculate current ( $I_N$ ) which would flow between them.



$$I = \frac{E}{R_1 + (R_2 \parallel R_3)}$$


$$I_N = \frac{R_3}{R_2 + R_3} \times I$$

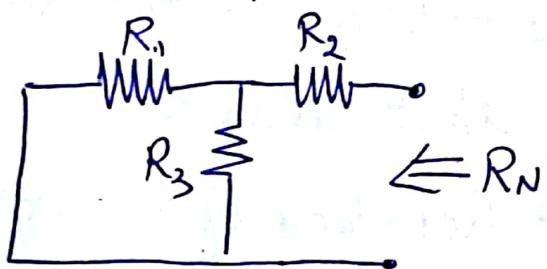- ② Replace voltage source by short circuit and calculate  $R_N$  b/w terminals across which load is connected.



$$R_N = (R_1 \parallel R_3) + R_2$$

- ③ Norton's Equivalent Circuit

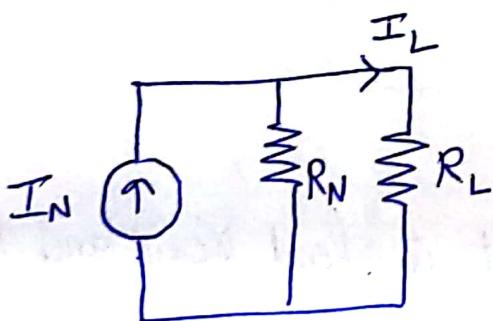


$$I_L = \frac{R_N}{R_N + R_L} \times I_N$$

(Applying current division formula)

d. Apply Norton's Theorem to calculate current flowing through


5Ω resistor of n/w shown

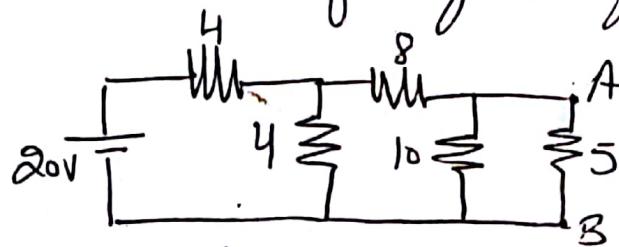

Ans

Step 1 Remove 5Ω resistor and put short across terminals A and B and find  $I_N$


A and B and find  $I_N$

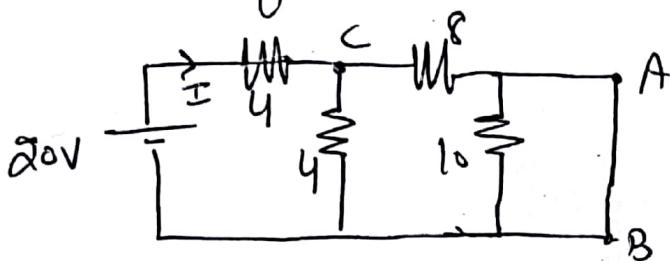

$$\text{Total Resistance seen by the battery} = 4 + (4//8) = \frac{20}{3} \Omega$$

$$\text{Current } I_B = \frac{20}{\frac{20}{3}} = 3A$$

(3 A) Current divides at point C

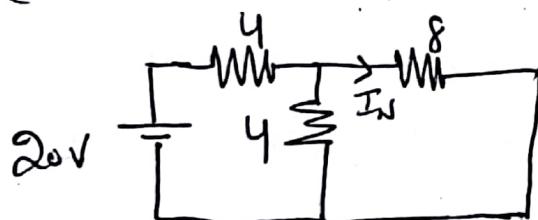


Current flowing through 10Ω resistance is 0A.

$$I_N = \frac{4}{4+8} \times 3 = 1A$$

Step 2

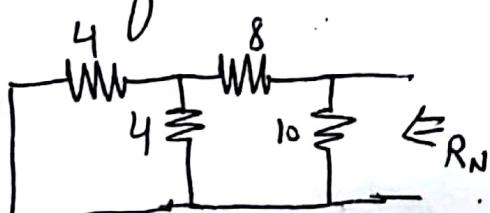
Battery has been removed and replaced by short circuit




$$R_N = (4//4+8) // 10$$

$$= (2+8) // 10 = 10 // 10 = 5\Omega$$

Step 3 Norton's Equivalent Circuit


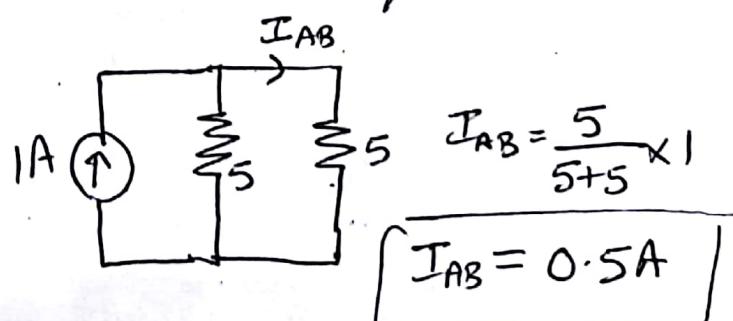


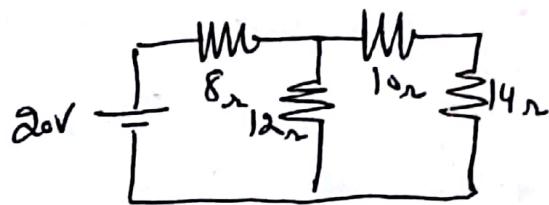Q Using Norton's Theorem determine the current in  $12\Omega$  in the n/w shown





Ans

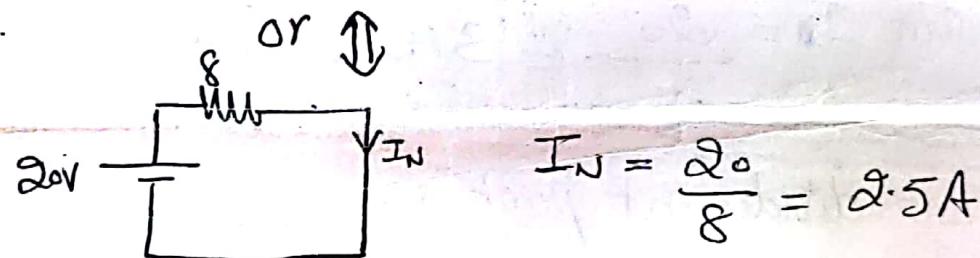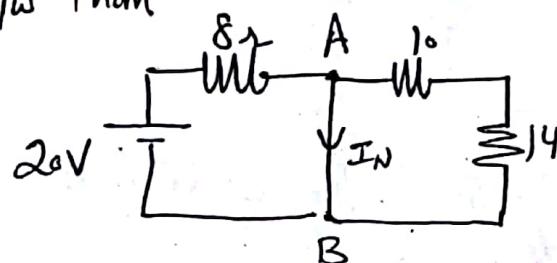Step 1:  $12\Omega$  resistor is removed and replaced by short circuit and calculate current  $I_N$  which would flow b/w them.



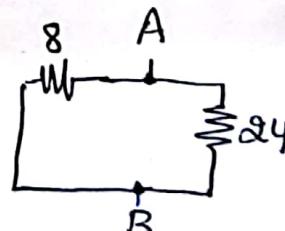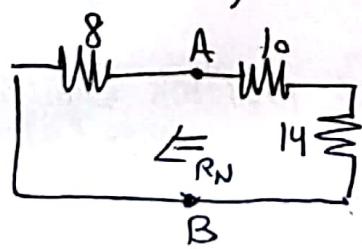
Step 2 Voltage Source is replaced by its internal resistance (zero in this case) and calculate  $R_N$



$$R_N = 8 // 24 = 6\Omega$$

Step 3

Norton Equivalent Circuit

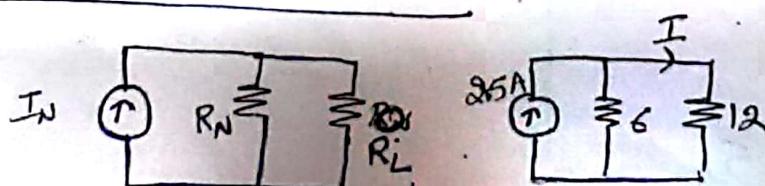


$$I = \frac{6}{6+12} \times 2.5 = 0.833A$$
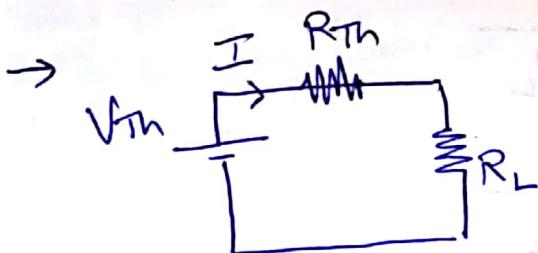
## Maximum Power Transfer Theorem

B (10)

→ Statement: The output obtained from a network is maximum when the load resistance  $R_L$  is equal to the internal resistance of the network as seen from the terminals of load.



$$\text{Current, } I = \frac{V_{Th}}{R_{Th} + R_L}$$

$$\text{Power Delivered to the load} = I^2 R_L$$

$$P = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

→ Power will be maximum if  $\frac{dP}{dR_L} = 0$

$$\frac{d}{dR_L} \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L = 0$$

$$V_{Th}^2 \left[ \frac{(R_{Th} + R_L)^2 - 2R_L(R_{Th} + R_L)}{(R_{Th} + R_L)^4} \right] = 0$$

$$(R_{Th} + R_L)^2 - 2R_L(R_{Th} + R_L) = 0$$

$$(R_{Th} + R_L)^2 = 2R_L(R_{Th} + R_L)$$

$$R_{Th} + R_L = 2R_L$$

$$\boxed{R_{Th} = R_L}$$

Internal Resistance = Load Resistance


→ Hence, it is proved that max. power is transferred to the load resistance  $R_L$ , when  $R_L$  is equal to  $R_{Th}$ .

$$\begin{aligned}\rightarrow \text{Max. Power Delivered to load} &= \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L = \left( \frac{V_{Th}}{R_L + R_L} \right)^2 R_L \\ &= \frac{V_{Th}^2}{4 R_L} \\ &= \frac{V_{Th}^2}{4 R_{Th}}\end{aligned}$$


$$(\frac{V^2}{R+2}) = 9$$

$$9 = \left( \frac{V^2}{R+2} \right) \frac{12}{25}$$

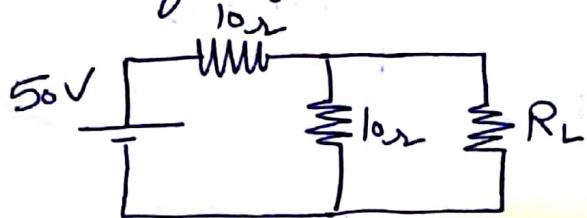Q1 Calculate the value of  $R_L$  so that max. Power is transferred from the battery for the circuit shown.



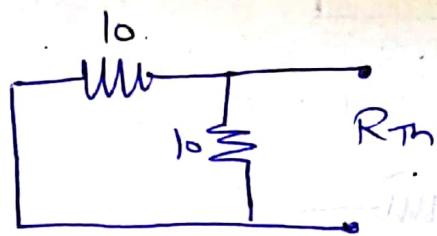
Ans Max. Power is delivered when  $R_L = R_{Th}$





$$R_{Th} = \frac{10 \times 10}{10 + 10} = 5\Omega$$

$$R_L = R_{Th} = 5\Omega$$

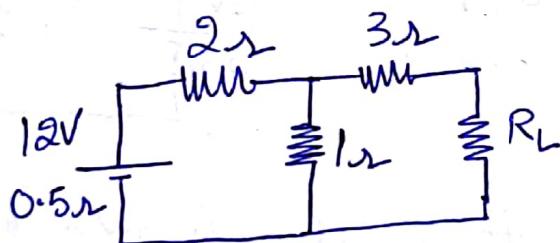Q2 Find the value of  $R_L$  at which max. Power is transferred to  $R_L$  and hence max. Power transferred to  $R_L$  in the circuit



Ans To find  $R_{Th}$

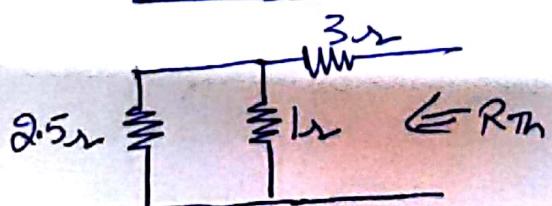
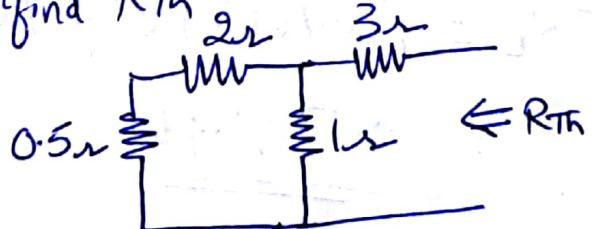


Parallel combination of  
2.5 and 1 =  $0.7143\Omega$


Series combination of  $0.7143$  and  $3$

$$R_{Th} = 3.7143\Omega$$

Max Power

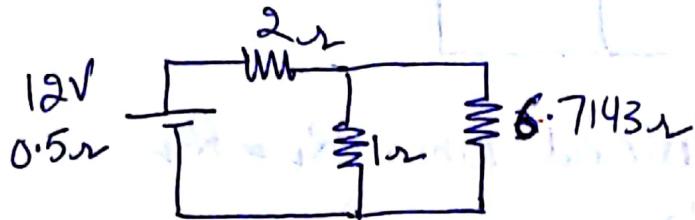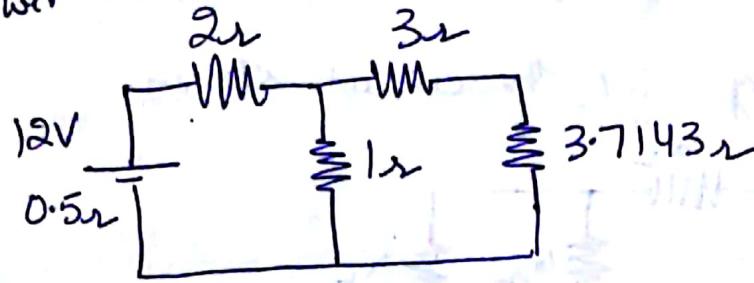

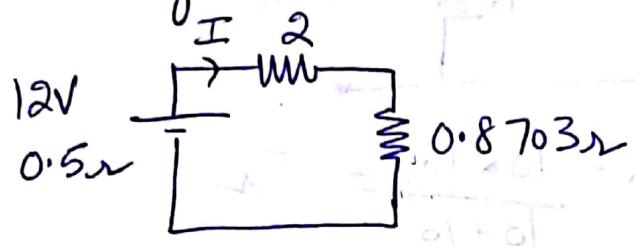
Parallel combination of 1 and  $6.7143\Omega$  =  $0.8703\Omega$



$$\text{Main Current, } I = \frac{12}{0.5 + 2 + 0.8703} = 3.5604 \text{ A}$$

→ Current through Resistance  $R_L$  is given by
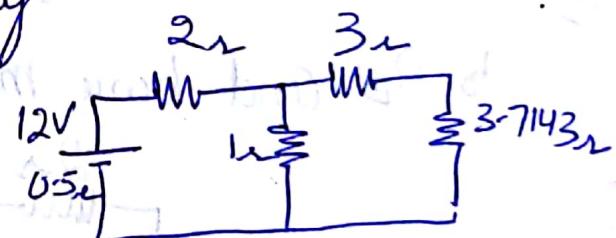
$$\frac{1}{1 + 6.7143} \times 3.5604$$
$$= 0.4615 \text{ A}$$




→ Max. Power Transferred to resistor is given by

$$= I^2 R_L = (0.4615)^2 \times 3.7143$$


$$= \underline{\underline{0.79119 \text{ W}}}$$

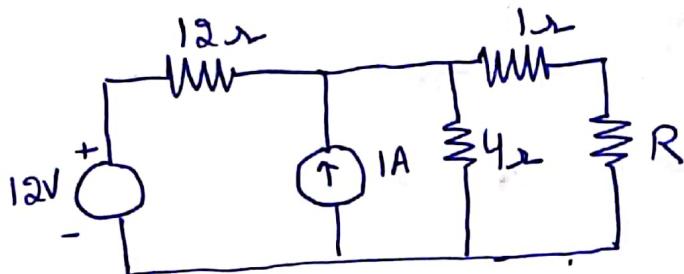Q For the circuit shown, derive the Thevenin's and Norton's equivalent wrt load resistance R




Ans

①

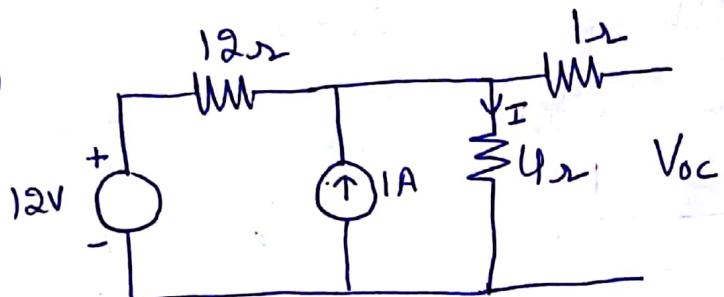

$$V_{oc} = 4I$$

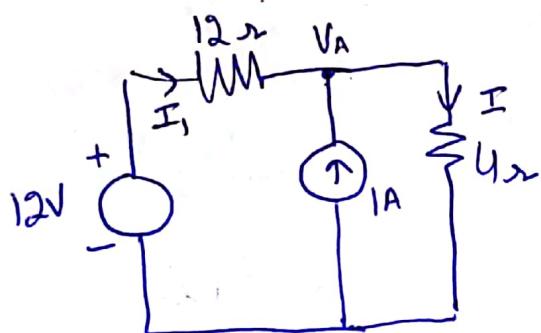

Solve for I using Nodal

$$I_1 + 1 = I$$


$$\frac{12 - V_A}{12} + 1 = \frac{V_A}{4}$$

$$V_A = 6V$$

$$I = \frac{V_A}{4} = \frac{6}{4} A$$

$$V_{oc} = \frac{6}{4} \times 4 = 6V$$


②

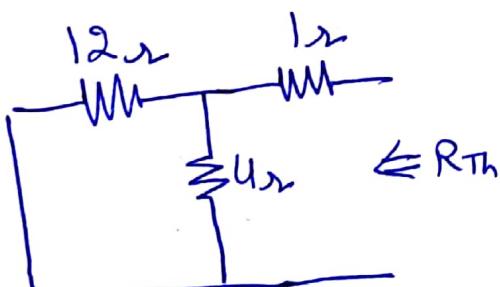


$$R_{Th} = (12 || 4) + 1 \\ = 3 + 1 = 4\Omega$$

③


Thevenin Equivalent circuit

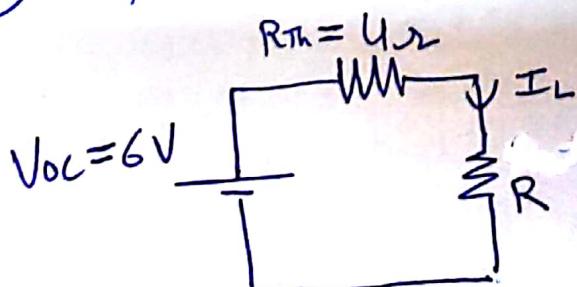

## Norton's Theorem

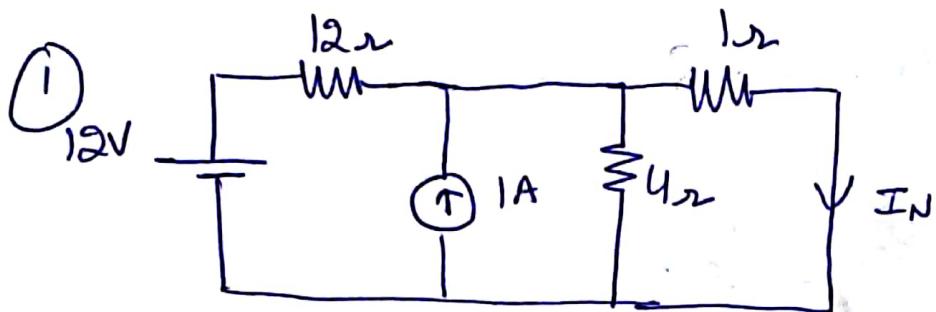

Applying Nodal for  $I_N$

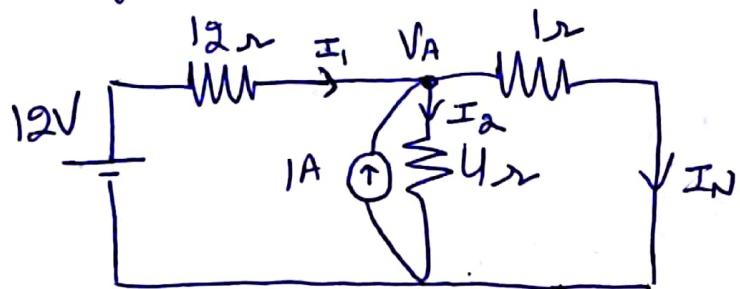


$$I_1 + 1 = I_2 + I_N$$

$$\frac{12 - V_A}{12} + 1 = \frac{V_A}{4} + \frac{V_A}{1}$$

$$V_A = \frac{3}{2} V$$

$$I_N = \frac{V_A}{1} = \frac{3}{2} A$$

②

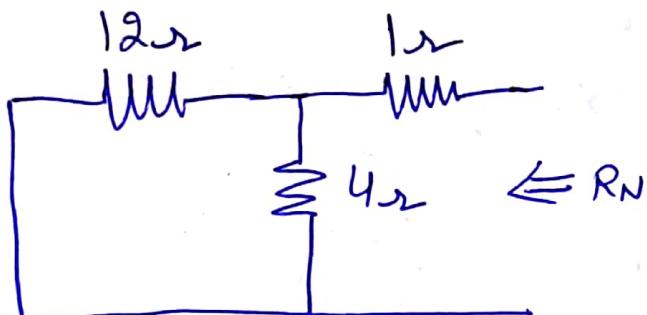

$$R_N = (12 || 4) + 1$$

$$= 4\Omega$$

③

Norton's Equivalent Ckt.

